

Calculating the "Loop Gain" of a feedback circuit

Why do we need Loop Gain??

- 1) Can calculate "Rin" and "Rout" in presence of feedback

Shunt:  $R_{inF} = \frac{R_{in}}{(1 + \text{Loop Gain})}$  ;  $R_{outF} = \frac{R_{out}}{(1 + \text{Loop Gain})}$



Series:  $R_{inF} = R_{in}(1 + \text{Loop Gain})$  ;  $R_{outF} = R_{out}(1 + \text{Loop Gain})$

- 2) To find the stability of a negative feedback loop.

There are two methods for calculating the Loop gain :-

- 1) Direct
- 2) Successive voltage and current injection

Example of Direct method

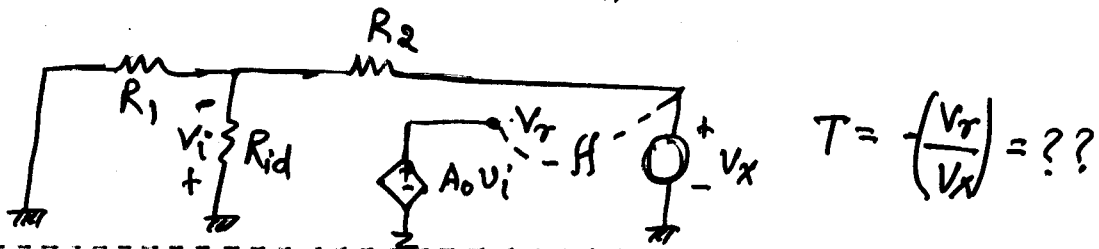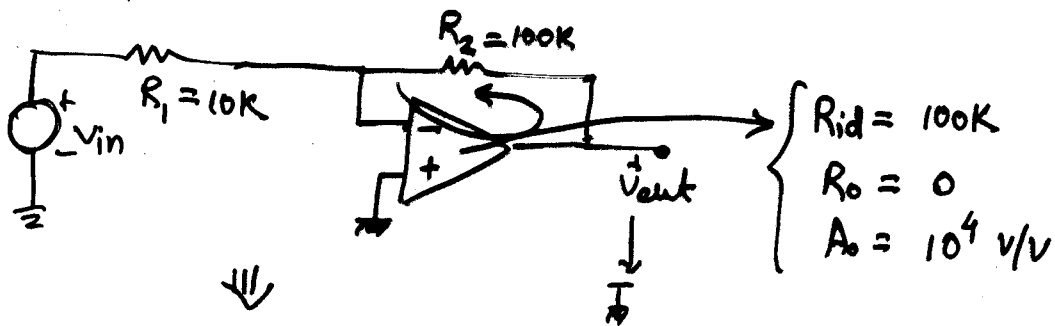


$$V_r = -10^4 v_i = 10^4 \underbrace{\left( \frac{-R_{id} \parallel R_1}{R_2 + R_{id} \parallel R_1} \right)}_{v_i} v_x$$

$$T = \frac{V_r}{V_x} = -10^4 \left( \frac{9.09}{109.09} \right) = -83.33$$

### Stability of Feedback Amplifiers

$$A_F(s) = \frac{A(s)}{1 + A(s)B(s)} = \frac{A(s)}{1 + T(s)}$$



$$T(s) = A(s)B(s)$$

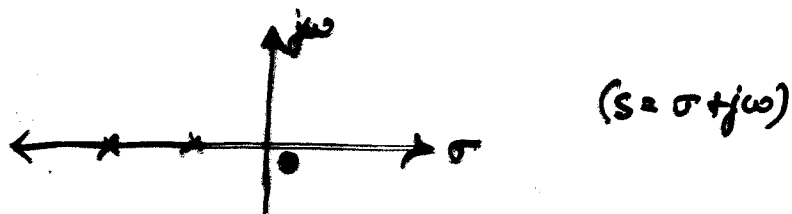


Two approaches:-

① Nyquist approach -


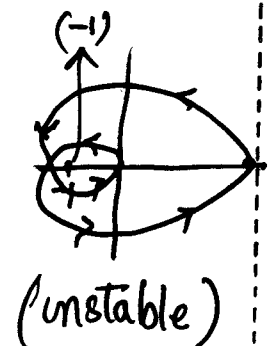
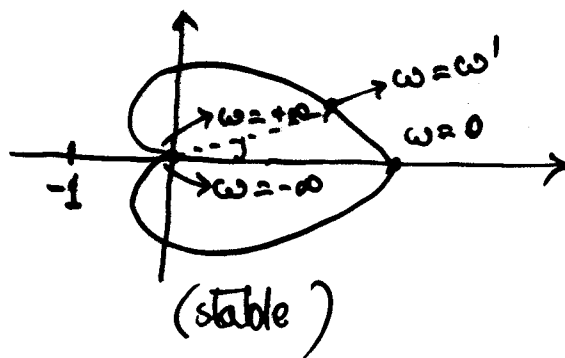
Plot  $T(j\omega)$  on a complex plane, varying  $\omega$  from  $-\infty$  to  $+\infty$ .



Bode plot


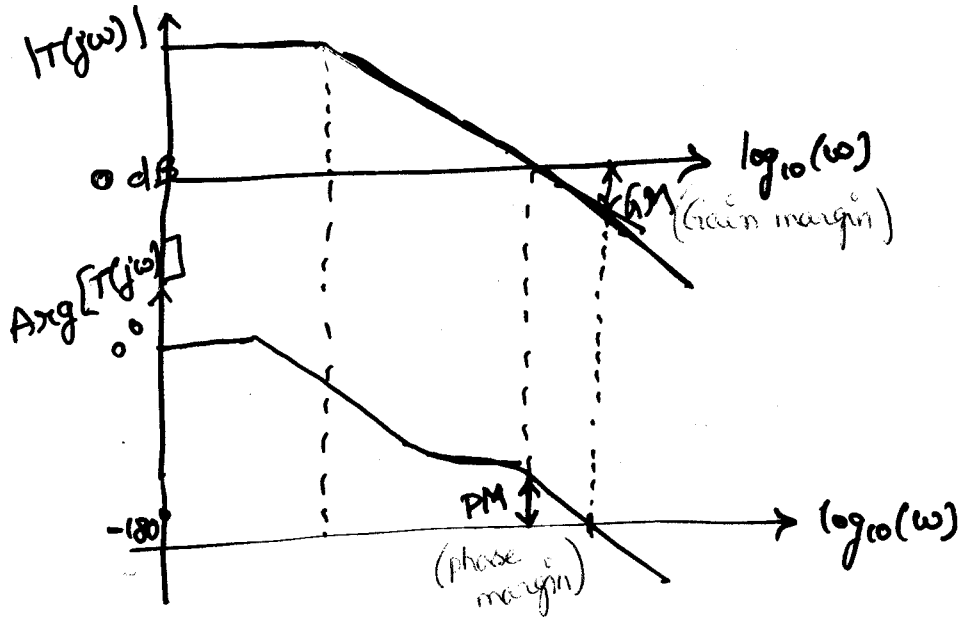


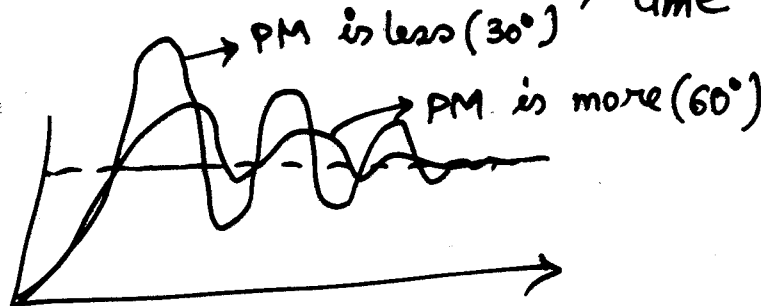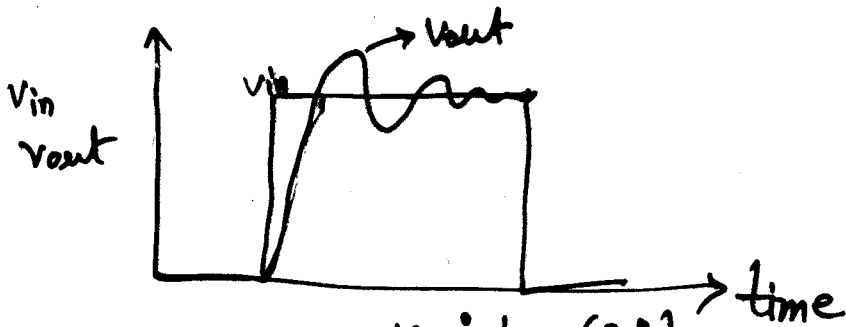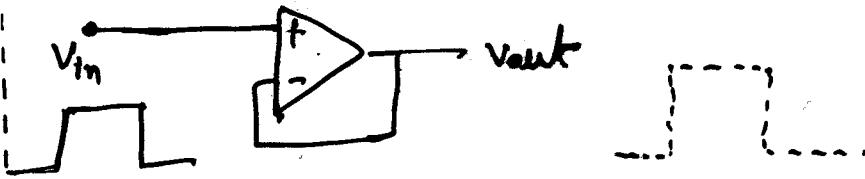- ① Phase margin (PM)
- ② Gain margin (GM)



$$A(s) = \frac{10^3}{\left(1 + \frac{s}{100}\right)\left(1 + \frac{s}{10^5}\right)} ; B(s) = 1$$

$$T(s) = A(s) \cdot B(s)$$

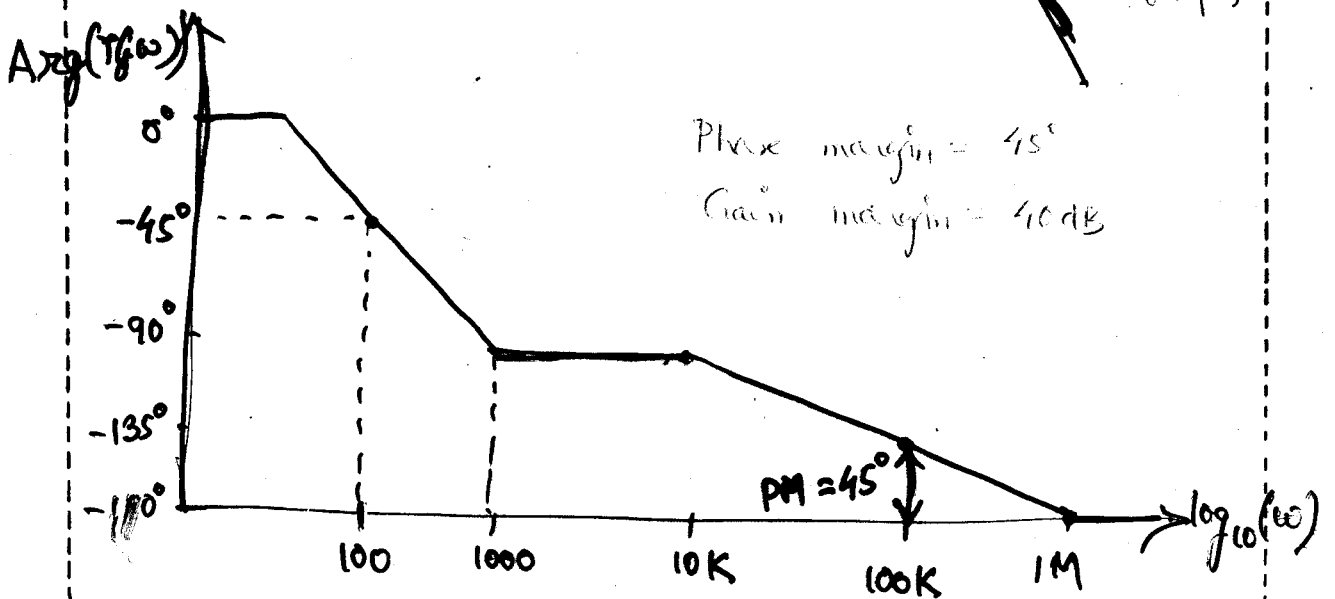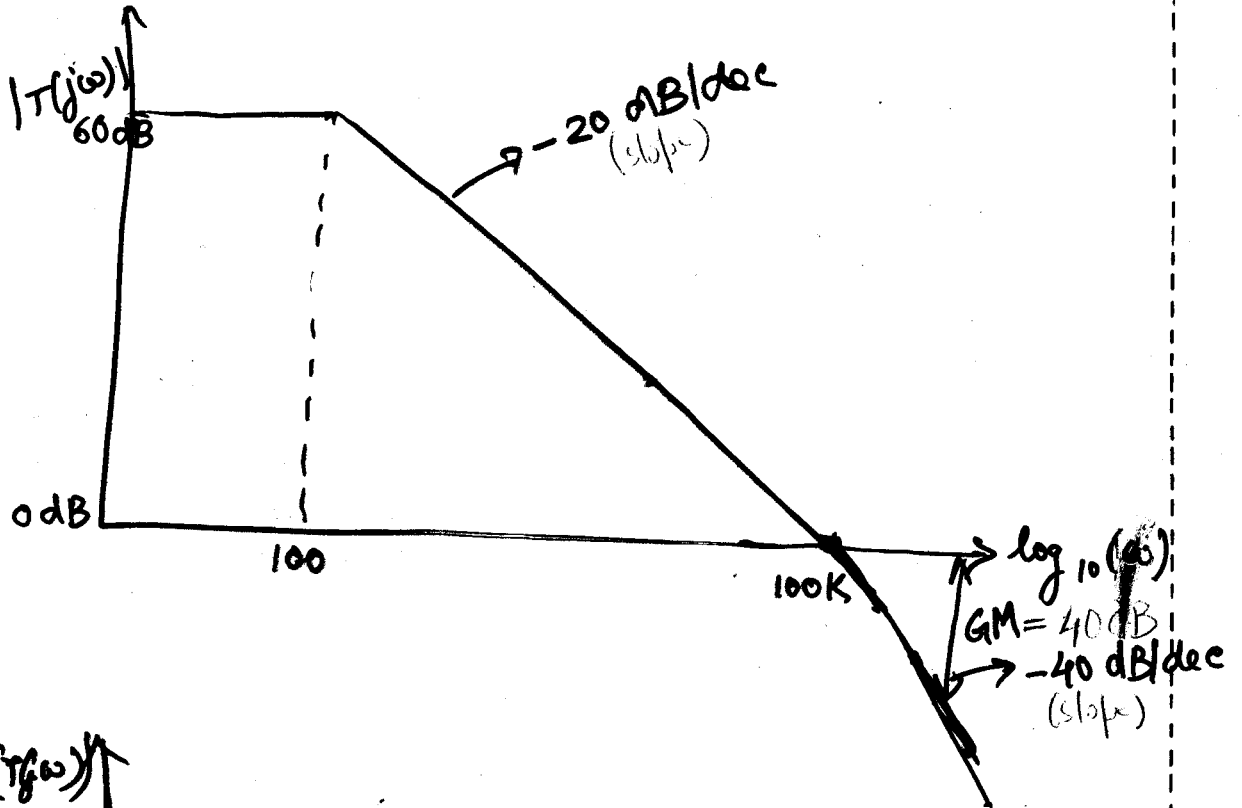

$R_{in}$  /  $R_{out}$  with feedback

1. Draw the circuit without feedback.
2. Find  $R_{in}/R_{out}$  without feedback.
3. Find Loop-gain ( $T$ )
4. If input signal is

$$\left. \begin{array}{l} \text{a) Voltage} \rightarrow R_{in}(1+T) \\ \text{b) Current} \rightarrow \frac{R_{in}}{(1+T)} \end{array} \right\} R_{inF}$$

If output signal is

$$\left. \begin{array}{l} \text{a) Voltage} \rightarrow \frac{R_o}{(1+T)} \\ \text{b) Current} \rightarrow R_o(1+T) \end{array} \right\} R_{outF}$$