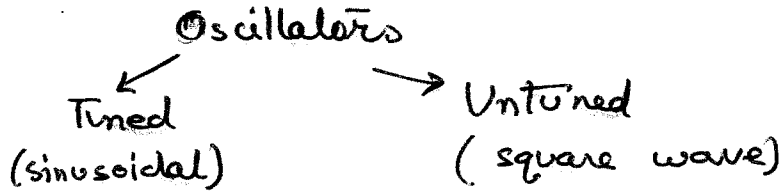
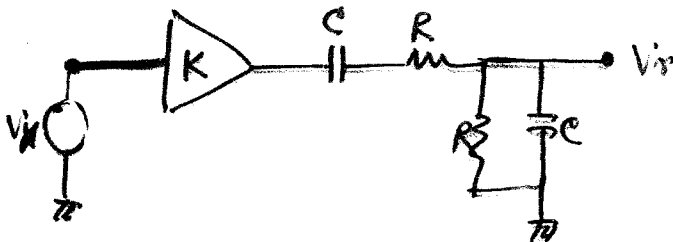
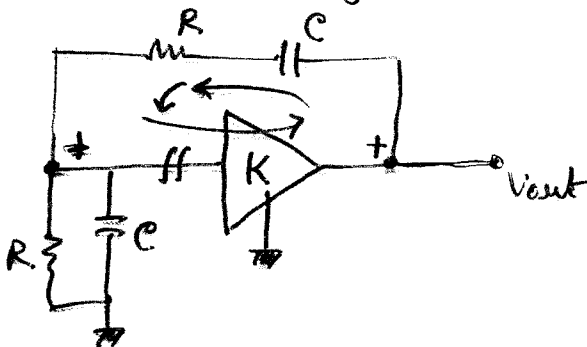


Oscillators

↳ some form of positive feedback

Criteria for oscillations

Loop gain: $T(j\omega) = 1 + j0$ or $1 \angle 0^\circ$

Wien Bridge Oscillator

$$T = \frac{V_y}{V_x}$$

$$T(s) = \frac{V_y}{V_x} = \frac{K \cdot (R \parallel \frac{1}{sC})}{(R \parallel \frac{1}{sC}) + R + \frac{1}{sC}}$$

$$T(s) = \frac{s K R C}{(s^2 R^2 C^2 + s 3 R C + 1)}$$

$$T(j\omega) = \frac{j\omega KRC}{\underbrace{(1 - \omega^2 R^2 C^2)}_{=0} + j3\omega RC} \approx (1) + j0$$

$$(1 - \omega^2 R^2 C^2) = 0 \Rightarrow T(j\omega) = \frac{K}{3} \approx 1 + j0$$

$$\downarrow$$

$$\boxed{\omega = \omega_{osc} = \frac{1}{RC}}$$

$$\downarrow$$

$$\boxed{K=3}$$


Ex.

$$R = 10k\Omega, C = 0.1\mu F$$


$$\omega_{osc} = \frac{1}{R \cdot C} = 10^3 \text{ rad/sec}$$

Amplitude stabilization.

Amplifier transfer function

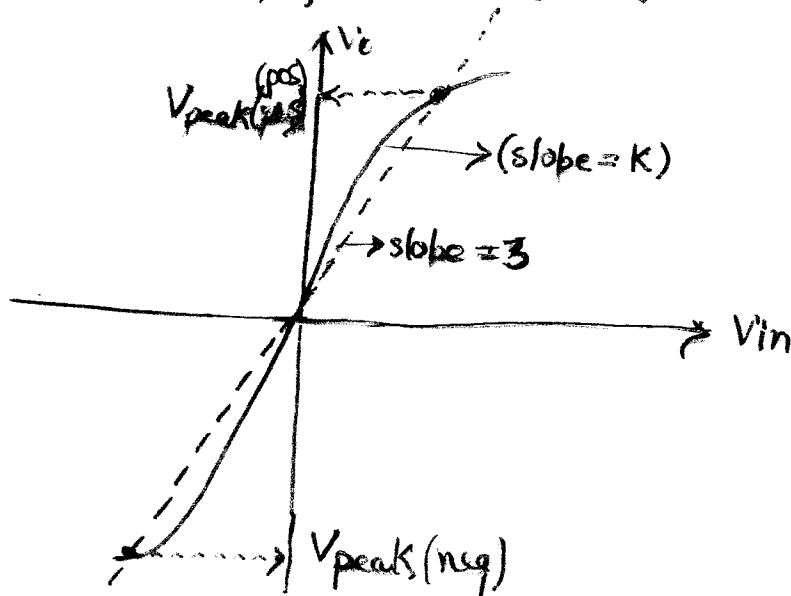

Modified Wien Bridge Oscillator

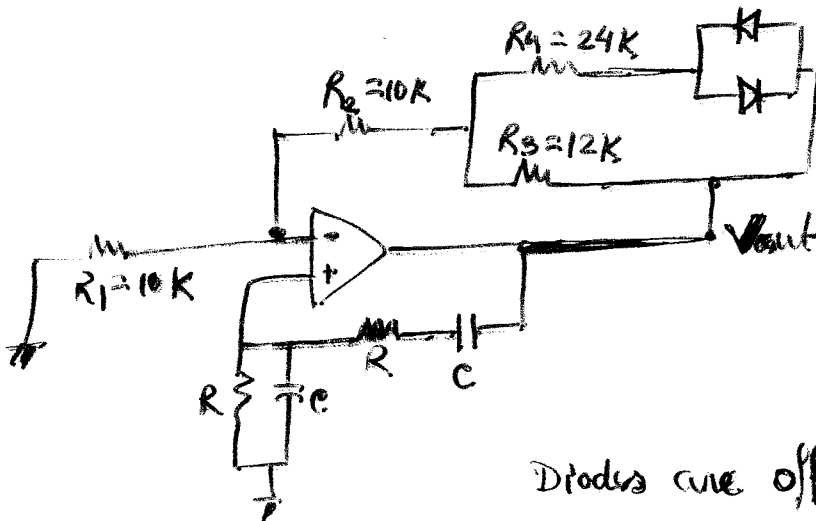

Diodes are off

$$\text{Gain (K)} = \frac{R_1 + R_2 + R_3}{R_1} = 3.2$$

Diodes are on

$$\text{Gain (K)} = \frac{R_1 + R_2 + (R_3 // R_4)}{R_1} = 2.8$$