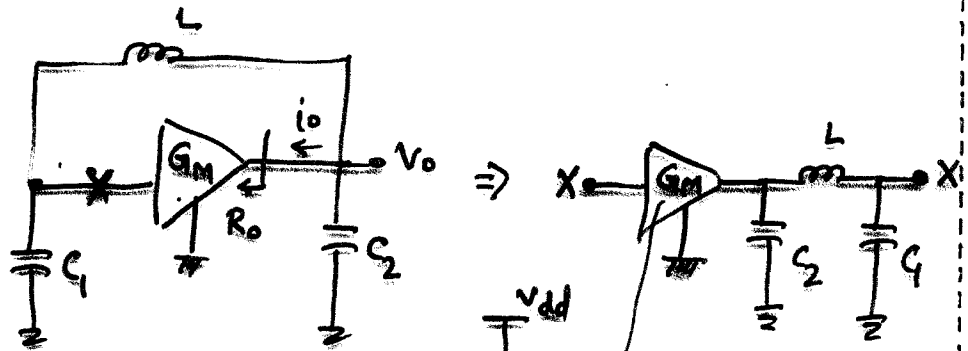


Oscillators


LC oscillators

1) Colpitts Oscillator




$$\omega_{osc} = \frac{1}{\sqrt{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)}}$$

$$G_m R_o = \frac{C_2}{C_1}$$

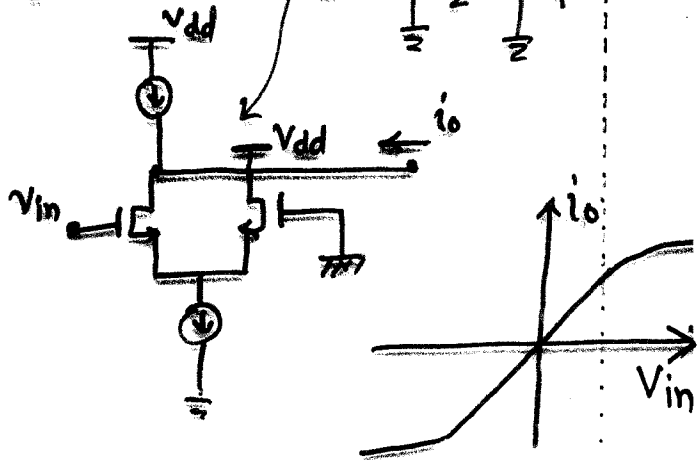



2) Hartley Oscillator

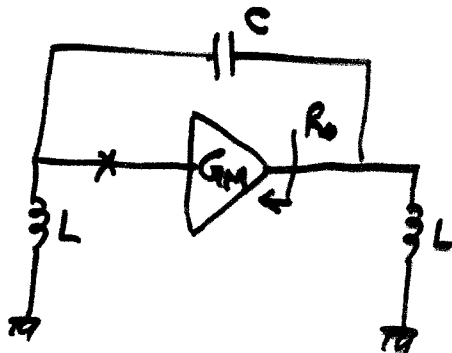


$$\omega_{osc} = \frac{1}{\sqrt{L_1 L_2}}$$

$$G_m R_o = \frac{L_1}{L_2}$$

### 3) LC oscillator

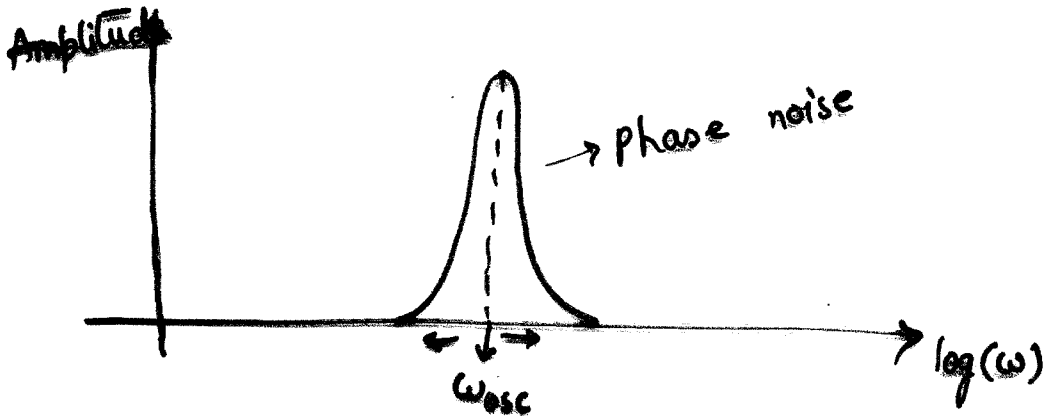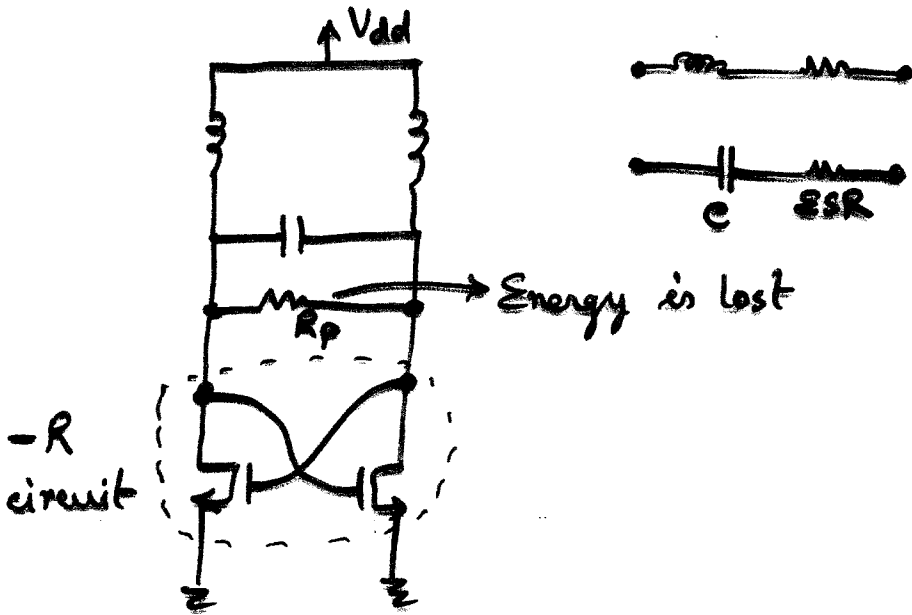

Ex

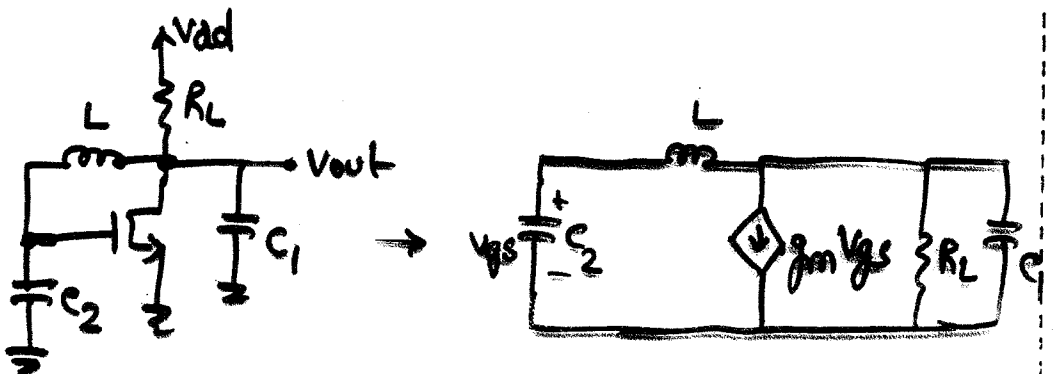

Nodal Equations -

$$\textcircled{1} \quad g_m V_{gs} + G_L V_{out} + sC_1 V_{out} + \frac{V_{out} - V_{gs}}{sL} = 0$$

$$\textcircled{2} \quad \frac{V_{out} - V_{gs}}{sL} = sC_2 V_{gs}$$

$T(j\omega)$

$$\Rightarrow (g_m + G_L - \omega^2 L C_2 G_L) + j\omega (C_1 - \omega^2 L C_1 C_2 + C_2) = 0$$

$$= 1 + j0 \leftarrow$$

$$\textcircled{1} \quad \omega_{osc} (C_1 - \omega_{osc}^2 L C_1 C_2 + C_2) = 0$$

$$\omega_{osc} = \frac{1}{\sqrt{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)}}$$

$$\textcircled{2} \quad (g_m + G_L - \omega_{osc}^2 L C_2 G_L) = 1$$

↓

$$g_m R_L = \frac{C_2}{C_1}$$