

"Quiz 12":

IEEE SSCS/CAS Atlanta Chapter Meeting

6:30pm - Refreshments


7:00pm - "Fundamental Property of MOS Transistors and Its Circuits Implications" - Dr. Eric Vittoz
Swiss Institute of Technology, Lausanne

ECE Auditorium

Quiz 11 - Solution


$g_m = 1 \text{ mA/V}$ and $r_{ds} = \infty$

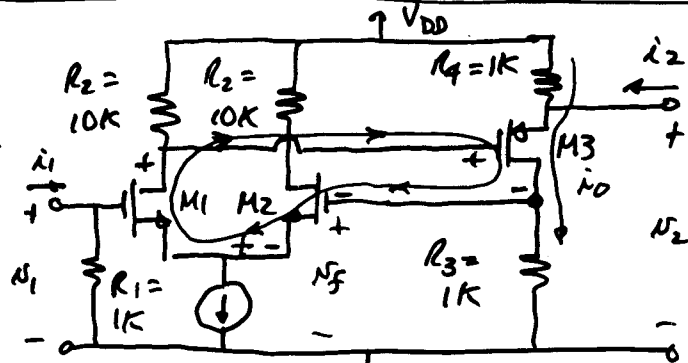Find $\frac{N_2}{N_1}$, $\frac{i_1}{i_2}$ & $\frac{N_2}{i_2}$





Solution

Identification of type of feedback:

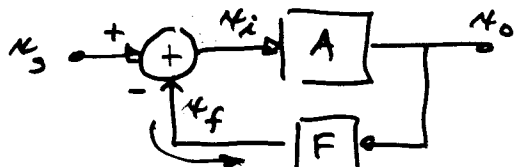

$$N_i = N_3 - N_f \rightarrow N_i = N_3 - N_f$$

$$i_i = i_3 - i_f$$

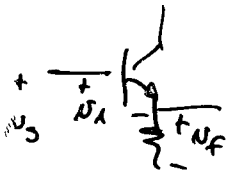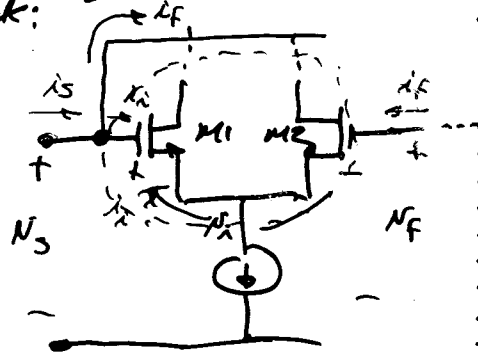


Redraw the circuit as open-loop:

A units are $\frac{A}{V}$

F units are $\frac{V}{A}$

$$F = \frac{N_f}{i_0} = 1k = R_3$$

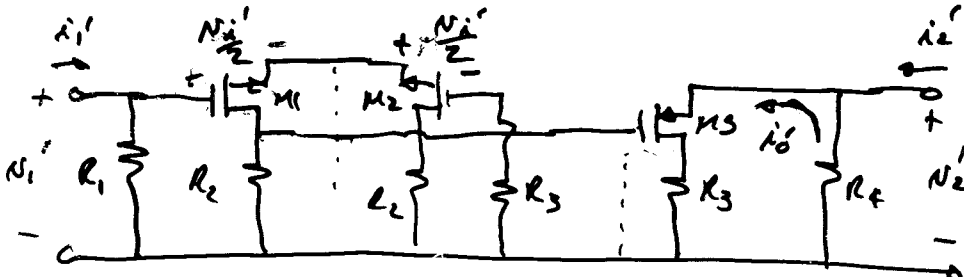

Rules for opening the loop (and finding the loading of the F network on the A network):

1.) Looking back into the F circuit from the input:

Short the output ^{node} if shunt (make $N_{out} = 0$)

Open the output if series (make $i_o = 0$)


2.) Looking back into the F ckt. from the output:

Short the input node if shunt

Open the input loop if series

$$A = \frac{i_o'}{v_s'}$$

$$N_s' = 2.5 \mu s$$

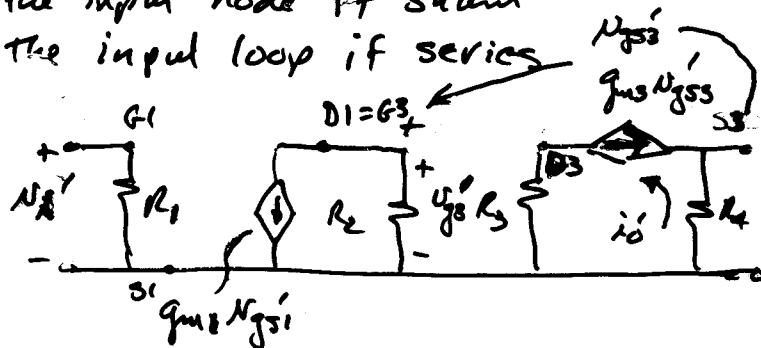

$$\frac{i_o'}{v_s'} = \left(\frac{i_o'}{v_{gs3}'} \right) \left(\frac{v_{gs3}'}{v_{gs3}''} \right) \left(\frac{v_{gs3}''}{v_{gs1}'} \right) \left(\frac{i_o'}{v_s'} \right) = (-g_{m3})$$

$$N_{gs3} = v_{gs3} - v_{gs3}' = v_{gs3} - (g_{m3} R_4 v_{gs3})$$

$$N_{gs3} (1 + g_{m3} R_4) = v_{gs3}$$

$$A = \frac{i_o'}{v_s'} = (-g_{m3}) \left(\frac{1}{1 + g_{m3} R_4} \right) (-g_{m1} R_2) \left(\frac{1}{2} \right) = 2.5 \mu s$$

$$\therefore A_F = \frac{i_o}{v_s} = \frac{A}{1 + AF} = \frac{2.5 \mu s}{1 + (2.5)(6)} = 0.714 \mu s$$

$$\frac{v_2}{v_1} = \frac{v_2}{v_s} = \left(\frac{i_o}{v_s} \right) (R_4) = \underline{\underline{0.714 V/V}}$$

R_1 is not influenced by feedback so

$$\frac{v_1}{i_1} = R_2 (1 + AF) \parallel R_1 = \infty \parallel R_1 = \underline{\underline{1 k\Omega}}$$

$$R_o = R_4 + \frac{1}{g_{m3}} = 1k + 1k = 2k \rightarrow R_{oF} = 2k \Omega (3.5) = 7k\Omega$$

$$R_{out} = \frac{v_2}{i_2} = (R_{oF} - R_4) \parallel R_4 = 6k \parallel 1k = \underline{\underline{857\Omega}}$$