
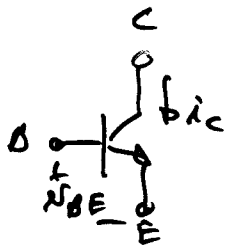
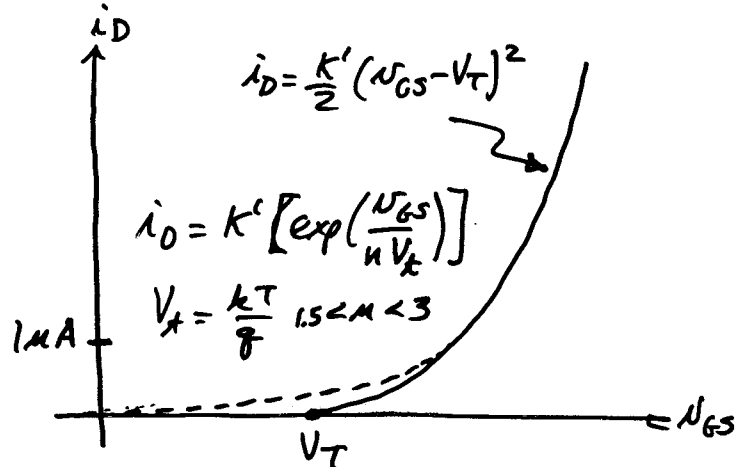


Quiz #12 due by noon today.

What is weak inversion operation for a MOSFET?




(Subthreshold)

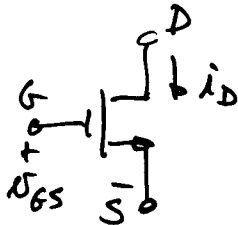


$i_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$

CHAPTER 12, SECTIONS

1.) Waveskaping Circuits

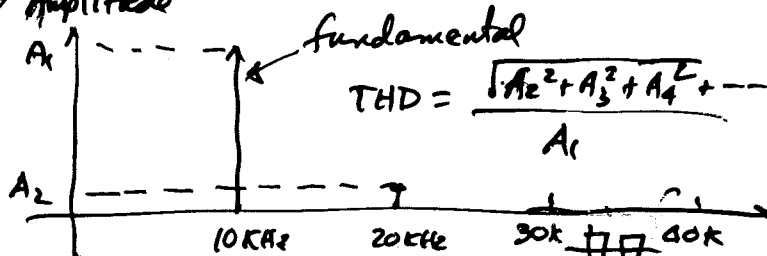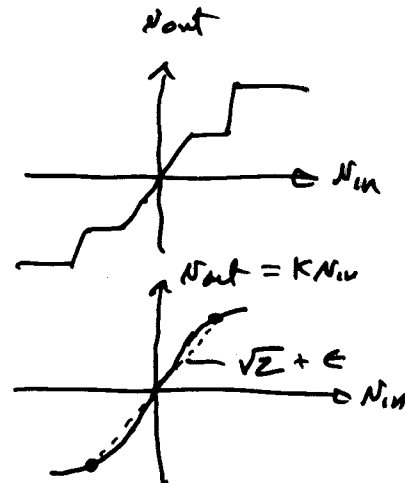
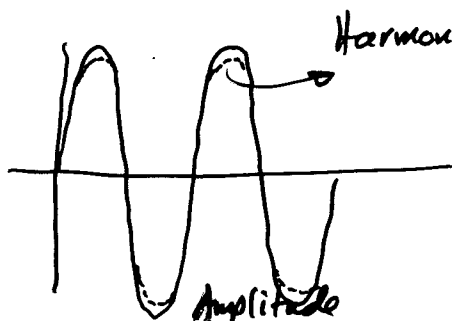


2.) Non-sinoidal oscillators


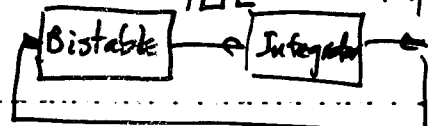


Rectification using the Op Amp

1.) No op amp (no fb)

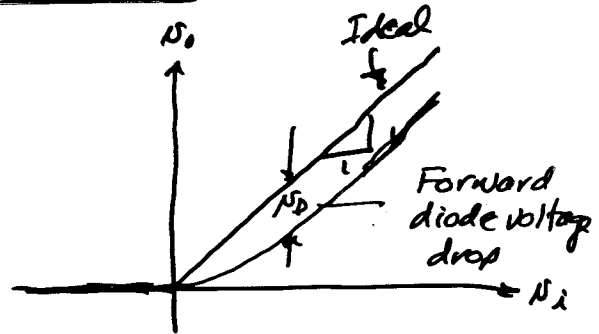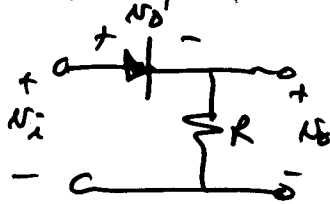

2.) With the op amp (w. fb.)

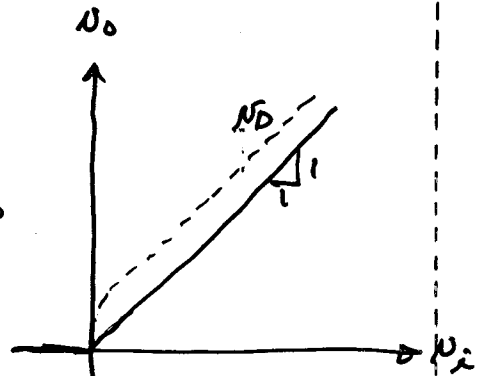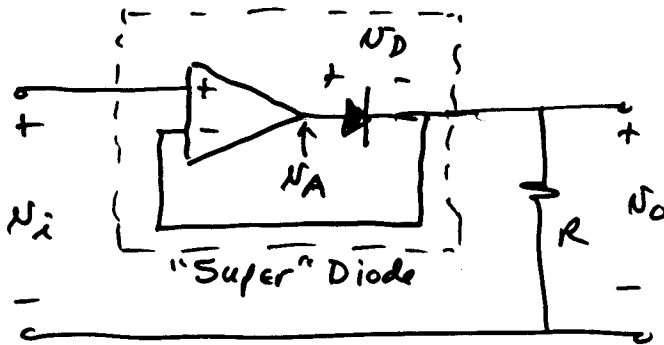


Assume \$A_v\$ is large but not infinity

$$\left. \begin{aligned} N_o &= N_A - N_D \\ N_A &= A_v (N_i - N_o) \end{aligned} \right\} \begin{aligned} N_o &= A_v (N_i - N_o) - N_D \\ N_o (1 + A_v) &= A_v N_i - N_D \end{aligned}$$

or $N_o = \frac{A_v N_i}{1 + A_v} - \frac{N_D}{1 + A_v}$ if $A_v \rightarrow \infty$, then $N_o = N_i$


3. Principle

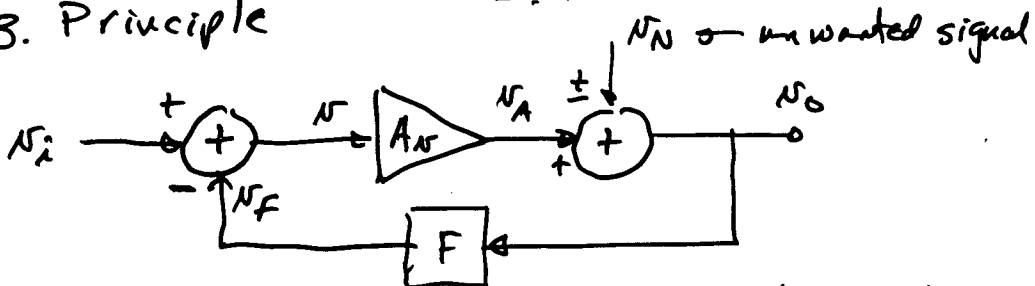

$$N_o = N_A \pm N_N = A_N (N_i - N_F) \pm N_N = A_N (N_i - F N_o) \pm N_N$$

$$N_o [1 + A_N F] = A_N N_i \pm N_N \Rightarrow N_o = \frac{A_N N_i}{1 + A_N F} \pm \frac{N_N}{1 + A_N F}$$

Precision Diode - The Op Amp Rectifier

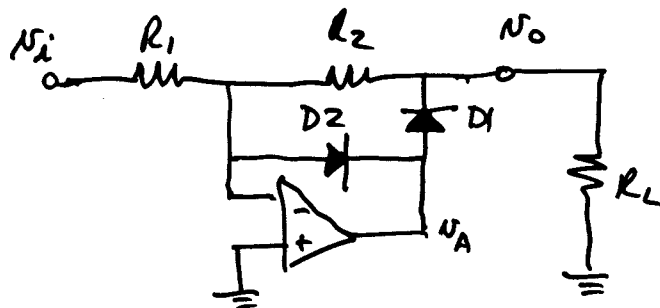


State of

N_i	D1	D2
0	OFF	OFF
> 0	OFF	ON
< 0	ON	OFF
0	ON	ON

Note: Only D1 or D2 is ON, not both

1.) D1 OFF D2 OFF is not a valid state

2.) D1 ON D2 OFF $\Rightarrow N_i < 0$

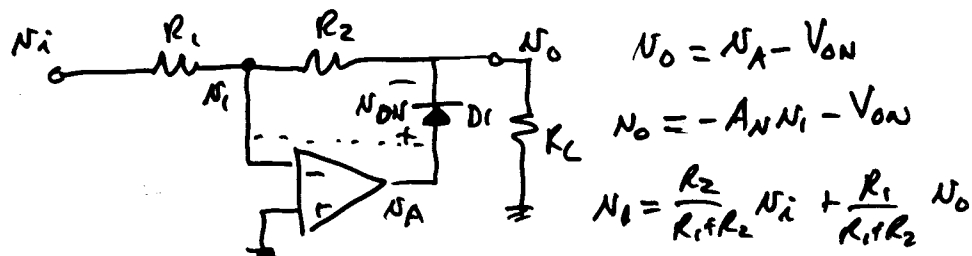


$$N_o = N_A - V_{ON}$$

$$N_o = -A_N N_i - V_{ON}$$

$$N_i = \frac{R_2}{R_1 + R_2} N_i + \frac{R_1}{R_1 + R_2} N_o$$
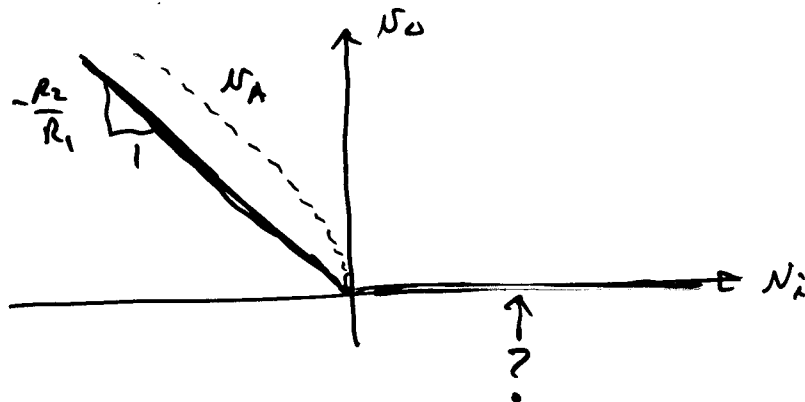
$$N_o = \left(\frac{-A_N R_2}{1 + A_N \frac{R_1}{R_1 + R_2}} \right) N_i - \frac{V_{ON}}{1 + A_N \frac{R_1}{R_1 + R_2}} \quad \underline{\underline{N_i < 0}}$$



RC Oscillator Example

Find the loop gain of the feedback circuit shown, $T(s)$, if the amplifier is an ideal voltage amplifier with a gain of K . Identify the oscillation frequency and the value of K necessary to oscillate.

Solution

Opening the loop gives,

$$T(s) = \frac{V_{out}}{V_{in}} = \left(\frac{KR}{R+(1/sC)} \right) \left(\frac{K(1/sC)}{R+(1/sC)} \right)$$

$$= \frac{K^2RCs}{(sRC+1)(sRC+1)} = \frac{K^2RCs}{s^2R^2C^2+s2RC+1}$$

$$\therefore \boxed{T(s) = \frac{K^2RCs}{s^2R^2C^2+s2RC+1}}$$

$$T(s) = \frac{sK^2RC}{s^2R^2C^2 + 2RCs + 1} \quad \rightarrow \quad T(j\omega) = \frac{j\omega K^2RC}{-\omega^2R^2C^2 + j\omega 2RC + 1}$$

$$\text{or} \quad T(j\omega) = \frac{j\omega K^2RC}{1 - \omega^2R^2C^2 + j\omega 2RC} = 1 + j0$$

To make $T(j\omega) = 1$, the term $1 - \omega^2R^2C^2$ in the denominator must go to zero. Therefore we get

$$1 - \omega_{osc}^2R^2C^2 = 0 \quad \rightarrow \quad \boxed{f_{osc} = \frac{1}{2\pi RC}}$$

Substituting this relationship back into $T(j\omega_{osc})$ gives,

$$T(j\omega_{osc}) = \frac{j\omega_{osc} K^2RC}{j\omega_{osc} 2RC} = \frac{K^2}{2} \quad \rightarrow \quad \boxed{K = \sqrt{2}}$$

KEY PRINCIPLE OF OSCILLATORS

- 1.) Find the open-loop gain, $T(j\omega)$.
- 2.) Set $T(j\omega) = 1 + j0$
- 3.) Solve for the two equations,

$$\text{Re}[T(j\omega)] = 1 \quad \text{and} \quad \text{Im}[T(j\omega)] = 0$$

- 4.) If these equations cannot be solved for real numbers for frequency and gain, then the circuit is not an oscillator.

