
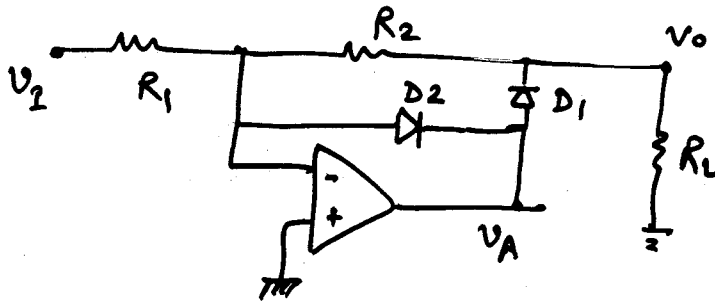



Practical Op Amp Rectifier

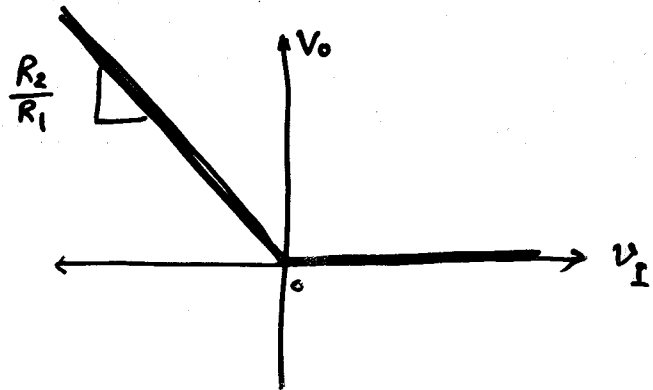



$V_1 < 0$



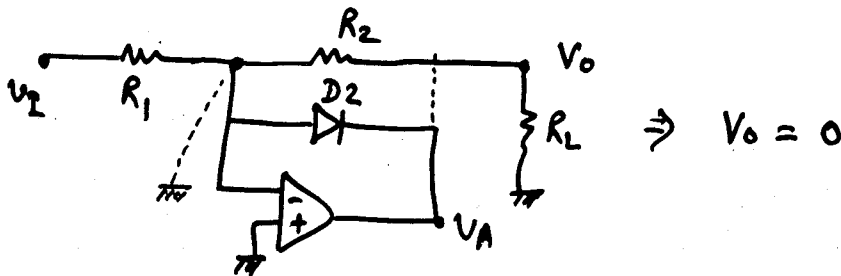$V_2 > 0$ \Rightarrow $D_2 \rightarrow$ ON, $D_1 \rightarrow$ OFF





Reverse the diodes

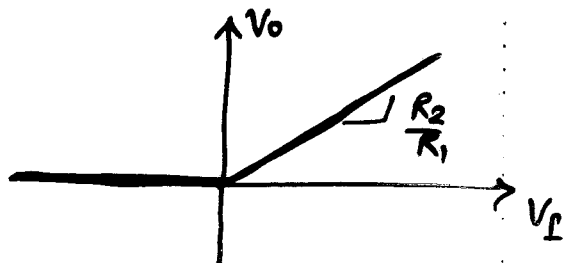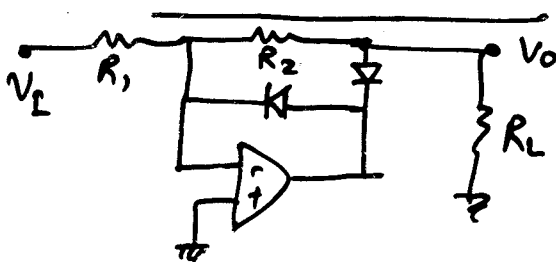


Absolute value circuit



$V_o = -|V_I|$ using precision rectifier circuit

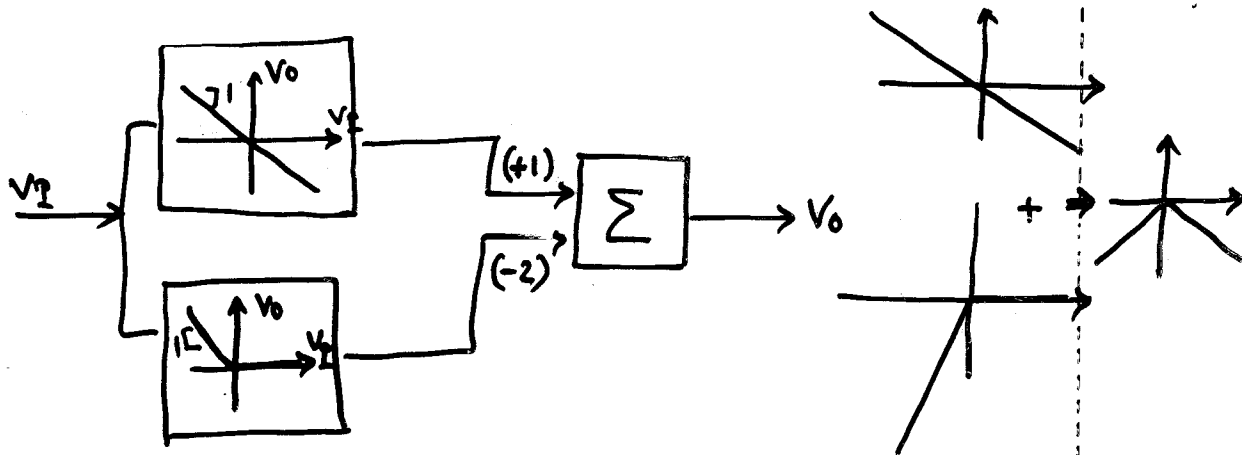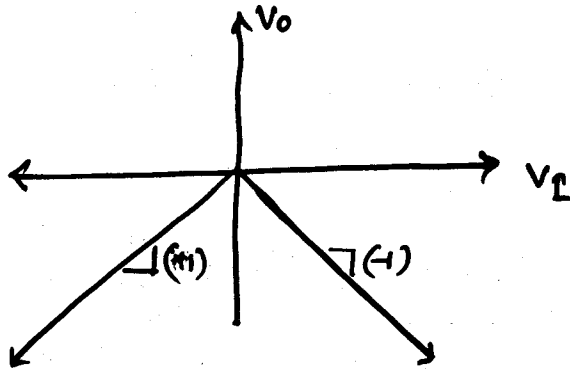


Realization

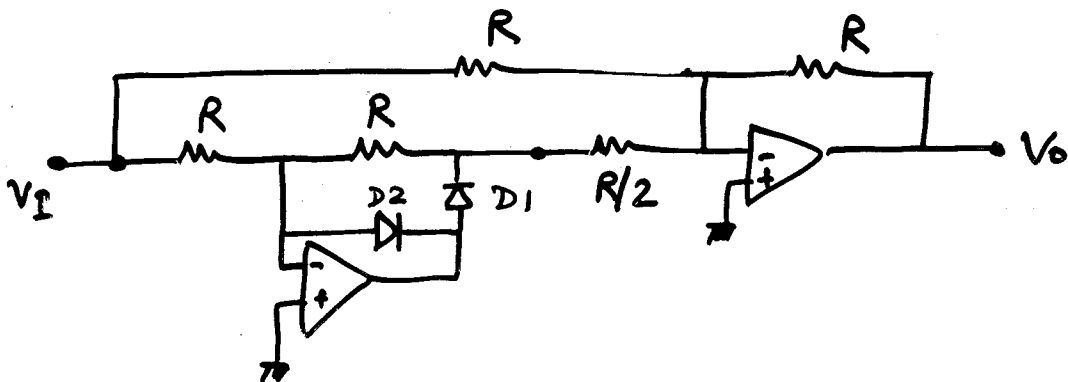


When $v_I < 0$

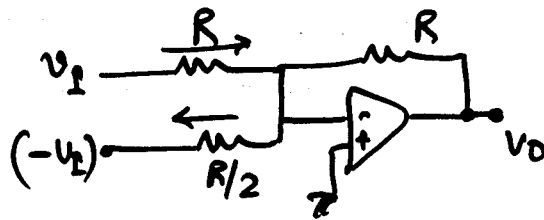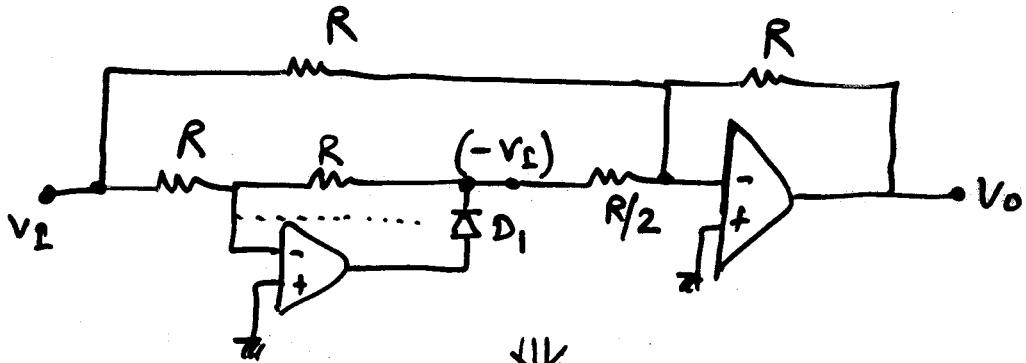


$V_O = (+v_I)$

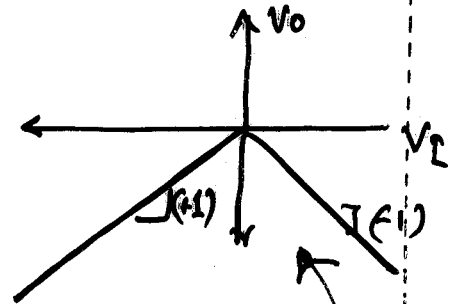

When $v_I > 0$

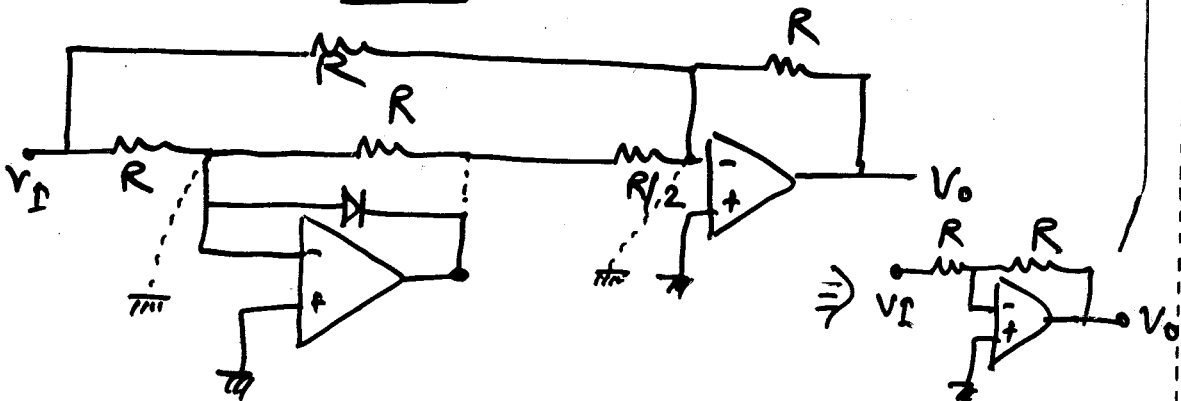

Limiting amplifiers

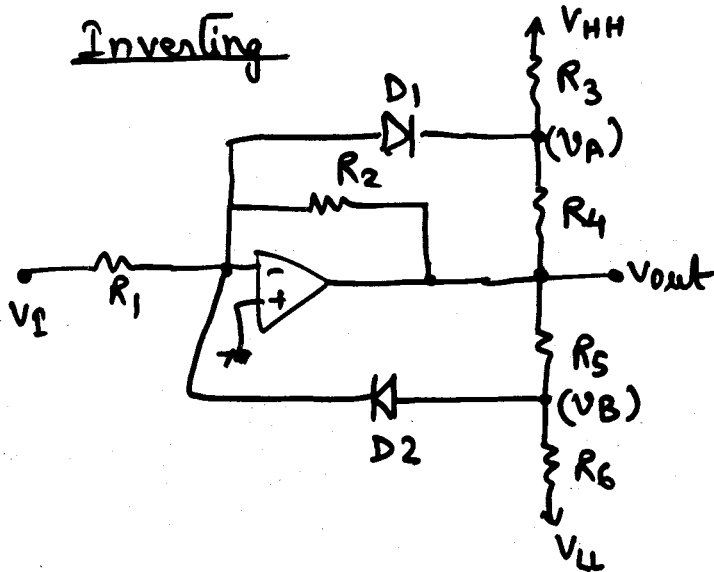

D1	D2	
OFF	OFF	✓
ON	OFF	✓
OFF	ON	✓
ON	ON	x

① D1 and D2 → OFF

$$v_{out} = \left(\frac{-R_2}{R_1} \right) v_I$$

② D1 is on and D2 is off.

↳ $V_A \leq 0$

$$V_A = \left(\frac{R_4}{R_3 + R_4} \right) V_{HH} + \left(\frac{R_3}{R_3 + R_4} \right) v_{out} \leq 0$$

$$v_{out} \leq \left(\frac{-R_4}{R_3} \right) V_{HH}$$

When D1 is on $\Rightarrow v_{out} = \frac{(R_2 || R_4)}{R_1} v_{in} - \frac{(R_2 || R_4)}{R_3} V_{HH}$

When $v_A = 0$ { point when D1 goes off }

$$v_{out} = \left(-\frac{R_2}{R_1}\right) v_i \quad ; \quad v_{out} = \left(-\frac{R_4}{R_3}\right) v_{HH}$$

$$\left(-\frac{R_2}{R_1}\right) v_i = \left(-\frac{R_4}{R_3}\right) v_{HH}$$

↓

$$v_i = \left(\frac{R_1 R_4}{R_2 R_3}\right) v_{HH}$$

