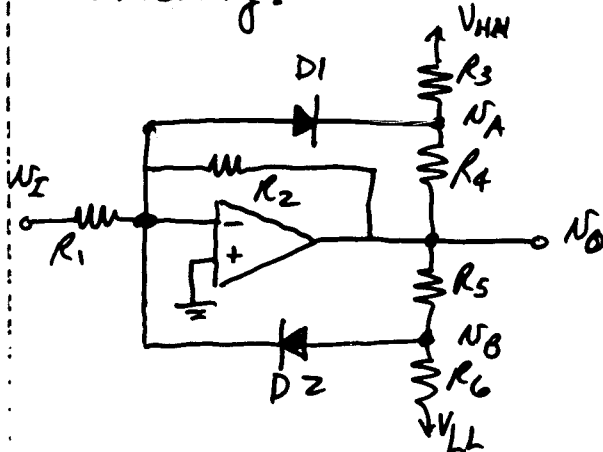


Quiz 13 - Oscillators

Homework 15 due on Friday 12/3/04

Limiting Amplifiers

Inverting:



Diode states:

D1	D2	
OFF	OFF	✓
ON	OFF	✓
OFF	ON	✓
ON	ON	X

1.) D1 and D2 OFF

$$V_O = -\frac{R_2}{R_1} V_I$$


2.) D1 ON and D2 OFF
($N_A \leq 0$)

$$N_A = \left(\frac{R_4}{R_3 + R_4}\right) V_{HH} + \left(\frac{R_3}{R_3 + R_4}\right) V_O$$

D1 goes between ON and OFF when $N_A = 0$

$$\therefore V_{O1} = -\frac{R_4}{R_3} V_{HH} \rightarrow V_{I1} = -\frac{R_1}{R_2} V_{O1} = +\frac{R_1 R_4}{R_2 R_3} V_{HH}$$

When D1 is ON,

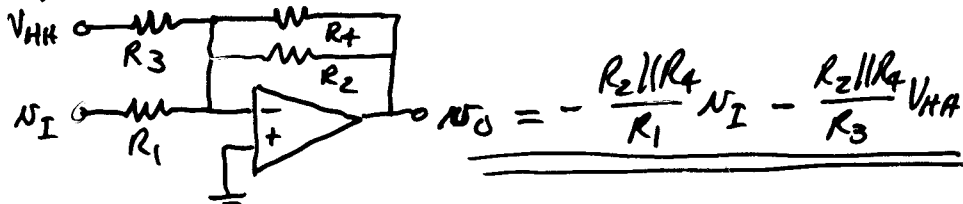

$$V_O = -\frac{R_2 \parallel R_4}{R_1} V_I - \frac{R_2 \parallel R_4}{R_3} V_{HH}$$

Inverting Limiting Amplifier - Cont'd


3) D1 OFF and D2 ON $\Rightarrow N_B \geq 0$

$$N_B = \left(\frac{R_6}{R_5 + R_6}\right) N_O + \left(\frac{R_5}{R_5 + R_6}\right) V_{LL}$$

D2 goes between ON and OFF when $N_B = 0$


$$\therefore V_{O2} = -\frac{R_5}{R_6} V_{LL} \rightarrow \underline{V_{I2} = +\frac{R_1 R_5}{R_2 R_6} V_{LL}}$$

When D1 OFF & D2 ON:



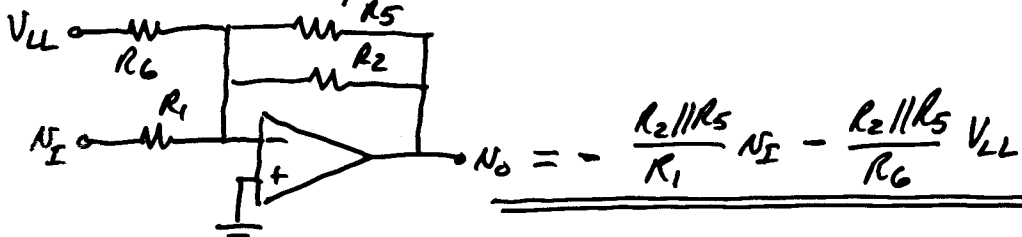


$$N_O = -\frac{R_2 || R_5}{R_1} N_I - \frac{R_2 || R_5}{R_6} V_{LL}$$



Result ($V_{HH} > 0, V_{LL} < 0$):

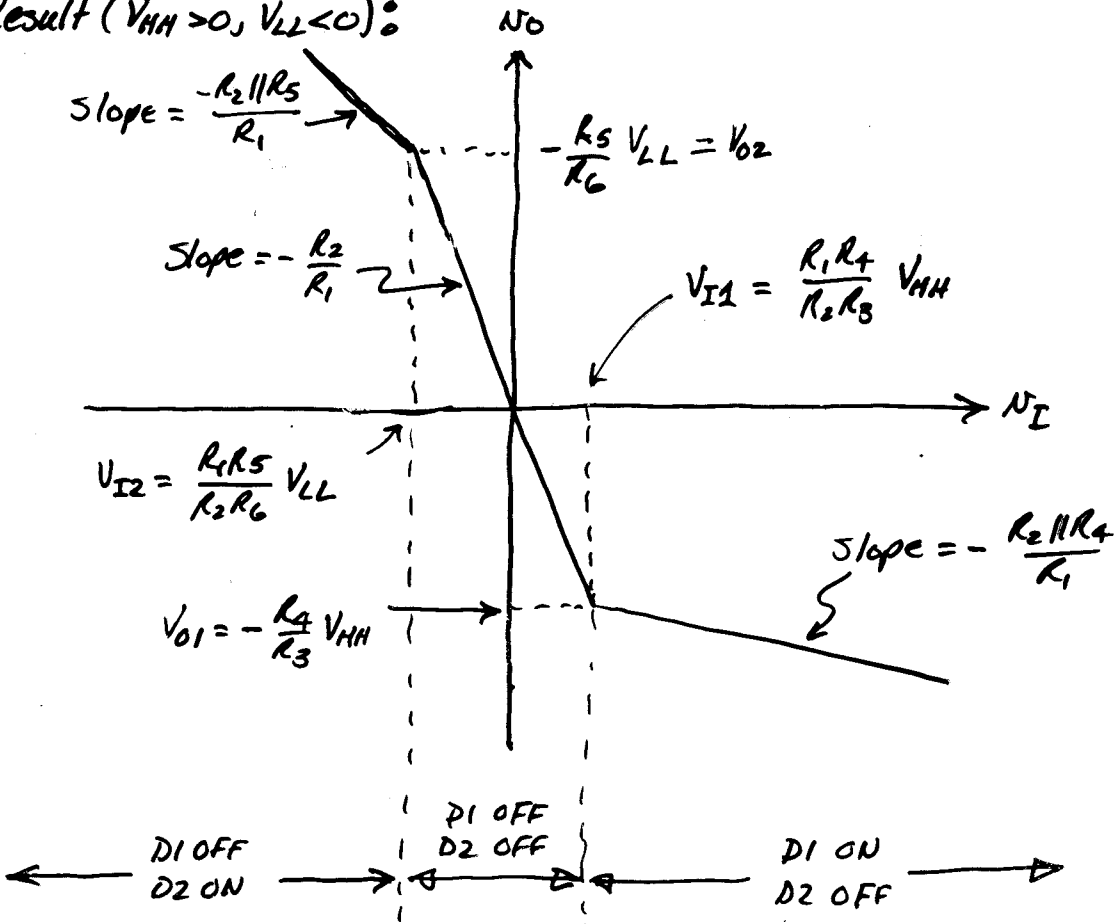



COMPARATORS (1 bit A to D conv.)

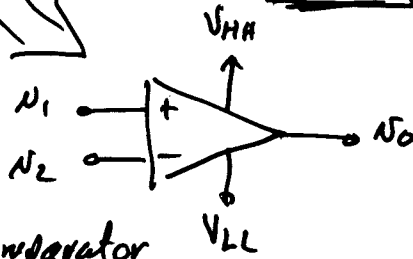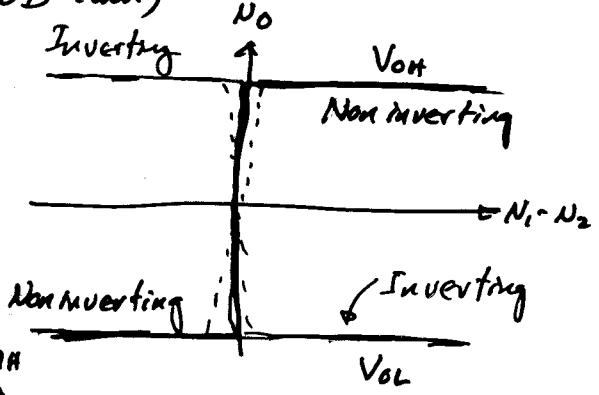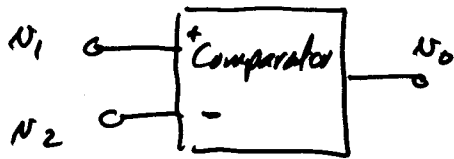

Limiting Comparator

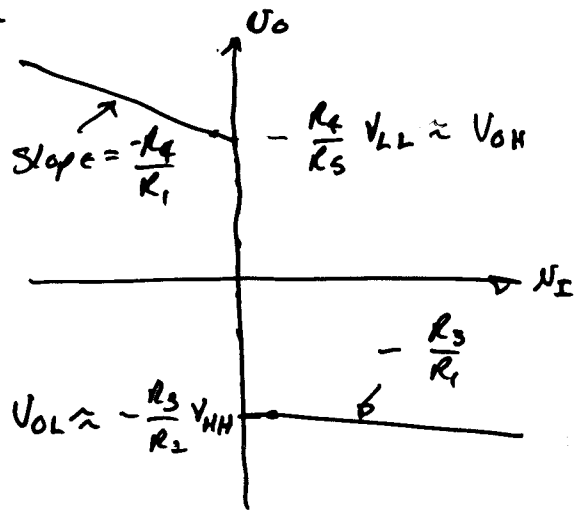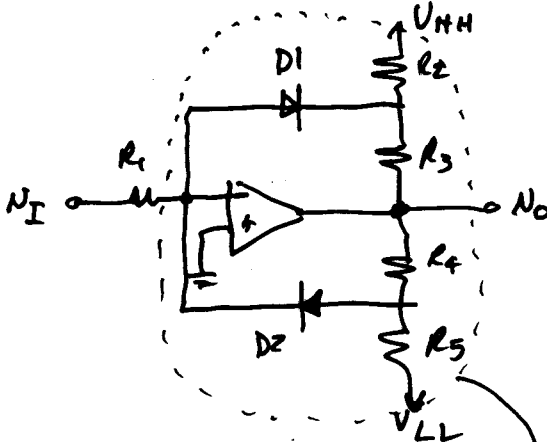


BISTABLE CIRCUITS

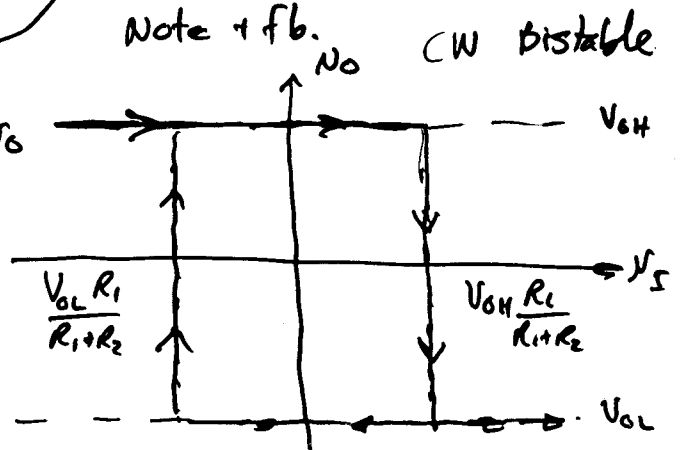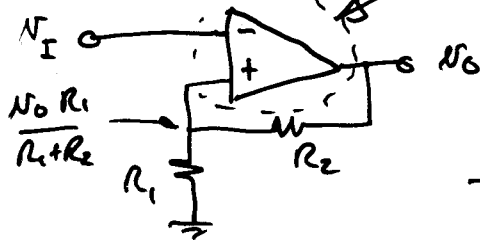


Note + fb.

CCW Bistable.

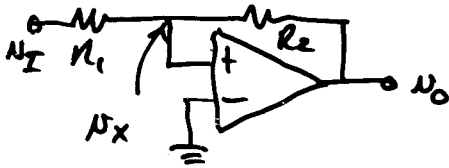
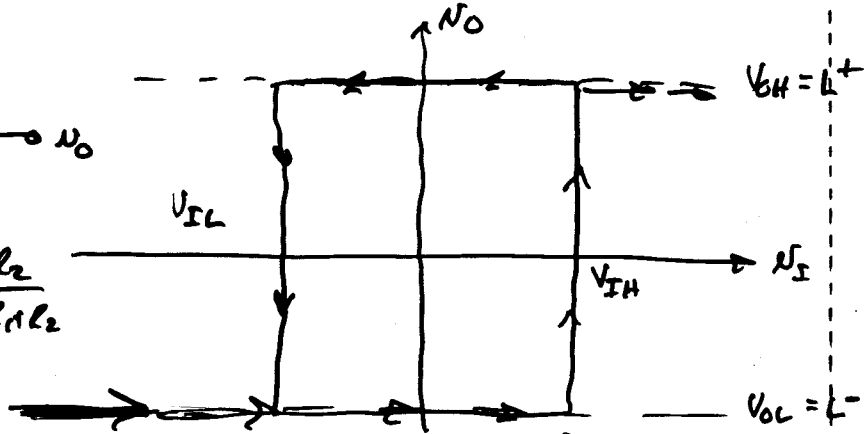
$$N_X = N_O \frac{R_1}{R_1 R_2} + N_I \frac{R_2}{R_1 R_2}$$



$$\frac{V_{IL} R_2}{R_1 R_2} + \frac{V_{OH} R_1}{R_1 R_2} = 0$$


$$0 = \frac{V_{OL} R_1}{R_1 R_2} + \frac{V_{IH} R_2}{R_1 R_2}$$

$$\therefore V_{IH} = -\frac{R_1}{R_2} V_{OL}$$


$$V_{IL} = -\frac{R_1}{R_2} V_{OH}$$

Waveform Generator

1.)

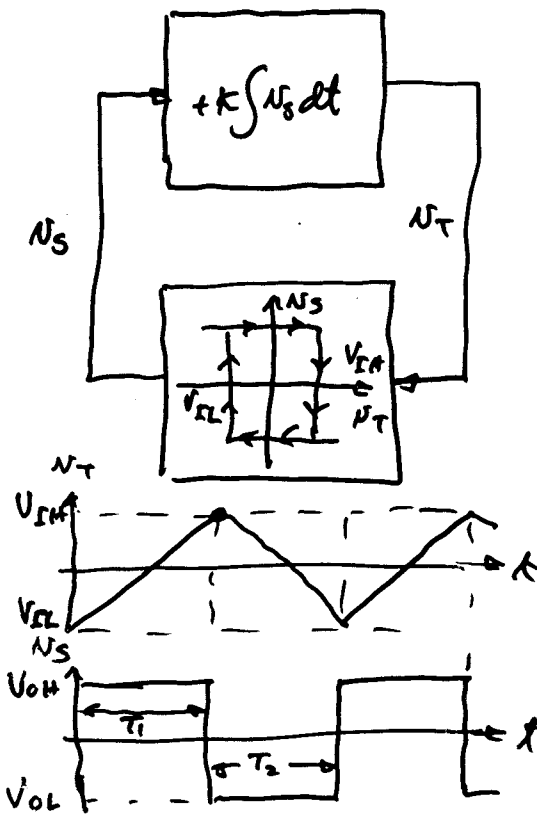

2.)

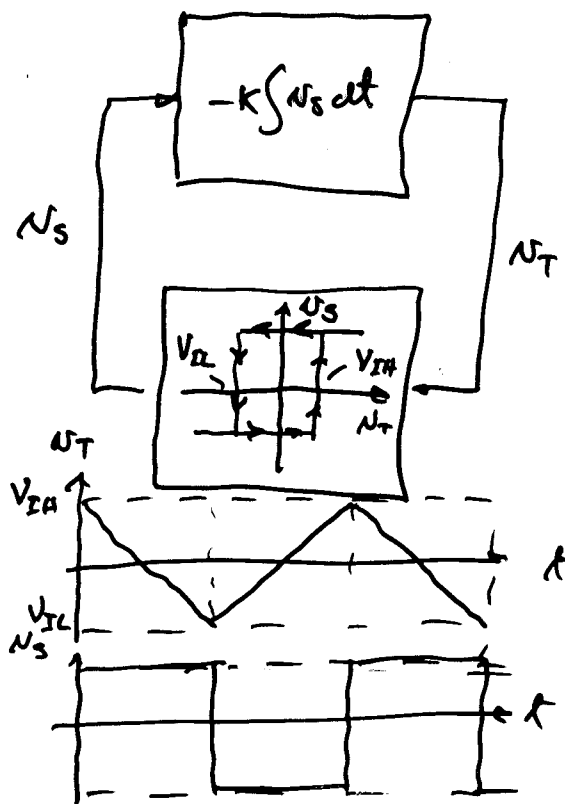

CW Bistable Waveform Generator

$$N_T(T_1) = V_{IL} + K \int_0^{T_1} V_{OH} dt = V_{IH} \rightarrow T_1 = \frac{V_{IH} - V_{IL}}{K V_{OH}}$$


$$N_T(T_2) = V_{IH} + K \int_0^{T_2} V_{OL} dt = V_{IL} \rightarrow T_2 = \frac{V_{IL} - V_{IH}}{K V_{OL}}$$

$$\text{Period} = T = T_1 + T_2 = \frac{V_{IH} - V_{IL}}{K V_{OH}} + \frac{V_{IL} - V_{IH}}{K V_{OL}} = \frac{V_{IH} - V_{IL}}{K} \left[\frac{1}{V_{OH}} + \frac{1}{V_{OL}} \right]$$

If $V_{OL} = -V_{OH}$ and $V_{IL} = -V_{IH}$, then $T = \frac{2 V_{IH}}{K V_{OL}}$

$$f_{osc} = -\frac{K V_{OL}}{4 V_{IH}}$$

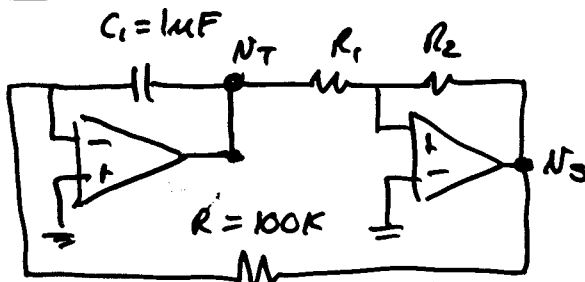Example of CW Bistable Waveform Generator





Let $R_1 = R_2 \Rightarrow V_{IH} = -V_{OL}$



and $V_{IL} = -V_{OH}$

$$K = \frac{1}{RC}$$
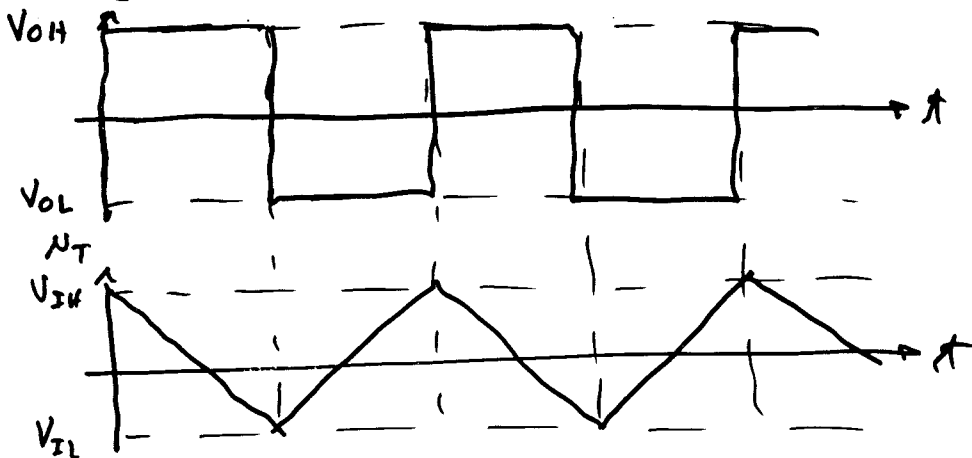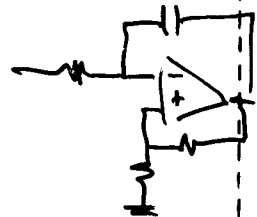
$$f_{osc} = \frac{1}{4RC} = \frac{1}{4 \cdot 100K \cdot 1uF} = \underline{\underline{2500 \text{ Hz}}}$$



Simple Single Op Amp Waveform Generator

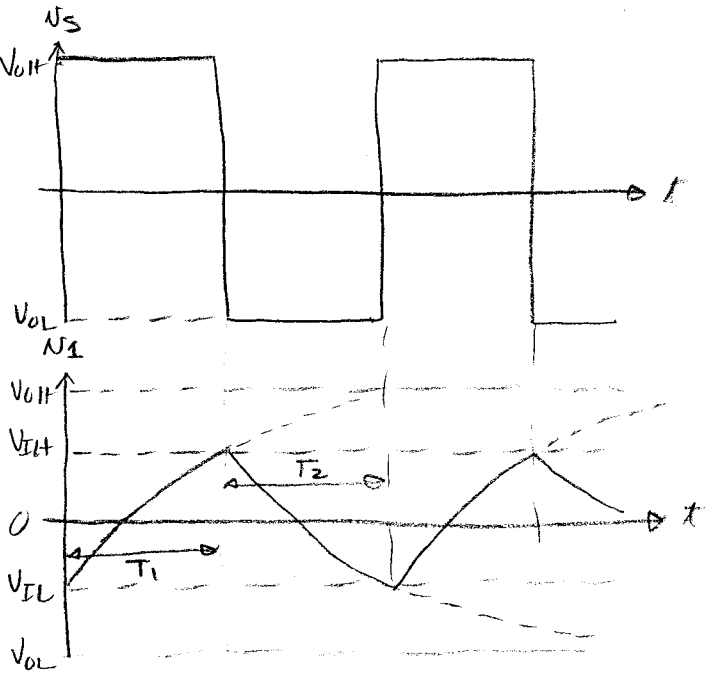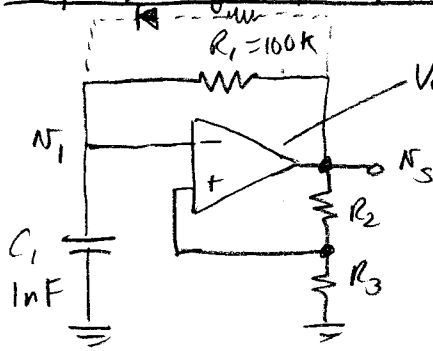

$$V_{IH} = \frac{R_3}{R_2 + R_3} V_{OH}$$

$$V_{IL} = \frac{R_3}{R_2 + R_3} V_{OL}$$

$$R_2 = R_3 \rightarrow V_{IH} = \frac{V_{OH}}{2}$$

$$\text{and } V_{IL} = \frac{V_{OL}}{2}$$

T₁

$$N_1 = A + B e^{-t/\tau}$$

$$\tau = R_1 C_1$$

$$N_1(0) = V_{IL} = A + B$$

$$N_1(\infty) = V_{OH} = A$$

$$\left. \begin{array}{l} N_1(0) = V_{IL} = A + B \\ N_1(\infty) = V_{OH} = A \end{array} \right\} \begin{array}{l} A = V_{OH} \\ B = V_{IL} - A = V_{IL} - V_{OH} \end{array}$$

$$\therefore N_1(x) = V_{OH} + (V_{IL} - V_{OH}) e^{-x/\tau} \rightarrow V_{IH} = V_{OH} + (V_{IL} - V_{OH}) e^{-T_1/\tau}$$

$$e^{-T_1/\tau} = \frac{V_{IH} - V_{OH}}{V_{IL} - V_{OH}} \rightarrow T_1 = \tau \ln \left(\frac{V_{IL} - V_{OH}}{V_{IH} - V_{OH}} \right) = \tau \ln \left(\frac{1 - V_{IL}/V_{OH}}{1 - V_{IH}/V_{OH}} \right)$$

T₂

$$N_1(0) = V_{IH} = A + B \quad N_1(\infty) = V_{OL} = A \rightarrow B = V_{IH} - A = V_{IH} - V_{OL}$$

$$\therefore N_1(x) = V_{OL} + (V_{IH} - V_{OL}) e^{-x/\tau} \rightarrow V_{IL} = V_{OL} + (V_{IH} - V_{OL}) e^{-T_2/\tau}$$

$$T_2 = \tau \ln \left(\frac{V_{IH} - V_{OL}}{V_{IL} - V_{OL}} \right) = \tau \ln \left(\frac{1 - V_{IH}/V_{OL}}{1 - V_{IL}/V_{OL}} \right)$$

$$\therefore T = T_1 + T_2 = \tau \left[\ln \left(\frac{1 - V_{IL}/V_{OH}}{1 - V_{IH}/V_{OH}} \right) + \ln \left(\frac{1 - V_{IH}/V_{OL}}{1 - V_{IL}/V_{OL}} \right) \right]$$

$$\frac{V_{IL}}{V_{OH}} = -\frac{1}{2}, \quad \frac{V_{IH}}{V_{OL}} = -\frac{1}{2}, \quad \frac{V_{IH}}{V_{OH}} = \frac{V_{IL}}{V_{OL}} = \frac{1}{2}$$

$$\therefore T = \tau \left[\ln \left(\frac{3/2}{1/2} \right) + \ln \left(\frac{3/2}{1/2} \right) \right] = 2\tau \ln(3)$$

$$f_{osc} = \frac{1}{T} = \frac{1}{2R_1 C_1 \ln(3)} = \frac{1}{2.197 R_1 C_1} = 4.55 \text{ kHz}$$