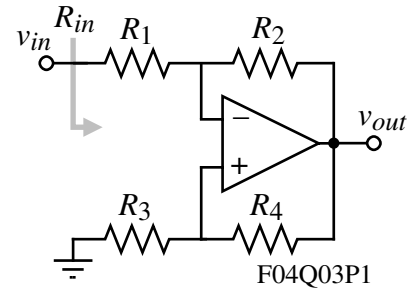


**QUIZ NO. 3 - SOLUTION**

(Average score = 6.8/10 of those taking the quiz)

The voltage amplifier shown uses an ideal op amp.

a.) Find the voltage gain,  $v_{out}/v_{in}$  in terms of the resistors  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$ .b.) Find the input resistance,  $R_{in}$ , in terms of resistors  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$ .c.) If  $R_1 = R_4 = 90\text{k}\Omega$  and  $R_2 = R_3 = 100\text{k}\Omega$  numerically evaluate  $v_{out}/v_{in}$  and  $R_{in}$ .Solution

a.) This problem cannot be worked using the inverting and voltage amplifier configurations so we must use that fact that the input voltage to the op amp is zero.

$$\therefore v_{id} = v^+ - v^- = \frac{v_{out} R_3}{R_3 + R_4} - \left[ \frac{v_{in} R_2}{R_1 + R_2} + \frac{v_{out} R_1}{R_1 + R_2} \right] = 0$$

$$v_{out} \left[ \frac{R_3}{R_3 + R_4} - \frac{R_1}{R_1 + R_2} \right] = \left( \frac{R_2}{R_1 + R_2} \right) v_{in} \quad \rightarrow \quad \frac{v_{out}}{v_{in}} = \frac{\frac{R_2}{R_1 + R_2}}{\frac{R_3}{R_3 + R_4} - \frac{R_1}{R_1 + R_2}}$$


Thus,

$$\frac{v_{out}}{v_{in}} = \frac{R_2}{R_3 \left( \frac{R_1 + R_2}{R_3 + R_4} \right) - R_1} = \frac{R_2 (R_3 + R_4)}{R_2 R_3 - R_1 R_4}$$

b.)  $v_{in} = i_1 R_1 - i_2 R_3$  but  $i_1 R_2 = i_2 R_4$  so we get,

$$v_{in} = i_1 R_1 - R_3 \left( \frac{R_2}{R_4} \right) i_1 = i_1 \left( R_1 - \frac{R_2 R_3}{R_4} \right)$$
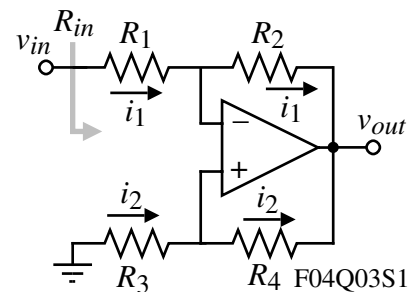
$$\therefore R_{in} = R_1 - \frac{R_2 R_3}{R_4} = \frac{R_1 R_4 - R_2 R_3}{R_4}$$



c.) The numerical values become,

$$\frac{v_{out}}{v_{in}} = \frac{100\text{k}\Omega}{100\text{k}\Omega(1) - 90\text{k}\Omega} = 10\text{V/V} \quad \text{and} \quad R_{in} = 90\text{k}\Omega - \frac{100\text{k}\Omega \cdot 100\text{k}\Omega}{90\text{k}\Omega} = -21.11\text{k}\Omega$$

$$\frac{v_{out}}{v_{in}} = 10 \text{ V/V} \quad \text{and} \quad R_{in} = -21.11\text{k}\Omega$$

Obviously, the voltage source driving this voltage amplifier must have a source resistance greater than  $21.11\text{k}\Omega$  for the circuit to remain stable.