

QUIZ NO. 6

NAME _____ Score _____ /10

A NMOS transistor amplifier is shown.

Assume the parameters of the transistor are

$K_N = 1 \text{ mA/V}^2$, $V_{TN} = 1 \text{ V}$, and $\lambda = 0$. (a.)

Find an algebraic expression for the small signal input resistance, R_{in} , the output

resistance, R_{out} , the voltage gain, v_{out}/v_{in} ,

and the current gain, i_{out}/i_{in} . (c.)

Numerically evaluate the small signal input resistance, R_{in} , the output resistances R_{out} ,

the voltage gain, v_{out}/v_{in} , and the current

gain, i_{out}/i_{in} .

