

## QUIZ NO. 7

NAME \_\_\_\_\_ Score \_\_\_\_\_ /10

Assume that Q1 and Q2 and the resistors  $R_C$  of the differential amplifier shown are matched. If  $\beta_F = 100$ ,  $V_t = 25\text{mV}$ ,  $V_{BEQ} = 0.6\text{V}$ , and  $V_A = \infty$ , find (a.) the numerical value of  $I_{C1}$  and  $I_{C2}$  if  $v_1 = v_2 = 0$ . (b.) For the rest of the problem assume that  $I_{C1} = I_{C2} = 0.5\text{mA}$  and find the numerical value of  $v_{C1}/v_{id}$  where  $v_{id} = v_1 - v_2$ . (c.) Find the numerical value of  $v_{C1}/v_{ic}$  where  $v_{ic} = v_1 = v_2$ . (d.) Find the numerical value of the differential input resistance defined as,

$$R_{id} = v_{id}/i_{in}.$$

