



QUIZ NO. 8 - SOLUTION

(Average score = 7.5/10 of those taking the quiz.)

r_{π} and β of the BJT shown are $1k\Omega$ and 100, respectively. Find the numerical value of all zeros, poles, and the midband gain for the voltage transfer function, $V_{out}(s)/V_{in}(s)$. What is the lower -3dB frequency?

Solution

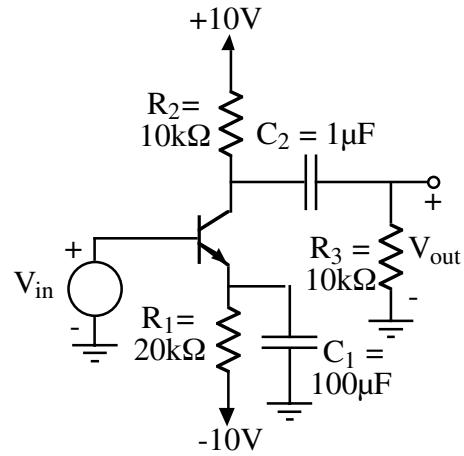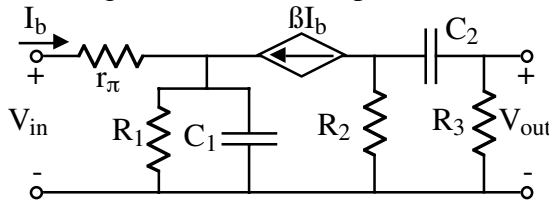The small signal model for this problem is:



$$\frac{V_{out}}{V_{in}} = \left(\frac{V_{out}}{I_b}\right)\left(\frac{I_b}{V_{in}}\right) = \left(\frac{-\beta R_2 R_3}{R_2 + R_3 + \frac{1}{sC_2}}\right) \left(\frac{1}{r_{\pi} + (1 + \beta) \left(\frac{R/sC_1}{R_1 + \frac{1}{sC_1}}\right)}\right)$$

$$= \left(\frac{-\beta R_2 R_3}{r_{\pi}(R_2 + R_3)}\right) \left(\frac{s}{s + \frac{1}{C_2(R_2 + R_3)}}\right) \left(\frac{s + \frac{1}{R_1 C_1}}{s + \frac{1}{r_{\pi} R_1 C_1}}\right) = A_o \left(\frac{s}{s + \omega_2}\right) \left(\frac{s + \omega_1'}{s + \omega_1}\right)$$

where

$$A_o = \frac{-\beta \cdot R_2 \parallel R_3}{r_{\pi}} = \frac{-100 \cdot 5k\Omega}{1k\Omega} = -500V/V$$

$$\omega_1 = \frac{1}{R_1 C_1} = \frac{1}{20k\Omega \cdot 100\mu F} = 0.5 \text{ rads/sec}$$

$$\omega_1' = \omega_1 \left(1 + \frac{(1 + \beta) R_1}{r_{\pi}}\right) = 0.5 \left(1 + \frac{101 \cdot 20}{1}\right) = 1010 \text{ rads/sec}$$

and

$$\omega_2 = \frac{1}{C_2(R_2 + R_3)} = \frac{1}{20k\Omega \cdot 1\mu F} = 50 \text{ rads/sec}$$

Therefore,

$$\text{Zeros at } s=0 \text{ and } s=-0.5 \text{ rad/sec}$$

$$\text{poles at } s = -50 \text{ rads/sec and } s = -1010 \text{ rads/sec}$$

$$\text{Midband gain} = A_o = -500V/V$$

The lower -3dB frequency is

$$\omega_L = \sqrt{50^2 + 1010^2} - 2(0.5^2) = 1018 \text{ rads/sec or } f_L = 161 \text{ Hz}$$