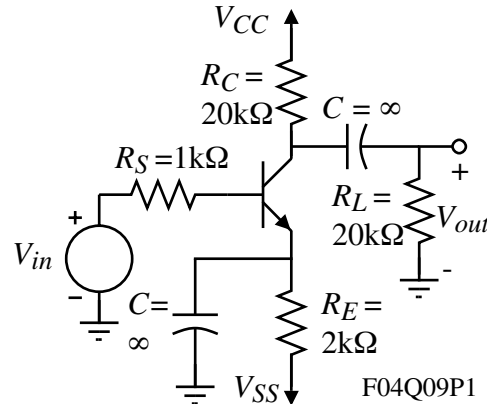


QUIZ NO. 9 - SOLUTION

(Average score = 8.6/10 of those taking the quiz)


Assume that the small-signal parameters of the BJT amplifier shown are $g_m = 10\text{mS}$, $r_\pi = 1\text{k}\Omega$, $r_x = 0$, $r_o = \infty$, $C_\pi = 10\text{pF}$, and $C_\mu = 1\text{pF}$.

- a.) Find the midband voltage gain of this amplifier, V_{out}/V_{in} .
- b.) Find the value of the upper -3dB frequency, f_H , in Hz, first using the Miller approximation and secondly using the open-circuit time constant approach.
- c.) Which of the two answers for f_H in part b.) is the most accurate and why?



Solution

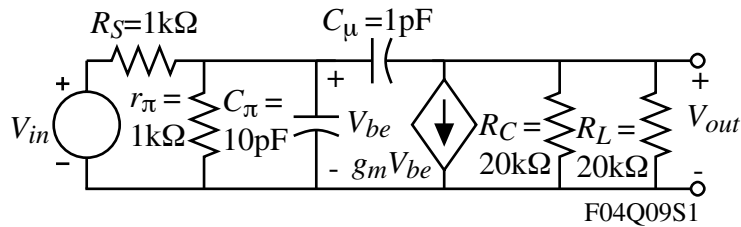a.) The small-signal model for all three parts of this problem is shown.



The MBG is,

$$\frac{V_{out}(0)}{V_{in}(0)} = -g_m(R_C \parallel R_L) \left(\frac{r_\pi}{r_\pi + R_S} \right) = \underline{\underline{-50 \text{ V/V}}}$$

b.) The Miller approximation gives the following capacitance between gate and source.

$$C_{eq} = C_\pi + [1 - g_m(R_C \parallel R_L)] C_\mu = 10\text{pF} + (1 + 100)1\text{pF} = 111\text{pF}$$


$$\therefore \omega_H = \frac{1}{(R_S \parallel r_\pi) C_{eq}} = \frac{1}{0.5\text{K} \cdot 111\text{pF}} = 18.02 \text{ Mrads/sec.} \rightarrow f_H = \frac{18.02 \times 10^6}{2\pi} = \underline{\underline{2.87\text{MHz}}}$$

The OCTC approach requires finding $R_{c\pi O}$ and $R_{c\mu O}$.

These are found as,

$$R_{c\pi O} = R_i = 500\Omega$$

$$R_{c\mu O} = ?$$

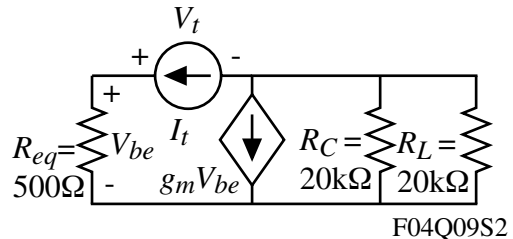

$$V_t = V_{be} + (I_t + g_m V_{be}) 10\text{k}\Omega = I_t R_{eq} + (I_t + g_m I_t R_{eq}) 10\text{k}\Omega$$

$$\therefore R_{c\mu O} = \frac{V_t}{I_t} = R_{eq} + (1 + g_m R_{eq}) 10\text{k}\Omega = 500\Omega + (1 + 5) 10\text{k}\Omega = 60.5\text{k}\Omega$$

$$\therefore \omega_H = \frac{1}{R_{c\pi O} C_\pi + R_{c\mu O} C_\mu} = \frac{1}{500 \cdot 10\text{pF} + 60.5\text{K} \cdot 1\text{pF}} = 15.27 \times 10^6 \text{ rads/sec.}$$

Thus, $f_H = \frac{15.27 \times 10^6}{2\pi} = \underline{\underline{2.43\text{MHz}}}$ However, since the RC products are poles we can solve for the poles as $(1/R_{c\pi O} C_\pi)^{-1} = 200 \text{ Mrads/sec}$ and $(1/R_{c\mu O} C_\mu)^{-1} = 16.53 \text{ Mrads/sec}$. The dominant pole is -16.53 Mrads/sec which give $f_H = \underline{\underline{2.63\text{MHz}}}$

c.) The answer given by the OCTC method is probably more correct because the impedance of C_μ at ω_H for the Miller approach turns out to be $(1/18.02 \times 10^6 \cdot 10^{-12}) = 55.5\text{k}\Omega$ which is not all that much greater than $R_L \parallel R_C = 10\text{k}\Omega$.