

QUIZ NO. 9

NAME _____ Score _____ /10

Assume that the small-signal parameters of the BJT amplifier shown are $g_m = 10\text{mS}$, $r_\pi = 1\text{k}\Omega$, $r_x = 0$, $r_o = \infty$, $C_\pi = 10\text{pF}$, and $C_\mu = 1\text{pF}$.

- Find the midband voltage gain of this amplifier, V_{out}/V_{in} .
- Find the value of the upper -3dB frequency, f_H , in Hz, first using the Miller approximation and secondly using the open-circuit time constant approach.
- Which of the two answers for f_H in part b.) is the most accurate and why?

