

QUIZ NO. 11


(Average Score = 5.5/10 for those taking this quiz.)

The simplified schematic of a feedback amplifier is shown. Assume that all transistors are matched and $g_m = 1\text{mA/V}$ and $r_{ds} = \infty$. Use the method of feedback analysis to find v_2/v_1 , $R_{in} = v_1/i_1$, and $R_{out} = v_2/i_2$.


Solution

This feedback circuit is series-series. The units of A are A/V and the units of β are V/A .

$$F = z_{12f} = \frac{v_{1f}}{i_{2f}} \Big|_{v_2=0} = R_3 = 1\text{k}\Omega$$

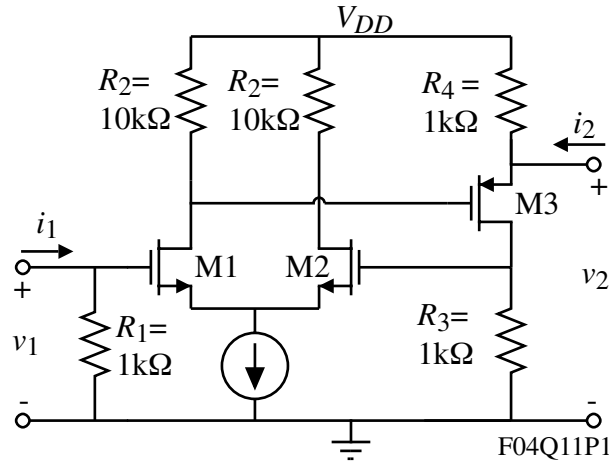

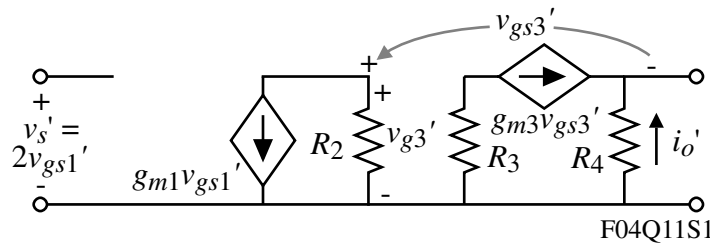The circuit for calculating the small-signal open-loop gain is,



$$A = \frac{i_o'}{v_s'} = \left(\frac{i_o'}{v_{gs3}'} \right) \left(\frac{v_{gs3}'}{v_{gs1}'} \right) \left(\frac{v_{gs1}'}{v_s'} \right) = (-g_{m3}) \left(\frac{1}{1+g_{m3}R_4} \right) (-g_{m1}R_2) \left(\frac{1}{2} \right)$$

$$A = \frac{i_o'}{v_s'} = (1\text{mS})(0.5)(5) = 2.5\text{mS} \rightarrow A_F = \frac{i_o}{v_s} = \frac{A}{1+AF} = \frac{2.5\text{mS}}{1+2.5 \cdot 1} = 0.714 \text{ mS}$$

$$\frac{v_2}{v_1} = \frac{v_2}{v_s} = \left(\frac{v_2}{i_o} \right) \left(\frac{i_o}{v_s} \right) = -R_4(0.714\text{mS}) = -0.714 \text{ V/V} \quad \boxed{\frac{v_2}{v_s} = -0.714 \text{ V/V}}$$

R_1 is not influenced by feedback* so $\boxed{\frac{v_1}{i_1} = R_1 = 1\text{k}\Omega}$

$$R_o = R_4 + (1/g_{m3}) = 1\text{k}\Omega + 1\text{k}\Omega = 2\text{k}\Omega \rightarrow R_{oF} = 2\text{k}\Omega(1+2.5) = 7\text{k}\Omega$$

$$R_{out} = \frac{v_2}{i_2} = (R_{oF} \parallel R_4) \parallel R_4 = 6\text{k}\Omega \parallel 1\text{k}\Omega = 857\Omega \quad \boxed{\frac{v_2}{i_2} = 875\Omega}$$

* The reason for this is that the input variable is v_s and the resistor, R_1 , in parallel with v_s does not influence the circuit so the input resistance without feedback is ∞ .