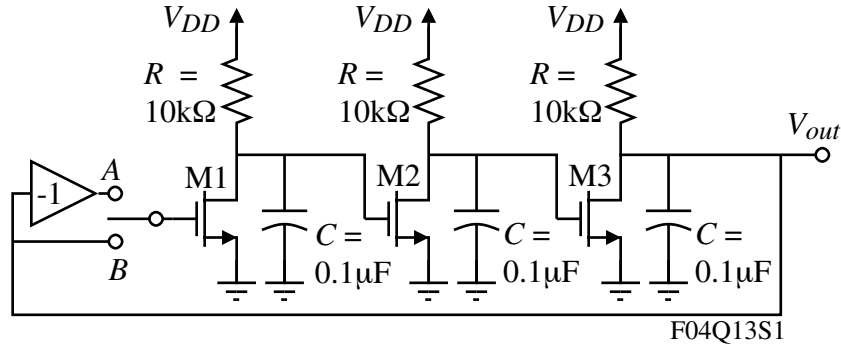


QUIZ NO. 13

(Average score = 7.0/10 of those taking the quiz)

The circuit shown is to be an oscillator. The transistors are identical with $r_{ds} = \infty$. (a.) Should the switch at the gate of M1 be connected to point A or B in order to oscillate? (b.) Find the frequency of oscillation in Hertz and the value of g_m necessary for oscillation.

Solution

(a.) We see that the gain of each amplifier can be written as

$$\frac{-g_m R}{sRC + 1}$$

and has a phase shift of $180^\circ - \tan^{-1}(\omega RC)$. This phase shift per amplifier varies from 180° to 90° . Three amplifiers cascaded give a phase shift of $540^\circ - 3\tan^{-1}(\omega RC)$ or $180^\circ - 3\tan^{-1}(\omega RC)$. If the switch is at A, the total loop phase shift would be $720^\circ - 3\tan^{-1}(\omega RC)$ or $3\tan^{-1}(\omega RC)$ and it would be impossible to get a loop phase shift of 360° . Therefore, the switch must be connected to B. (If you can't follow this, you could just pick a position and see if the equations for oscillation can be satisfied or not.)

(b.) With the switch is connected to B, the gain from the gate of M1 to V_{out} can be expressed as,

$$\frac{V_{out}}{V_{g1}} = T(s) = \left(\frac{-g_m R}{sRC + 1} \right)^3 = \frac{(-g_m R)^3}{(sRC)^3 + 3s^2 R^2 C^2 + 3sRC + 1}$$

$$T(j\omega) = \frac{-(g_m R)^3}{[1 - 3\omega^2 R^2 C^2] + j\omega RC [3 - \omega^2 R^2 C^2]} = 1 + j0$$

$$\omega_{osc} = \frac{\sqrt{3}}{RC} = \frac{1.732}{10 \times 10^3 \cdot 1 \times 10^{-7}} = 1.732 \text{ Krad/sec} \quad \rightarrow \quad \underline{f_{osc} = 275.7 \text{ Hz}}$$

Also, from the above equation, we get

$$-(g_m R)^3 = 1 - 3\omega^2 R^2 C^2 = 1 - 9 = -8$$

$$\therefore (g_m R)^3 = 8 \quad \rightarrow \quad g_m R = 8^{0.33} = 2 \quad \rightarrow \quad g_m = \frac{2}{10 \text{ K}\Omega} = \underline{200 \mu\text{S}}$$