

QUIZ NO. 13

NAME _____ Score _____ /10

The circuit shown is to be an oscillator. The transistors are identical with $r_{ds} = \infty$. (a.) Should the switch at the gate of M1 be connected to point A or B in order to oscillate? (b.) Find the frequency of oscillation in Hertz and the value of g_m necessary for oscillation.

