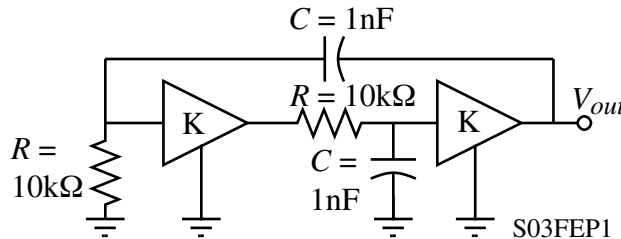


FINAL EXAMINATION – SOLUTION

(Average Score = 78/100)

Problem 1 - (20 points - This problem must be attempted)


The circuit shown is a RC oscillator. Find the frequency of oscillation in Hertz and the voltage gain, K , of the voltage amplifiers necessary for oscillation. The voltage amplifiers have infinite input resistance and zero output resistance.

**Solution**

The loop gain can be found from the schematic shown:

$$T(s) = \frac{V_r}{V_x} = K^2 \left(\frac{1}{sRC+1} \right) \left(\frac{sRC}{sRC+1} \right)$$
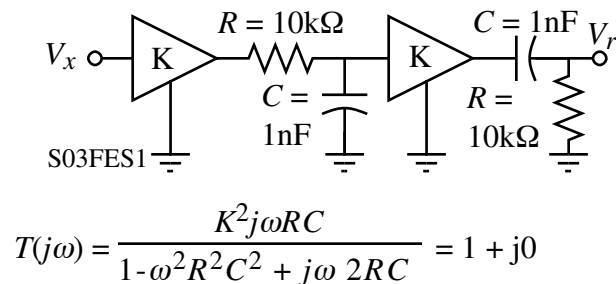
$$= \frac{K^2 sRC}{s^2 R^2 C^2 + 2sRC + 1} \quad \rightarrow$$



$$T(j\omega) = \frac{K^2 j\omega RC}{1 - \omega^2 R^2 C^2 + j\omega 2RC} = 1 + j0$$

We see from this equation that for oscillation to occur, the following conditions must be satisfied:

$$1 - \omega^2 R^2 C^2 = 0 \quad \text{and} \quad K^2 = 2$$

or


$$\omega_{osc} = \frac{1}{RC} = \frac{1}{10^4 \cdot 10^{-9}} = 10^5 \text{ radians/sec.} \quad \rightarrow \quad f_{osc} = \underline{\underline{15.9\text{kHz}}}$$

and

$$K = \sqrt{2} = \underline{\underline{1.414}}$$

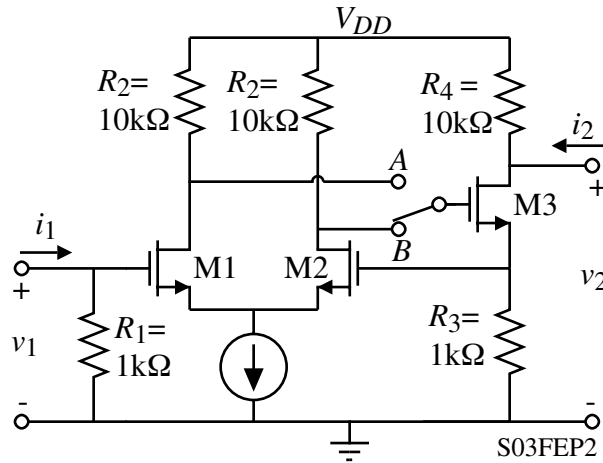Problem 2 – (20 points – This problem must be attempted)

The simplified schematic of a feedback amplifier is shown. Assume that all transistors are matched and $g_m = 1\text{mA/V}$ and $r_{ds} = \infty$. (a.) Where should the switch be connected for negative feedback? (b.) Use the method of feedback analysis to find v_2/v_1 , $R_{in} = v_1/i_1$, and $R_{out} = v_2/i_2$.




Solution

(a.) A quick check of the ac voltage changes around the loop show that the switch should be connected to B.

(b.) This feedback circuit is series-series. The units of A are A/V and the units of β are V/A .

$$\beta = z_{12f} = \frac{v_{1f}}{i_{2f}} \Big|_{i_{1f}=0} = R_3 = 1\text{k}\Omega$$

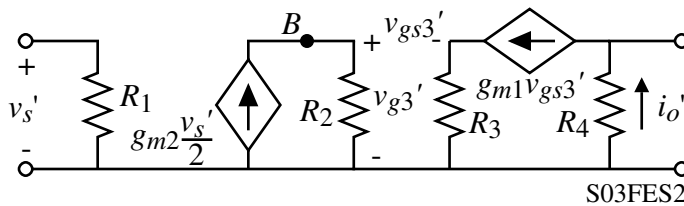The circuit for calculating the small-signal open-loop gain is,



$$A = \frac{i_o'}{v_s'} = \left(\frac{i_o'}{v_{gs3'}} \right) \left(\frac{v_{gs3'}}{v_{gs'}} \right) \left(\frac{v_{gs'}}{v_s'} \right) = (g_{m3}) \left(\frac{1}{1+g_{m3}R_3} \right) \left(\frac{g_{m2}R_2}{2} \right)$$

$$A = \frac{i_o'}{v_s'} = (1\text{mS})(0.5)(5)(2) = 2.5\text{mS} \rightarrow A_F = \frac{i_o}{v_s} = \frac{A}{1+A\beta} = \frac{2.5\text{mS}}{1+2.5 \cdot 1} = 0.714 \text{ mS}$$

$$\frac{v_2}{v_1} = \frac{v_2}{v_s} = \left(\frac{v_2}{i_o} \right) \left(\frac{i_o}{v_s} \right) = -R_4(0.714\text{mS}) = -7.14 \text{ V/V}$$

$$\frac{v_2}{v_s} = -7.14 \text{ V/V}$$

R_1 is not influenced by feedback so $\frac{v_1}{i_1} = R_1 = 1\text{k}\Omega$

$$R_o = R_4 + \infty = \infty \rightarrow R_{oF} = \infty(1+2.5) = \infty$$

$$R_{out} = \frac{v_2}{i_2} = (R_{oF} \parallel R_4) \parallel R_4 = \infty \parallel 10\text{k}\Omega = 10\text{k}\Omega$$

$$\frac{v_2}{i_2} = R_4 = 10\text{k}\Omega$$


Problem 3 - (20 points - This problem is optional)

An inverting and noninverting unity gain voltage amplifier are shown using op amps. If the differential voltage gain of each op amp is given as


$$A_{vd}(s) = \frac{10^4}{\frac{s}{100} + 1}$$

find the closed loop -3dB bandwidth, $\omega_{-3\text{dB}}$ for each of the two op amp configurations.

Assume the op amps have infinite differential input resistance and zero output resistance.

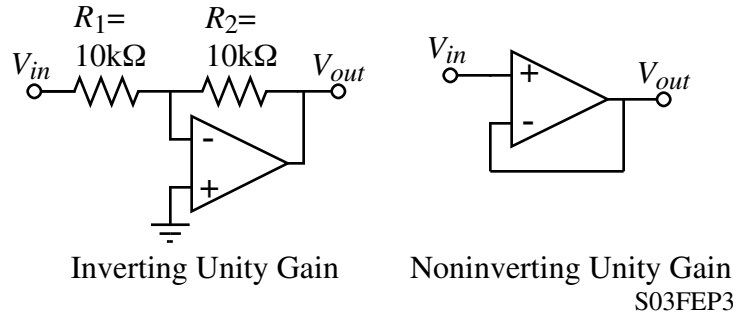Solution

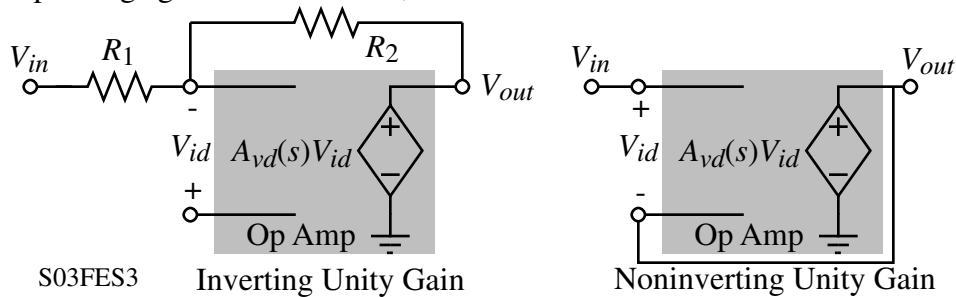The best approach is to replace the op amp with its small-signal model and calculate the closed loop voltage gain. The model is,



Inverting unity gain amplifier:

$$V_{out} = -A_{vd}(s)V_{id} = -A_{vd}(s)\left(\frac{R_2}{R_1+R_2}V_{in} + \frac{R_1}{R_1+R_2}V_{out}\right) = -\frac{A_{vd}(s)R_2}{R_1+R_2}V_{in} - \frac{A_{vd}(s)R_1}{R_1+R_2}V_{out}$$

$$V_{out}\left(1 + \frac{A_{vd}(s)R_1}{R_1+R_2}\right) = -\frac{A_{vd}(s)R_2}{R_1+R_2}V_{in} \rightarrow \frac{V_{out}}{V_{in}} = -\frac{\frac{A_{vd}(s)R_2}{R_1+R_2}}{1 + \frac{A_{vd}(s)R_1}{R_1+R_2}} = -\frac{\frac{A_{vd}(s)}{2}}{1 + \frac{A_{vd}(s)}{2}}V_{in}$$

$$\frac{V_{out}}{V_{in}} = -\frac{0.5}{\frac{1}{A_{vd}(s)} + 0.5} = -\frac{0.5 \times 10^4}{\frac{s}{100} + 1 + 0.5 \times 10^4} \approx \frac{0.5 \times 10^6}{s + 0.5 \times 10^6} \rightarrow \omega_{-3\text{dB}} = \underline{\underline{0.5 \times 10^6 \text{ radians/sec.}}}$$


For the noninverting unity gain amplifier, $R_1 = \infty$ and $R_2 = 0$ to give,

$$V_{out} = A_{vd}(s)V_{id} = A_{vd}(s)(V_{in} - V_{out}) \rightarrow \frac{V_{out}}{V_{in}} = \frac{A_{vd}(s)}{1 + A_{vd}(s)} = \frac{10^4}{\frac{s}{100} + 1 + 10^4} \approx \frac{10^6}{s + 10^6}$$


$$\therefore \omega_{-3\text{dB}} = \underline{\underline{10^6 \text{ radians/sec.}}}$$

Problem 4 - (20 points - This problem is optional)

- 1.) If $g_m = 1\text{mA/V}$, what is the midband voltage gain of the amplifier shown? Assume $r_d = \infty$.
- 2.) Find all poles and zeros of this amplifier in radians/sec.

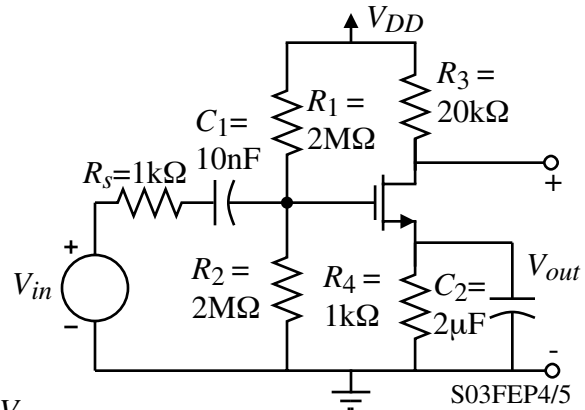Solution

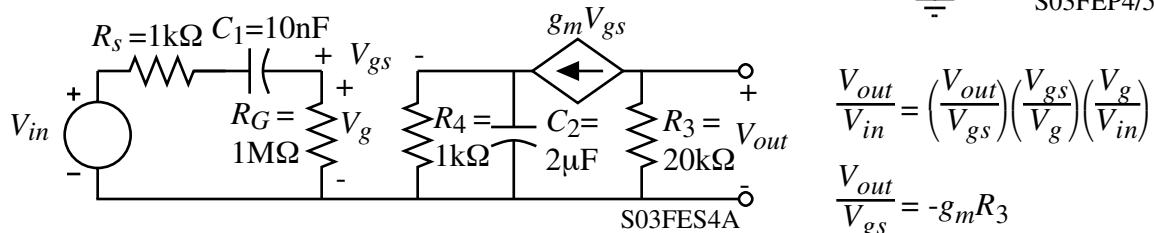The small-signal model for this problem is,



$$\frac{V_{out}}{V_{in}} = \left(\frac{V_{out}}{V_{gs}}\right) \left(\frac{V_{gs}}{V_g}\right) \left(\frac{V_g}{V_{in}}\right)$$

$$\frac{V_{out}}{V_{gs}} = -g_m R_3$$

$$V_{gs} = V_g - V_s = V_g - g_m R_4 \parallel (1/s C_2) V_{gs} \rightarrow V_{gs} \left(1 + \frac{g_m R_4}{s R_4 C_2 + 1}\right) = V_g$$

$$\frac{V_{gs}}{V_g} = \frac{s R_4 C_2 + 1}{s R_4 C_2 + 1 + g_m R_4} = \frac{s + \frac{1}{R_4 C_2}}{s + \frac{1 + g_m R_4}{R_4 C_2}} \frac{V_g}{V_{in}} = \frac{R_G}{R_G + R_S + \frac{1}{s C_1}} = \left(\frac{R_G}{R_G + R_S}\right) \frac{s}{s + \frac{1}{C_1 (R_G + R_S)}}$$

$$\therefore \frac{V_{out}}{V_{in}} = (-g_m R_3) \left(\frac{s + \frac{1}{R_4 C_2}}{s + \frac{1 + g_m R_4}{R_4 C_2}}\right) \left[\left(\frac{R_G}{R_G + R_S}\right) \frac{s}{s + \frac{1}{C_1 (R_G + R_S)}}\right]$$

$$\text{MBG} = \frac{-g_m R_3 R_G}{R_G + R_S} = \frac{-1\text{mS} \cdot 20\text{k}\Omega \cdot 1\text{M}\Omega}{1\text{M}\Omega + 1\text{k}\Omega} = \underline{\underline{-19.98\text{V/V}}}$$

$$\text{Zeros at } \underline{s = 0} \text{ and } s = -\frac{1}{R_4 C_2} = \frac{-1}{10^3 \cdot 2 \times 10^{-6}} = \underline{\underline{-500 \text{ radians/sec.}}}$$

$$\text{Poles at } s = -\frac{1 + g_m R_4}{R_4 C_2} = \frac{-2}{10^3 \cdot 2 \times 10^{-6}} = \underline{\underline{-1000 \text{ radians/sec}}}$$

and

$$s = -\frac{1}{C_1 (R_G + R_S)} = \frac{-1}{10^{-8} \cdot 1.001 \times 10^6} = \underline{\underline{-99.9 \text{ radians/sec.}}}$$

Problem 5 - (20 points - This problem is optional)

The FET in the amplifier shown has $g_m = 1\text{mA/V}$, $r_d = \infty$, $C_{gd} = 0.5\text{pF}$, and $C_{gs} = 10\text{pF}$. (a.) Find the midband gain, V_{out}/V_{in} . (b.) Find the upper -3dB frequency, f_H , in Hz.

Solution

The high-frequency, small-signal model for this problem is shown below.

The MBG can be found as,

$$\begin{aligned} \text{MBG} &= (-g_m R_3) \left(\frac{R_G}{R_s + R_G} \right) \\ &= (-20) \left(\frac{1\text{M}\Omega}{1\text{k}\Omega + 1\text{M}\Omega} \right) = \underline{\underline{-19.98 \text{ V/V}}} \end{aligned}$$

The two approaches to working this problem are the OTC and Miller. Let us choose Miller since it is simpler and more direct.

$$C_{total} = C_{gs} + C_{gd}(1+20) = 10\text{pf} + 0.5\text{pf}(21) = 20.5\text{pF}$$

The resistance seen by C_{total} is $R_s \parallel R_G = 1\text{k}\Omega \parallel 1\text{M}\Omega = 0.999\text{k}\Omega$

$$\therefore \omega_{-3\text{dB}} = \frac{1}{999 \times 20.5 \times 10^{-12}} = 48.829 \text{ Mradians/sec.} \rightarrow f_{-3\text{dB}} = \underline{\underline{7.77\text{MHz}}}$$

Check to see if the Miller approach is valid.

$$\frac{1}{\omega_{-3\text{dB}} C_{gd}} = \frac{1}{(48.829 \times 10^6)(0.5\text{pF})} = 40.96\text{k}\Omega \text{ which is twice } R_3$$

We probably should try the OTC approach to see how it compares-

$$R_{C_{gs}} \approx 1\text{k}\Omega \rightarrow \omega_{C_{gs}} = \frac{1}{C_{gs} \cdot 1\text{k}\Omega} = 100 \text{ Mrads/sec.}$$



and

$$R_{C_{gd}} \approx R_s + (1+g_m R_s)R_3 = 1\text{k}\Omega + 2(20\text{k}\Omega) = 41\text{k}\Omega$$

$$\omega_{C_{gd}} = \frac{1}{C_{gd} \cdot 41\text{k}\Omega} = 48.78 \text{ Mrads/sec.}$$

$$\therefore \omega_H \approx \frac{1}{\frac{1}{100\text{Mrads/sec}} + \frac{1}{48.78\text{Mrads/sec}}} = 32.75 \text{ Mrads/sec.} \rightarrow f_{-3\text{dB}} = \underline{\underline{5.21\text{MHz}}}$$

Using the more exact analysis of algebraically solving the nodal equations gives $f_{-3\text{dB}} = \underline{\underline{5.95\text{MHz}}}$

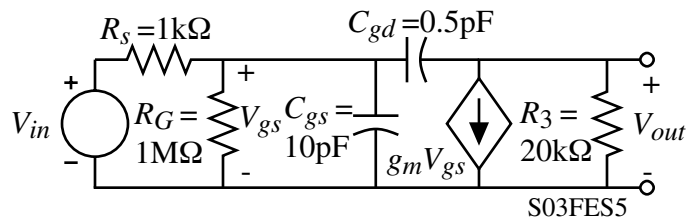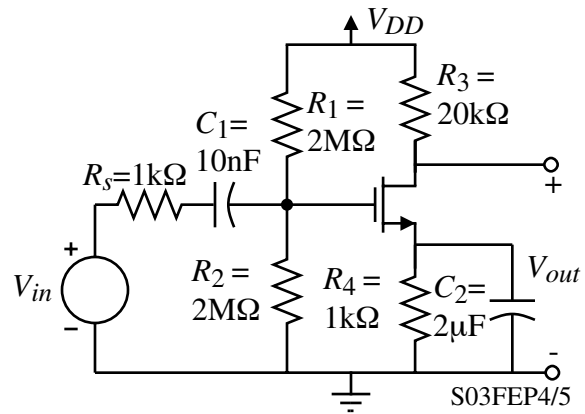



Problem 6 - (20 points - This problem is optional).

A BJT amplifier is shown. Assume that the BJT has the small signal parameters of $\beta_F = 100$, $V_f = 25\text{mV}$, and $V_A = \infty$.

- Find the midband voltage gain of this amplifier, V_{out}/V_{in} .
- Find the value of the lower -3dB frequency, f_L , in Hz, using any method that is appropriate.

Solution

Small-signal model for this problem:

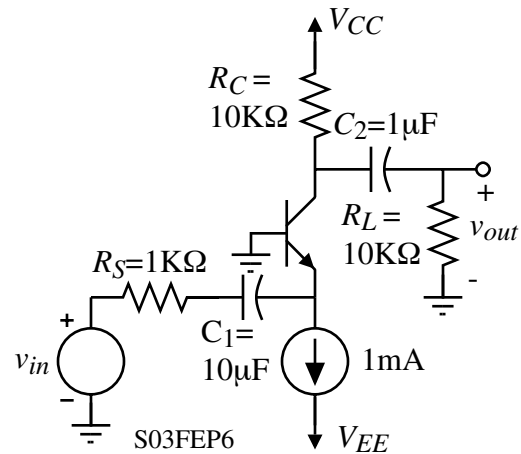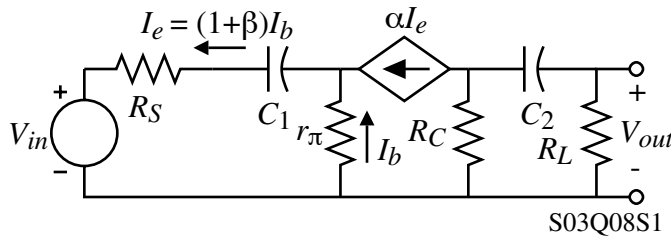

$$g_m = \frac{1\text{mA}}{25\text{mV}} = 40\text{mS}$$

$$r_\pi = \frac{\beta_F}{g_m} = 2.5\text{k}\Omega$$

Use the direct approach:

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \left(\frac{V_{out}}{I_e}\right) \left(\frac{I_e}{V_{in}}\right) = \left(\frac{-\alpha_F R_C R_L}{R_C + R_L + \frac{1}{sC_2}}\right) \left(\frac{-1}{R_S + \frac{1}{sC_1} + \frac{1}{g_m}}\right) \\ &= \left(\frac{\alpha_F R_C R_L}{R_C + R_L}\right) \left(\frac{g_m}{1 + g_m R_S}\right) \left(\frac{s}{s + \frac{1}{C_2(R_C + R_L)}}\right) \left(\frac{s}{s + \frac{1}{C_1\left(R_S + \frac{1}{g_m}\right)}}\right) \end{aligned}$$

$$\therefore MBG = \left(\frac{\alpha_F R_C R_L}{R_C + R_L}\right) \left(\frac{g_m}{1 + g_m R_S}\right) = (5\text{K}) \left(\frac{40\text{mS}}{1 + 40}\right) = \frac{200}{41} = \underline{\underline{+4.878\text{V/V}}}$$

$$\omega_1 = \frac{1}{C_1\left(R_S + \frac{1}{g_m}\right)} = \frac{10^6}{10(1000 + 25)} = 97.56 \text{ rads/sec.}$$

$$\omega_2 = \frac{1}{C_2(R_C + R_L)} = \frac{10^6}{1(20\text{K})} = 50 \text{ rads/sec.}$$


Since ω_1 and ω_2 are within an octave of each other then there is no dominant root so that we will simply sum the roots which is identical with the short-circuit time constant approach to give, ω_L as,

$$\omega_L \approx \omega_1 + \omega_2 = 147.56 \text{ rads/sec.} \rightarrow f_L \approx \underline{\underline{23.5 \text{ Hz}}}$$

Problem 7 – (20 points, this problem is optional)

A common-emitter BJT amplifier is shown. Assume that the BJT has a $\beta = h_{fe} = 100$, $C_{\mu} = 2\text{pF}$, $V_T = 25\text{mV}$, $f_T = 500\text{MHz}$, $r_b = 0\Omega$, and $r_o = \infty$.

- a.) Find the numerical values of r_{π} , g_m , and C_{π}
 b.) If $r_{\pi} = 1\text{k}\Omega$, $g_m = 0.01\text{A/V}$ and $C_{\pi} = 10\text{pF}$ for the above amplifier, find the value of the upper -3dB frequency, f_H , in Hz.

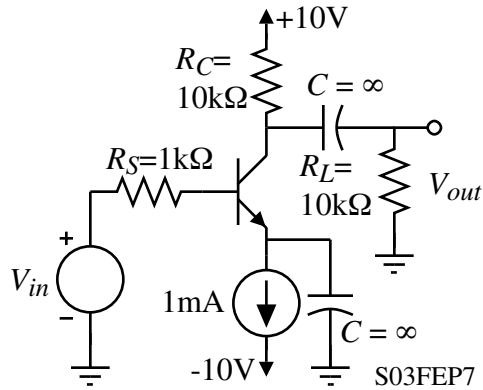
Solution

$$a.) \quad g_m = \frac{I_C}{V_T} = \frac{1\text{mA}}{25\text{mV}} = 0.04 \text{ A/V}$$

$$r_{\pi} = \frac{\beta_o}{g_m} = \frac{100}{0.04} = 2500\Omega$$

$$C_{\pi} = \frac{g_m}{\omega_T} - C_{\mu} = \frac{0.04}{2\pi \cdot 500 \times 10^6} - 2\text{pF} = 12.732\text{pF} - 2\text{pF} = 10.732 \text{ pF}$$

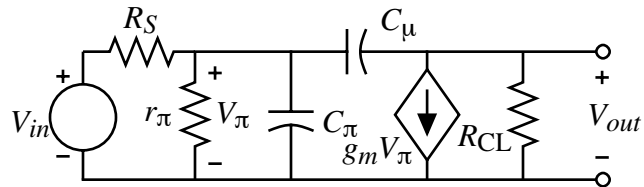- b.) The high-frequency, small-signal model for this problem is shown where $R_{CL} = R_C \parallel R_L = 5\text{k}\Omega$. The midband gain of this amplifier is given by



$$\frac{V_{out}}{V_{in}} = \left(\frac{V_{out}}{V_{\pi}} \right) \left(\frac{V_{\pi}}{V_{in}} \right) = -g_m R_{CL} \left(\frac{r_{\pi}}{r_{\pi} + R_S} \right) = (-0.01 \cdot 5\text{k}\Omega)(0.5) = -25\text{V/V}$$

$$\therefore \text{MBG} = -25 \text{ V/V}$$

Using Miller's theorem on this problem:

$$\text{If } \frac{1}{\omega_H C} \gg R_C \parallel R_L, \text{ then } C_{eq} \approx C_{\pi} + C_{\mu} (1 + g_m R_C \parallel R_L) = 10\text{pf} + 2\text{pF}(1+50) = 112\text{pF}$$

$$\text{We know that, } \omega_H = \frac{1}{C_{eq}(r_{\pi} \parallel R_S)} = \frac{1}{(112\text{pF} \cdot 500\Omega)} = 17.86 \text{ Mrads/sec.}$$

$$\therefore f_H = \frac{\omega_H}{2\pi} = 2.842 \text{ MHz}$$

Note that:



$$\frac{1}{\omega_H C} = \frac{10^6}{17.86 \cdot 2} = 28.06\text{k}\Omega > 5\text{k}\Omega \text{ so the Miller approximation (neglecting } C_{\mu}) \text{ is valid.}$$

Problem 8 – (20 points, this problem is optional)


A feedback amplifier is shown. Use the methods of feedback analysis to find the numerical values of v_2/v_1 , v_1/i_1 , and v_2/i_2 . Assume that all transistors are matched and that $g_m = 1\text{mS}$, and $r_{ds} = \infty$.

Solution

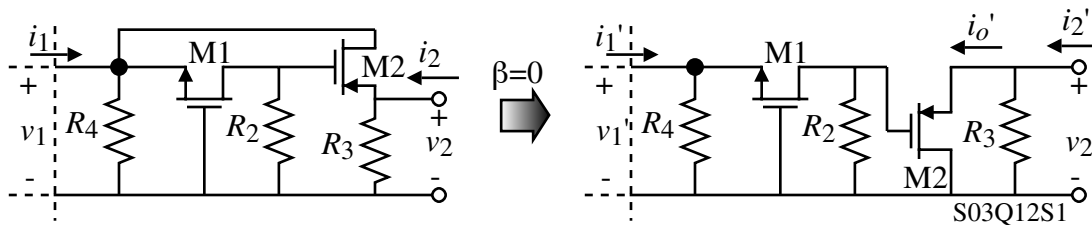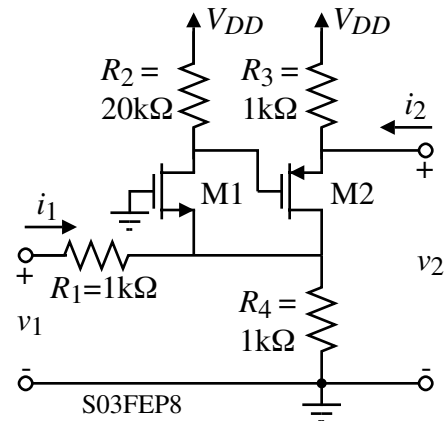The feedback circuit is shunt-series. You should know by now not to include R_1 in the feedback circuit. The simplified transistor circuit and the open-loop equivalent is shown below. It is easy to see that $\beta = i_{1F}/i_{2F} (v_{1F}=0) = -1$.



The small-signal, open-loop circuit is,

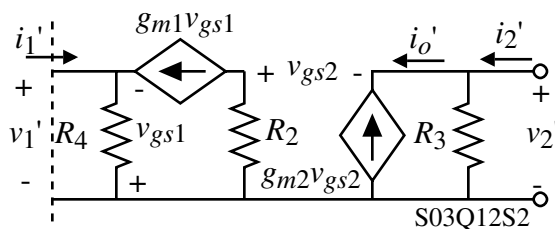

$$A = \frac{i_o'}{i_1'} = \left(\frac{i_o'}{v_{gs2}'}\right) \left(\frac{v_{gs2}'}{v_{g2}'}\right) \left(\frac{v_{g2}'}{v_{gs1}'}\right) \left(\frac{v_{gs1}'}{i_1'}\right)$$

$$v_{gs2}' = v_{g2}' - v_{s2}' = v_{g2}' - g_{m2}R_3 v_{gs2}'$$

$$\therefore v_{gs2}'(1 + g_{m2}R_3) = v_{g2}'$$

Also, $i_1' + \frac{v_{gs1}'}{R_4} + g_{m1}v_{gs1}' = 0 \Rightarrow$

$$i_1' = -\left(\frac{1}{R_4} + g_{m1}\right) v_{gs1}'$$

$$\therefore A = \frac{i_o'}{i_1'} = (-g_{m2}) \left(\frac{1}{1 + g_{m2}R_3}\right) (-g_{m1}R_2) \left(\frac{-1}{\frac{1}{R_4} + g_{m1}}\right) = (-1\text{mS})(0.5)(-20)(-0.5\text{k}\Omega) = -5$$

A/A

Now, $\frac{i_o}{i_1} = \frac{-5}{1 + (-1)(-5)} = -\frac{5}{6} \text{ A/A}$

$$R_{in}(\beta=0) = R_4 \parallel (1/g_{m1}) = 0.5\text{k}\Omega, R_{inF} = \frac{0.5\text{k}\Omega}{1+5} = \frac{1}{12} \text{ k}\Omega = 83.33\Omega \quad \frac{v_1}{i_1} = \underline{\underline{1083.33\Omega}}$$

$$\frac{v_2}{v_1} = \frac{i_o}{i_1} \left(\frac{-R_3}{(v_1/i_1)}\right) = -\frac{5}{6} \frac{-1000}{1083.33} = \frac{10}{13} = \underline{\underline{0.7692 \text{ V/V}}}$$

$$R_o(\beta=0) = R_3 + (1/g_{m2}) = 2\text{k}\Omega, \quad R_{oF} = 2\text{k}\Omega(1+5) = 12\text{k}\Omega$$

$$\frac{v_2}{i_2} = (12\text{k}\Omega - 1\text{k}\Omega) \parallel 1\text{k}\Omega = 11\text{k}\Omega \parallel 1\text{k}\Omega = \frac{11}{12} \text{ k}\Omega = \underline{\underline{916.67\Omega}}$$