

Homework Assignment No. 1 – Solutions**Problem 1**

(a.) The first thing to do is to find Thevenin's equivalent circuit seen from the diode.

The Thevenin voltage is,

$$V_{TH} = V_{IN} \left(\frac{2}{3} - \frac{1}{3} \right) = \frac{V_{IN}}{3}$$

The Thevenin resistance is,

$$R_{TH} = 1\text{k}\Omega \parallel 2\text{k}\Omega + 1\text{k}\Omega \parallel 2\text{k}\Omega = \frac{4}{3} \text{ k}\Omega$$



The equivalent circuit now becomes,

Now, with $V_{IN} = 10\text{V}$, we know the diode is forward biased. Therefore, replacing it with a short-circuit gives,

$$V_D = \underline{0\text{V}} \quad \text{and} \quad I_D = \frac{10}{3} \times \frac{3}{4\text{k}\Omega} = \underline{2.5\text{mA}}$$

(b.) With $V_{IN} = -10\text{V}$, we know the diode is reverse biased. Therefore replacing it with an open-circuit gives,

$$V_D = \underline{-3.33\text{V}} \quad \text{and} \quad I_D = \underline{0\text{mA}}$$

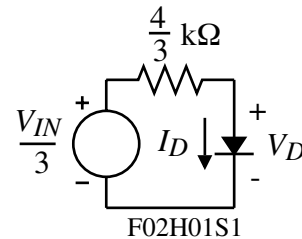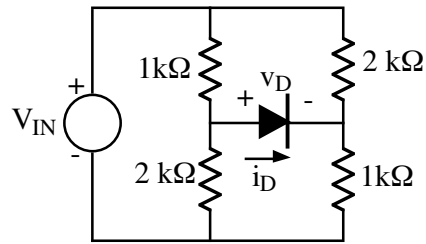


Problem 2

An enhancement NMOS amplifier is shown. The following questions are independent of each other (i.e. the answer of one is *not* used in the next question).

(a.) If $I_D = 0.5\text{mA}$, $V_T = 1\text{V}$, and $K = 0.5\text{mA/V}$, find g_m .

(b.) If $g_m = 0.5\text{mA/V}$ and $r_o = \infty$, find an algebraic expression for R_{out} and $A_v = v_{out}/v_{in}$.

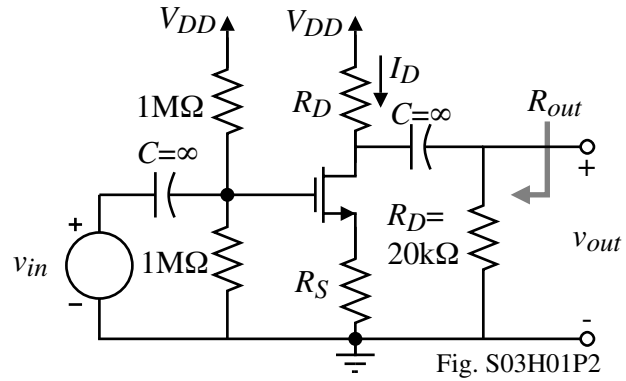(c.) Design R_D and R_S to give $R_{out} = 10\text{k}\Omega$ and $A_v = -10\text{V/V}$ if $g_m = 2\text{mA/V}$ and $r_o = \infty$.



Solution


a.) $g_m = \sqrt{2KI_D} = \sqrt{2 \cdot 500 \cdot 500} \mu\text{A} = 707\mu\text{S} = \underline{0.707\text{mS}}$

b.) The corresponding small-signal model:

$$\frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_{gs}} \frac{v_{gs}}{v_{in}}$$

$$\frac{v_{out}}{v_{gs}} = -g_m(R_D \parallel R_L)$$
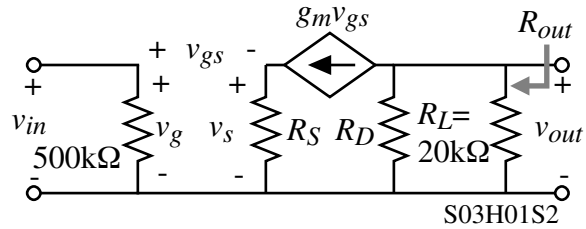
$$v_{gs} = v_g - v_s = v_{in} - (g_m R_S v_{gs})$$




which gives $\frac{v_{gs}}{v_{in}} = \frac{1}{1+g_m R_S} \rightarrow \frac{v_{out}}{v_{gs}} = \frac{-g_m(R_D \parallel R_L)}{1+g_m R_S}$ and $R_{out} = R_D \parallel R_L$

c.) $R_{out} = 10\text{k}\Omega = R_D \parallel R_L = R_D \parallel 20\text{k}\Omega \rightarrow R_D = \underline{20\text{k}\Omega}$

$$\frac{v_{out}}{v_{in}} = -10 = \frac{-g_m(R_D \parallel R_L)}{1+g_m R_S} = \frac{-20}{1 + \frac{R_S}{500}} \rightarrow R_S = \underline{500\Omega}$$

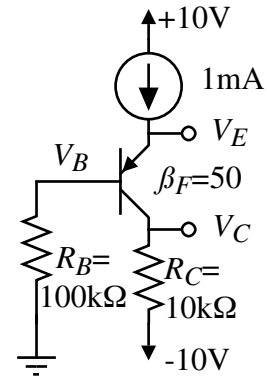Problem 3

A pnp BJT circuit is shown. (a.) Find the dc values of I_E , I_C , I_B , V_E , V_C and V_B if $\beta = 50$ and $V_{EB(on)} = 0.65V$. (b.) For what value of R_C does the BJT become saturated? (Recall that saturation of a BJT corresponds to the BE and BC junctions forward biased.)



Solution

(a.) Note that $I_E = 1\text{mA}$ $\alpha_F = \frac{\beta_F}{1 + \beta_F} = \frac{50}{51} = 0.98$

$\therefore I_C = \alpha_F I_E = 0.98 \cdot 1\text{mA} = 0.98\text{mA} \Rightarrow I_C = 0.98\text{mA}$

$I_B = \frac{I_C}{\beta_F} = \frac{0.98\text{mA}}{50} = 19.6\mu\text{A} \Rightarrow I_B = 19.6\mu\text{A}$


Now, $V_B = I_B \cdot 100\text{k}\Omega = 1.96\text{V} \Rightarrow V_B = 1.96\text{V}$

$V_E = V_B + V_{EB(on)} = 1.96\text{V} + 0.65\text{V} = 2.61\text{V} \Rightarrow V_E = 2.61\text{V}$

Finally, $V_C = -10\text{V} + I_C \cdot 10\text{k}\Omega = -10\text{V} + 0.98\text{mA} \cdot 10\text{k}\Omega = -0.2\text{V} \Rightarrow V_C = -0.2\text{V} \approx 0\text{V}$

(b.) Saturation occurs when $V_{BC} = 0$ or $V_B = V_C$. Therefore, $V_C = 1.96\text{V}$. The current through R_C is still 0.98mA , so solving for R_C gives,

$R_C = \frac{V_C + 10\text{V}}{I_C} = \frac{11.96\text{V}}{0.98\text{mA}} = 12.20\text{k}\Omega \Rightarrow R_C = 12.2\text{k}\Omega$

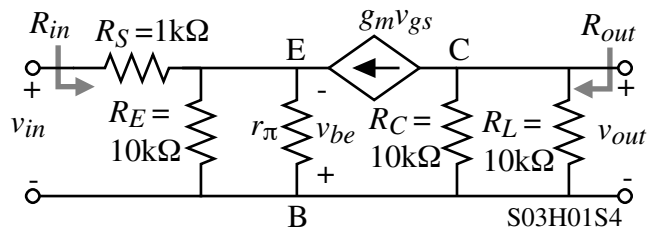

Problem 4

For the transistor shown, $\beta = 100$, $r_{\pi} = 2.5\text{k}\Omega$, and $g_m = 0.04\text{S}$. Draw the small signal model and find the numerical values of the small signal voltage gain, v_{out}/v_{in} , the input resistance, R_{in} , and the output resistance, R_{out} .

Solution

Small-signal model:


$$R_{in} = R_S + R_E \parallel \frac{r_{\pi}}{1+\beta} + R_S + R_E \parallel \frac{1}{g_m}$$

$$R_{in} = 1\text{k}\Omega + 10\text{k}\Omega \parallel 25\Omega = \underline{1024.9\Omega}$$

$$R_{out} = R_C \parallel R_L = \underline{5\text{k}\Omega}$$

$$\frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_{be}} \frac{v_{be}}{v_{in}} = [-g_m(R_C \parallel R_L)] \left(\frac{-\left(\frac{r_{\pi}}{1+\beta}\right) \parallel R_E}{R_S + \left(\frac{r_{\pi}}{1+\beta}\right) \parallel R_E} \right) = [-g_m(R_C \parallel R_L)] \left(\frac{-\left(\frac{1}{g_m}\right) \parallel R_E}{R_S + \left(\frac{1}{g_m}\right) \parallel R_E} \right)$$

$$= (-40 \cdot 3.33) \left(\frac{-24.9}{1024.9} \right) = \underline{+3.24\text{V/V}}$$

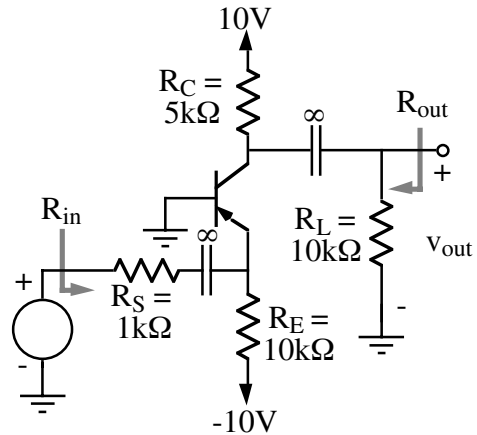

Problem 5

The following questions give the dc voltages at the terminals of an active device. You are to calculate the designated dc current.

- a.) Find the diode current, I_D , where $I_S = 100\text{fA}$ and $V_T = 0.025\text{V}$ (2 pts).


Obviously, the diode is forward biased. Therefore,

$$I_D = I_S \exp\left(\frac{V_D}{V_T}\right) = 10^{-13} \exp\left(\frac{0.6}{0.025}\right) = \underline{2.65 \text{ mA}}$$

- b.) Find the drain-source current, I_{DS} , where $K_n' = 25\mu\text{A}/\text{V}^2$, $V_{TN} = 1\text{V}$ and $W/L = 10$ (2 pts).

We see that the enhancement, n-channel MOSFET is in the saturation region. Therefore,
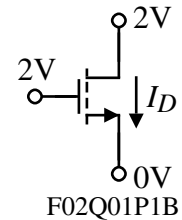
$$I_{DS} = \frac{K_n' W}{2L} (V_{GS} - V_{TN})^2 = \frac{25 \cdot 10}{2} (2-1)^2 = \underline{125 \mu\text{A}}$$




- c.) Find the collector, emitter, and base currents, I_C , I_E , and I_B if $I_S = 100\text{fA}$, $V_T = 0.025\text{V}$ and $\beta_F = 100$ (4 pts).

We see that the npn BJT is in the forward active region. Therefore,

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) = 10^{-13} \exp\left(\frac{0.7}{0.025}\right) = \underline{144.6 \text{ mA}}$$
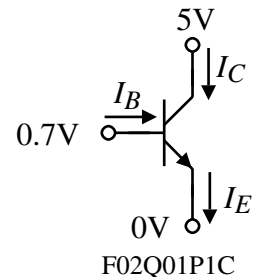
$$I_B = \frac{I_C}{\beta_F} = \underline{1.446 \text{ mA}} \quad \text{and} \quad I_E = I_C + I_B = \underline{146 \text{ mA}}$$



- d.) Repeat (b.) if $V_D = 1\text{V}$ and $V_G = 3\text{V}$ (2 pts).

We see that the enhancement, n-channel MOSFET is in the linear region. Therefore,

$$I_{DS} = K_n' \frac{W}{L} \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} = 25 \cdot 10 (3-1-0.5)(1) = \underline{375 \mu\text{A}}$$