


Homework Assignment No. 2 – Solutions**11.16**

$$g_{11} = \left. \frac{i_1}{v_1} \right|_{i_2=0} : v_1 = 10^4 i_1 + 101 i_1 (240\text{k}\Omega) \rightarrow g_{11} = 4.124 \times 10^{-8} \text{ S} = 4.12 \times 10^{-8} \text{ S}$$

$$g_{12} = \left. \frac{i_1}{i_2} \right|_{v_1=0} : i_1 = -\frac{240\text{k}\Omega}{240\text{k}\Omega + 10\text{k}\Omega} (i_2 + 100i_1) \rightarrow g_{12} = -9.90 \times 10^{-3}$$

$$g_{21} = \left. \frac{v_2}{v_1} \right|_{i_2=0} : v_2 = 101i_1(240\text{k}\Omega) \mid i_1 = g_{11}v_1 \rightarrow g_{21} = 1.00$$

$$g_{22} = \left. \frac{v_2}{i_2} \right|_{v_1=0} : i_2 = \frac{v_2}{240\text{k}\Omega} + \frac{v_2}{10\text{k}\Omega} + 100 \frac{v_2}{10\text{k}\Omega} \rightarrow g_{22} = 99.0 \Omega$$

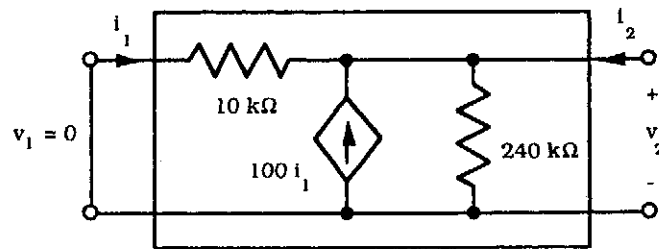**11.34**

$$V_o = V_s \frac{R_{IN}}{R_{IN} + R_s} A \frac{R_{IN}}{R_{IN} + R_{OUT}} A \frac{R_L}{R_L + R_{OUT}}$$

$$A_v = \frac{5000}{5000 + 1000} (-1000) \frac{5000}{5000 + 250} (-1000) \frac{100}{100 + 250} = +2.27 \times 10^5$$

$$A_i = \frac{I_o}{I_s} = \frac{2.27 \times 10^5 V_s}{100} \frac{1}{\frac{V_s}{6000}} = +1.36 \times 10^7$$

$$A_p = \frac{2.27 \times 10^5 V_s (+1.36 \times 10^7 I_s)}{V_s I_s} = +3.09 \times 10^{12}$$

11.37


$$A_v = \frac{2\pi \times 10^7 s}{(s + 20\pi)(s + 2\pi \times 10^4)} = \frac{1000s}{(s + 20\pi) \left(1 + \frac{s}{2\pi \times 10^4}\right)} \mid A_{\text{mid}} = +1000 = 60 \text{ dB}$$

$$f_L = \frac{20\pi}{2\pi} = 10 \text{ Hz} \mid f_H = \frac{2\pi \times 10^4}{2\pi} = 10 \text{ kHz} \mid \text{BW} = 10\text{kHz} - 10\text{Hz} = 9.99 \text{ kHz}$$

Bandpass Amplifier

11.43

Using MATLAB: `n=[2e7*pi 0]; d=[1 (20*pi+2e4*pi) 40e4*pi^2]; bode(n,d)`

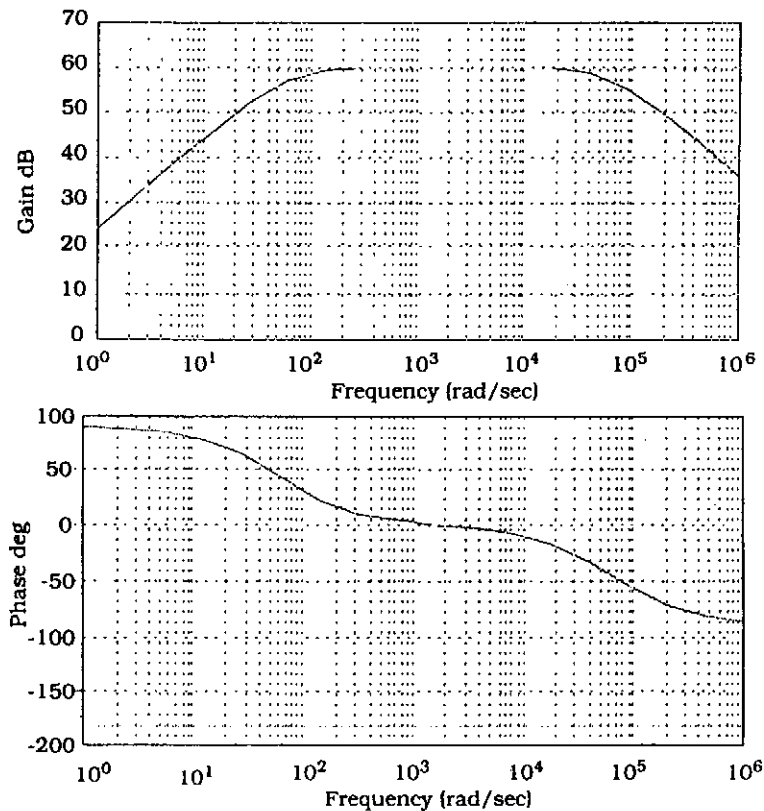
**11.55**

$$(a) A_{mid} = +10^{\frac{20}{20}} = +10 \quad | \quad A_v = \frac{10}{1 + \frac{s}{2\pi \times (5 \times 10^6)}} = \frac{10}{1 + \frac{s}{10^7 \pi}} = \frac{10^8 \pi}{s + 10^7 \pi}$$

$$(b) A_{mid} = -10^{\frac{20}{20}} = -10 \quad | \quad A_v = -\frac{10^8 \pi}{s + 10^7 \pi}$$

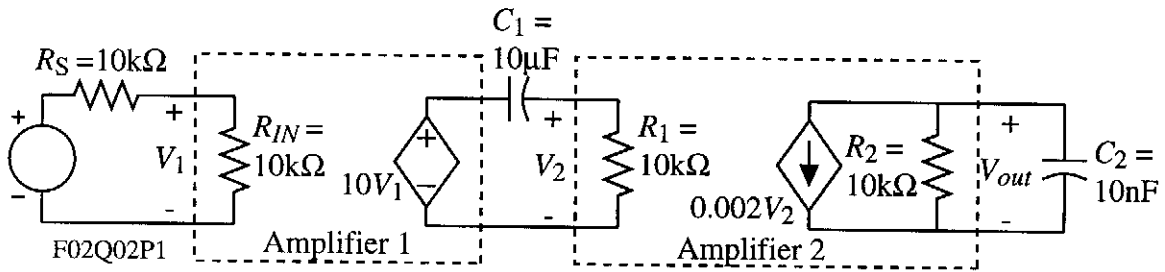Problem 6

a.) Find the transfer function, $V_{out}(s)/V_S(s)$, of the circuit shown and identify the location of the poles and zeros. What is the gain in the region where the transfer function is independent of frequency?



$$\frac{V_{out}(s)}{V_S(s)} = \left(\frac{V_{out}}{V_2} \right) \left(\frac{V_2}{V_1} \right) \left(\frac{V_1}{V_{in}} \right) = \left(\frac{-G(R_2/sC_2)}{R_2 + 1/sC_2} \right) \left(\frac{10R_1}{R_1 + 1/sC_1} \right) \left(\frac{R_{IN}}{R_S + R_{IN}} \right)$$

where $G = 0.002$ A/V. Rearranging gives,

$$\frac{V_{out}(s)}{V_S(s)} = \left(\frac{R_{IN}}{R_S + R_{IN}} \right) \left(\frac{10sR_1C_1}{sR_1C_1 + 1} \right) \left(\frac{-GR_2}{sR_2C_2 + 1} \right) = \left(\frac{10(-20)}{2} \right) \left(\frac{\frac{s}{10}}{\frac{s}{10} + 1} \right) \left(\frac{1}{\frac{s}{10^4} + 1} \right)$$

Poles are at -10 rads/sec. and -10^4 rads/sec. and the zeros are at 0 and ∞ .

The gain in the frequency independent range (midband) is $-100V/V$.

b.) Sketch the asymptotic (straight-line) plot for the magnitude and phase of transfer function shown. Use the same plot for phase shift. Label the phase shift on the right side of the plot.

$$A(s) = \frac{-10s}{(s+1)(s+100)} \rightarrow A(j\omega) = \left(\frac{-10}{100} \right) \left(\frac{\frac{j\omega}{1}}{\left(1 + \frac{j\omega}{1} \right) \left(1 + \frac{j\omega}{100} \right)} \right)$$

The asymptotic plot of the magnitude and phase of the above transfer function is shown:

