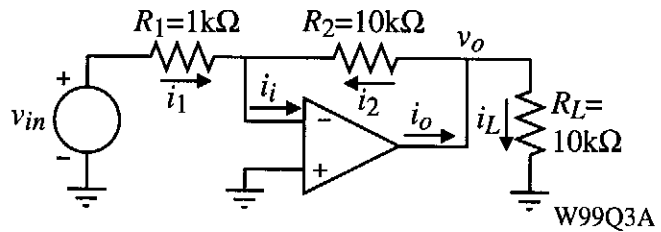


Homework Assignment No. 3 - Solution

1.) The op amps in this problem are ideal.

a.) If $v_{in} = +1V$, find the value the currents i_1 , i_i , i_2 , i_o , and i_L including the sign.



$$i_1 = \frac{1V}{1k\Omega} = 1mA$$

$$i_i = 0$$

$$i_2 = \frac{-10V}{10k\Omega} = -1mA$$

$$i_L = \frac{-10V}{1k\Omega} = -1mA$$


$$i_o = i_2 + i_L = -2mA$$

b.) Express v_o as a function of v_1 and v_2 .

Note: $v_{o1} = -v_2$

And

$$v_o = -5v_1 - 10v_{o1}$$

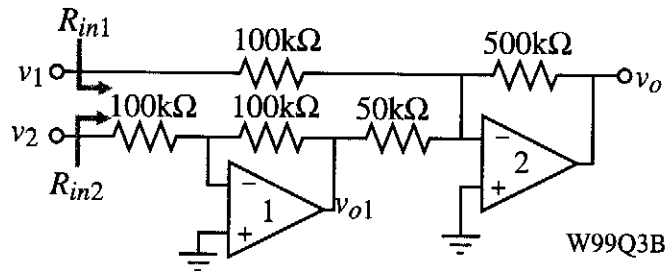

$$\therefore v_o = -5v_1 - 10(-v_2) = -5v_1 + 10v_2$$

$$v_o = -5v_1 + 10v_2$$

$$R_{in1} = R_{in2} = 100k\Omega$$


c.) Find R_{in} and v_o if $i_1 = 0.1mA$.

$$R_{in} = 0$$


and

$$v_o = 100k\Omega \cdot i_1 = 100k\Omega \cdot 0.1mA = 10V$$

R_{in} and v_o if $i_1 = 0.1mA$.

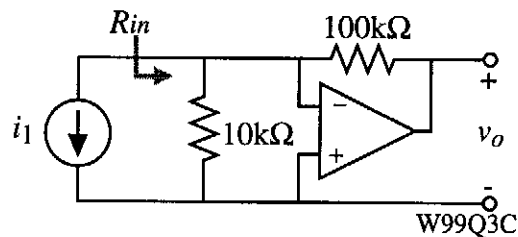

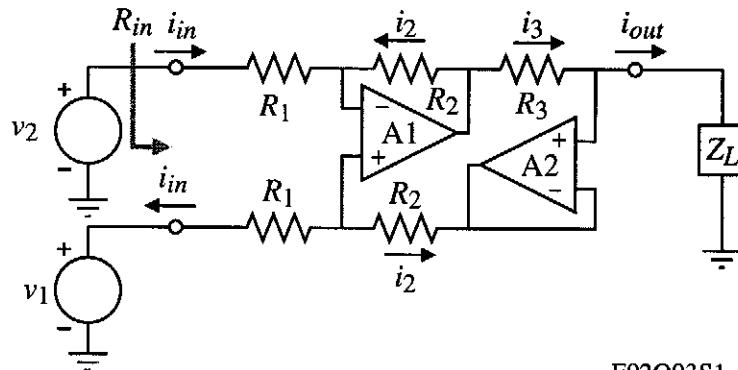2.) Assume that the op amps are ideal and find i_{out} as a function of the inputs, v_1 and v_2 . Find the input resistance defined as $R_{in} = (v_2 - v_1)/i_{in}$.



F02Q03S1

Solution

From the circuit we can write the following equations based on an ideal op amp:

$$i_{out} = i_3, \quad v_2 - v_1 = 2R_1 i_{in}, \quad i_2 R_2 + i_2 R_2 = i_3 R_3, \quad i_{in} = -i_2$$

$$\therefore i_{out} = i_3 = \frac{2R_2 i_2}{R_3} = \frac{2R_2}{R_3} (-i_{in}) = \frac{2R_2}{R_3} \left(-\frac{v_2 - v_1}{2R_1} \right) = \frac{R_2}{R_1 R_3} (v_1 - v_2)$$

$$i_{out} = \frac{R_2}{R_1 R_3} (v_1 - v_2)$$

The input resistance, R_{in} is seen to be equal to $2R_1$. $R_{in} = 2R_1$

12.21 (a) Note that voltages refer to the node numbers on the next page

Using voltage division since $i_+ = 0$, $v_2 = v_4 + 6 \frac{4.99\text{k}\Omega}{4.99\text{k}\Omega + 5.00\text{k}\Omega}$

$$v_2 = v_4 + (6 - v_4) \frac{4.99\text{k}\Omega}{4.99\text{k}\Omega + 5.00\text{k}\Omega} = 0.5005v_4 + 2.997\text{V}$$

Since $v_{id} = 0$, $v_1 = v_2$ and $v_5 = v_1 - \frac{4 - v_1}{5\text{k}\Omega} (5.01\text{k}\Omega)$



Solving for v_5 yields $v_5 = 1.992\text{V} + 1.002v_4$

$$i_o = \frac{v_5 - v_4}{10\text{k}\Omega} = 199\mu\text{A} + 2 \times 10^{-7} v_4$$

v_4 is unknown; let us assume $2 \times 10^{-7} v_4 \ll 199 \times 10^{-6} \text{A}$ which requires $v_4 \ll 995\text{V}$. So for $v_4 < 100\text{V}$, which should almost always be true in transistor circuits, $i_o = 199\mu\text{A}$.

For $Z_L = 10\text{k}\Omega$, $v_4 = 1.99\text{V}$, $v_2 = 3.99\text{V}$, $v_1 = 3.99\text{V}$, $v_5 = 3.99\text{V}$

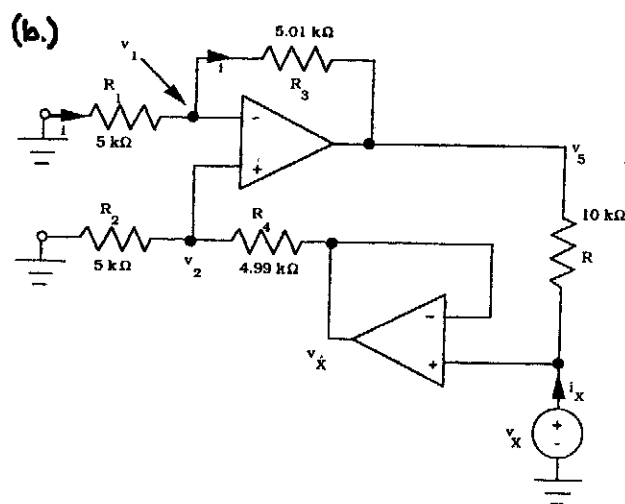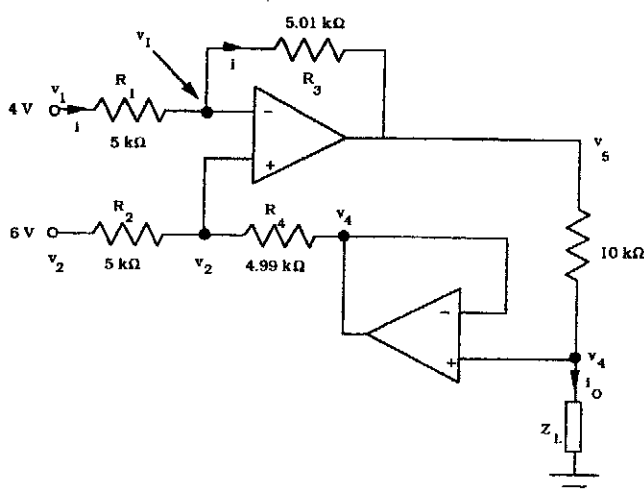Note that $v_5 - v_4 = 2\text{V} = (6\text{V} - 4\text{V})$



$R_{\text{OUT}} = \frac{v_x}{i_x}$ and $i_x = \frac{v_x - v_5}{10\text{k}\Omega}$ So we need to find i_x , and hence v_5 , in terms of v_x

$$v_1 = v_2 = v_x \frac{5.00\text{k}\Omega}{4.99\text{k}\Omega + 5.00\text{k}\Omega} = 0.5005v_x$$

$$v_5 = v_1 + i (5.01\text{k}\Omega) = v_1 + \frac{v_1}{5\text{k}\Omega} (5.01\text{k}\Omega) = 2.002v_1 = 1.002v_x$$

$$i_x = \frac{v_x - v_5}{10\text{k}\Omega} = \frac{v_x - 1.002v_x}{10\text{k}\Omega} = -\frac{0.002v_x}{10\text{k}\Omega} \text{ and } R_{\text{OUT}} = -5\text{M}\Omega! \text{ A negative output resistance!}$$

12.24 Applying op-amp assumption 1 to the circuit on the next page, the voltage at the top of R_2 is v_{O2} , and applying op-amp assumption 2,


$$\frac{v_s}{R_1} = -\frac{v_{O2}}{R_2} \quad \text{or} \quad v_{O2} = -v_s \frac{R_2}{R_1}$$

Since the op-amp input currents are zero, and

$$i = \frac{v_s}{R_1}, \quad v_{O1} = -iR_2 - iR_3 = -\left(\frac{R_2}{R_1} + \frac{R_3}{R_1}\right)v_s$$

Alternatively, the voltage at the bottom of R_2 is zero, so
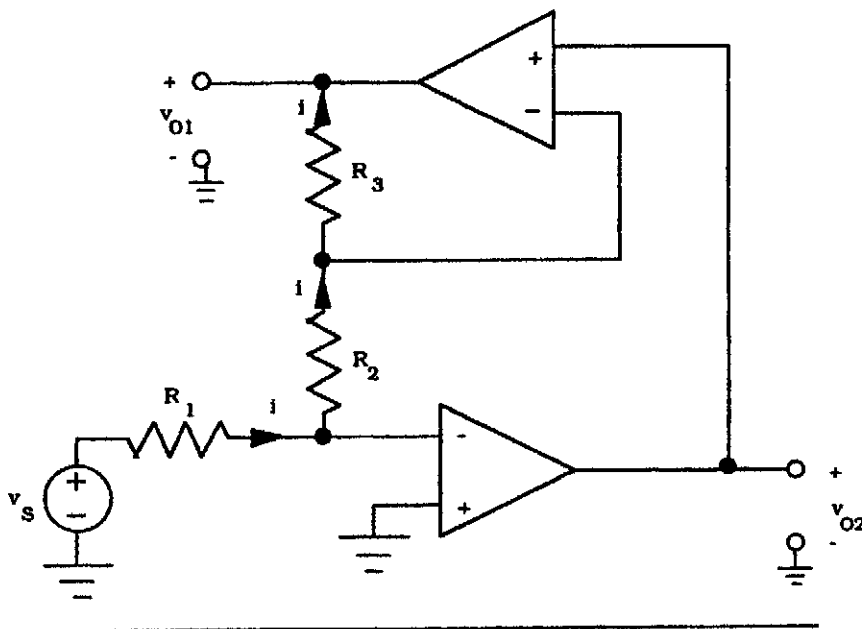
$$v_{O1} = \left(1 + \frac{R_3}{R_2}\right)v_{O2} = \left(1 + \frac{R_3}{R_2}\right)\left(-\frac{R_2}{R_1}\right)v_s = -\left(\frac{R_2}{R_1} + \frac{R_3}{R_1}\right)v_s$$



12.74

$$\beta = \frac{2\text{k}\Omega}{2\text{k}\Omega + 40\text{k}\Omega} = \frac{1}{21} \quad | \quad A\beta = \frac{10^5}{21} = 4760 \gg 1$$

$$(a) \quad A_V = -\frac{R_2}{R_1} = -\frac{40\text{k}\Omega}{2\text{k}\Omega} = -20 \quad | \quad f_H = \beta f_T = \frac{3 \times 10^6 \text{ Hz}}{21} = 143 \text{ kHz}$$

$$(b) \quad A_V = (-20)^3 = -8000 \text{ (78dB)} \quad | \quad f_{H3} = 0.51 f_H = 72.9 \text{ kHz}$$