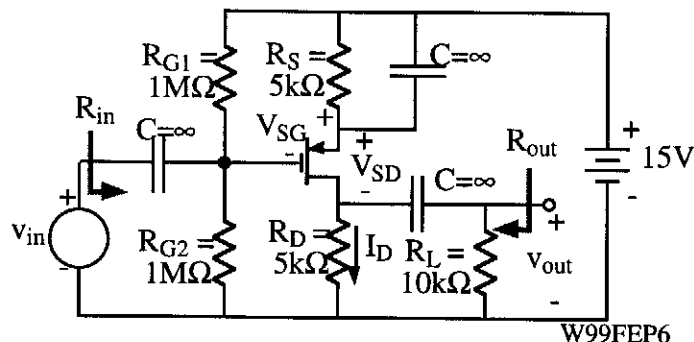


Homework Assignment No. 5 - Solutions

1.) Find the dc operating point, the small signal voltage gain, v_{out}/v_{in} , the small signal input resistance, R_{in} , and the small signal output resistance, R_{out} , if $K = 0.1\text{mA/V}^2$, $V_t = -1\text{V}$, and $\lambda = 0.01\text{V}^{-1}$.

**Solution**

Finding the dc Thevenin equivalent circuit looking out the gate gives $V_{GG} = 7.5\text{V}$ and $R_G = 0.5\text{M}\Omega$. Assuming saturation gives $I_D = K(V_{GS} - V_t)^2$. Combining with

$$V_{GG} = 7.5\text{V} = V_{GS} + I_D R_S$$

gives $7.5 = V_{GS} + 5\text{k}\Omega \cdot 0.1\text{mA/V}^2 (V_{GS} - 1)^2 = V_{GS} + 0.5V_{GS}^2 - V_{GS} + 0.5$

which reduces to $V_{GS}^2 = 14 \rightarrow V_{GS} = \sqrt{14} = 3.74\text{V}$

This gives $I_D = 0.1\text{mA}(3.75 - 1)^2 = 0.752\text{mA}$. Finally, $V_{DS} = 15 - I_D(R_D + R_S) = 7.48\text{V}$

$$\therefore \boxed{V_{SG} = 3.74\text{V}, I_D = 0.752\text{mA} \text{ and } V_{SD} = 7.48\text{V}}$$

Note that the MOSFET is indeed saturated.


The small signal model parameters are $g_m = 2\sqrt{KI_D} = 2\sqrt{0.1 \cdot 0.752} = 0.548\text{mA/V}$ and

$$r_{ds} = (\lambda I_D)^{-1} = 100/0.752 = 133\text{k}\Omega.$$

The small-signal model for this problem is,

$$\frac{v_{out}}{v_{in}} = -g_m (r_{ds} \parallel R_D \parallel R_L) = -0.548(133 \parallel 5 \parallel 10) \\ = -1.782\text{V/V}, R_{in} = 500\text{k}\Omega$$

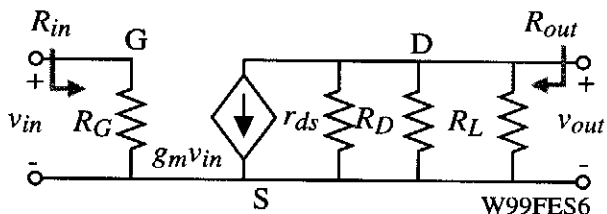and $R_{out} = r_{ds} \parallel R_D \parallel R_L = 3.25\text{k}\Omega$.



$$\therefore \boxed{R_{in} = 500\text{k}\Omega, R_{out} = 3.25\text{k}\Omega \text{ and } \frac{v_{out}}{v_{in}} = -1.782\text{ V/V}}$$

2.) Problem 13.91 of the text.

3.) Problem 13.100 of the text. [$A_v = -4.60\text{ V/V}$]

4.) Problem 13.108 of the text.

13.91

$$g_m = \sqrt{2 \left(500 \frac{\mu\text{A}}{\text{V}^2} \right) (100 \mu\text{A}) (1 + 0.02(5))} = 332 \mu\text{S} \quad | \quad r_o = \frac{50 + 5\text{V}}{100 \mu\text{A}} = 550 \text{k}\Omega$$

$$A_v = - \left(\frac{6.8 \text{M}\Omega}{6.8 \text{M}\Omega + 0.1 \text{M}\Omega} \right) (332 \mu\text{S}) (550 \text{k}\Omega \parallel 50 \text{k}\Omega \parallel 120 \text{k}\Omega) = -10.9$$

13.100

$$g_m = \frac{2}{3} \sqrt{1 \text{mA} (1 \text{mA}) [1 + 0.015(9)]} = 710 \mu\text{S} \quad | \quad r_o = \frac{1}{0.015} + 9\text{V} = 75.7 \text{k}\Omega$$


$$A_v = - \left(\frac{1 \text{M}\Omega}{1 \text{M}\Omega + 10 \text{k}\Omega} \right) (710 \mu\text{S}) (75.7 \text{k}\Omega \parallel 7.5 \text{k}\Omega \parallel 160 \text{k}\Omega) = -4.60$$

13.108

$$R_{\text{IN}} = R_G = 6.8 \text{M}\Omega \quad | \quad R_{\text{OUT}} = 50 \text{k}\Omega \parallel r_o$$

$$r_o = \frac{(50 + 5)\text{V}}{0.1 \text{mA}} = 550 \text{k}\Omega \quad | \quad R_{\text{OUT}} = 50 \text{k}\Omega \parallel 550 \text{k}\Omega = 45.8 \text{k}\Omega$$

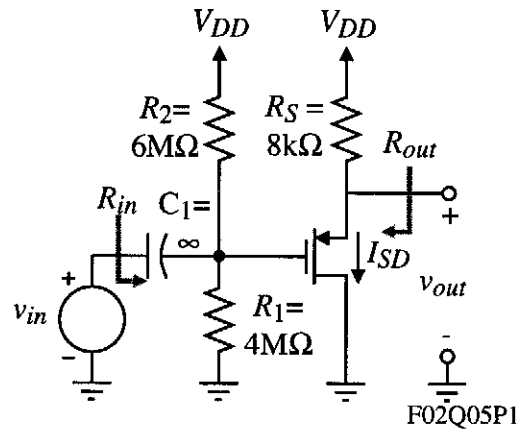5.) A PMOS common-drain amplifier is shown. Assume the parameters of the transistor are $k_F = 0.5\text{mA/V}^2$, $V_{TP} = -1\text{V}$, and $\lambda = 0$. (a.) If $I_{SD} = 0.5\text{mA}$, find the small signal model parameter values for g_m and r_o . (b.) Find an algebraic expression for the small signal input resistance, R_{in} , the output resistance, R_{out} , and the voltage gain, v_{out}/v_{in} . (c.) Numerically evaluate the small signal input resistance, R_{in} , the output resistance, R_{out} , and the voltage gain, v_{out}/v_{in} .




Solution

$$(a.) g_m = \sqrt{2I_{SD}k_P} = \sqrt{2 \cdot 0.5 \cdot 0.5} \text{ mS} = \underline{0.707\text{mS}}$$

and $r_o = \infty$

(b.) First we need a small signal model.

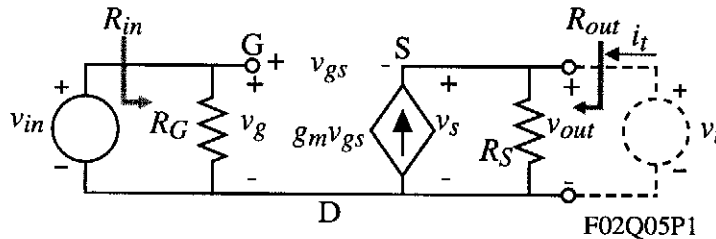

Obviously, $R_{in} = R_G = R_1 \parallel R_2$. For R_{out} we apply the voltage source, v_t , and set $v_{in} = 0$ and solve for v_t/i_t which equivalent to R_{out} .

$$\begin{aligned} \therefore i_t &= G_S v_t - g_m v_{gs} = G_S v_t - g_m (v_g - v_s) = G_S v_t - g_m (0 - v_s) \\ &= G_S v_t + g_m v_s = G_S v_t + g_m v_t = (G_S + g_m) v_t \end{aligned}$$

$$\therefore R_{out} = \frac{v_t}{i_t} = \frac{1}{G_S + g_m} = \frac{R_S}{1 + g_m R_S} \rightarrow \boxed{R_{out} = \frac{R_S}{1 + g_m R_S}}$$

The output voltage can be expressed as,

$$v_{out} = g_m R_S v_{gs} = g_m R_S (v_g - v_s) = g_m R_S (v_{in} - v_{out})$$

$$\therefore v_{out}(1 + g_m R_S) = g_m R_S v_{in} \rightarrow \boxed{\frac{v_{out}}{v_{in}} = \frac{g_m R_S}{1 + g_m R_S}}$$

$$(c.) R_{in} = R_G = R_1 \parallel R_2 = \underline{2.4\text{M}\Omega}, R_{out} = \frac{8\text{k}\Omega}{1 + 0.707 \cdot 8} = \underline{1.2\text{k}\Omega} \text{ and } \frac{v_{out}}{v_{in}} = \frac{0.707 \cdot 8}{1 + 0.707 \cdot 8} = \underline{0.85\text{V/V}}$$