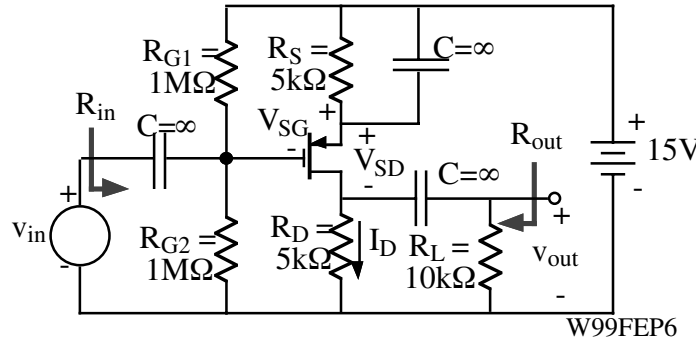


Homework Assignment No. 5

Due on Wednesday, February 12, 2003

1.) Find the dc operating point, the small signal voltage gain, v_{out}/v_{in} , the small signal input resistance, R_{in} , and the small signal output resistance, R_{out} , if $K_n = 0.1\text{mA/V}^2$, $V_{TP} = -1\text{V}$, and $\lambda = 0.01\text{V}^{-1}$.



- 2.) Problem 13.91 of the text.
- 3.) Problem 13.100 of the text. [$A_v = -4.60 \text{ V/V}$]
- 4.) Problem 13.108 of the text.

5.) A PMOS common-drain amplifier is shown. Assume the parameters of the transistor are $k_F = 0.5\text{mA/V}^2$, $V_{TP} = -1\text{V}$, and $\lambda = 0$. (a.) If $I_{SD} = 0.5\text{mA}$, find the small signal model parameter values for g_m and r_o . (b.) Find an algebraic expression for the small signal input resistance, R_{in} , the output resistance, R_{out} , and the voltage gain, v_{out}/v_{in} . (c.) Numerically evaluate the small signal input resistance, R_{in} , the output resistance, R_{out} , and the voltage gain, v_{out}/v_{in} .

