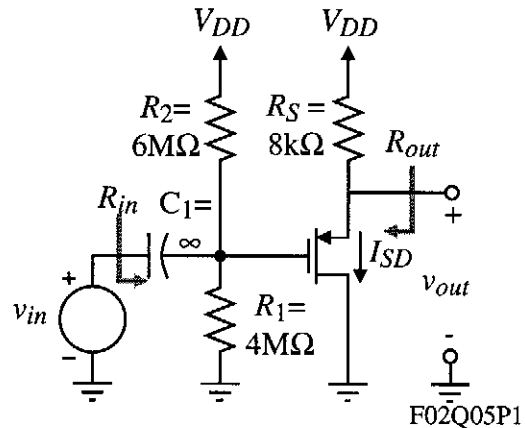


Homework Assignment No. 6 - Solution


- 1.) A PMOS common-drain amplifier is shown. Assume the parameters of the transistor are $k_F = 0.5\text{mA/V}^2$, $V_{TP} = -1\text{V}$, and $\lambda = 0$. (a.) If $I_{SD} = 0.5\text{mA}$, find the small signal model parameter values for g_m and r_o . (b.) Find an algebraic expression for the small signal input resistance, R_{in} , the output resistance, R_{out} , and the voltage gain, v_{out}/v_{in} . (c.) Numerically evaluate the small signal input resistance, R_{in} , the output resistance, R_{out} , and the voltage gain, v_{out}/v_{in} .



Solution

(a.) $g_m = \sqrt{2I_{SD}k_P} = \sqrt{2 \cdot 0.5 \cdot 0.5} \text{ mS} = \underline{0.707\text{mS}}$ and $r_o = \underline{\infty}$

(b.) First we need a small signal model.

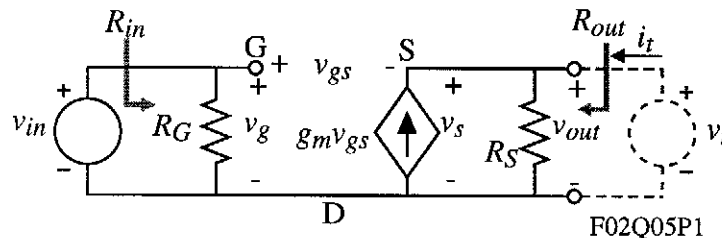

Obviously, $R_{in} = R_G = R_1 \parallel R_2$. For R_{out} we apply the voltage source, v_t , and set $v_{in} = 0$ and solve for v_t/i_t which equivalent to R_{out} .

$$\begin{aligned} \therefore i_t &= G_S v_t - g_m v_{gs} = G_S v_t - g_m (v_g - v_s) = G_S v_t - g_m (0 - v_s) \\ &= G_S v_t + g_m v_s = G_S v_t + g_m v_t = (G_S + g_m) v_t \end{aligned}$$

$$\therefore R_{out} = \frac{v_t}{i_t} = \frac{1}{G_S + g_m} = \frac{R_S}{1 + g_m R_S} \rightarrow \boxed{R_{out} = \frac{R_S}{1 + g_m R_S}}$$

The output voltage can be expressed as,

$$v_{out} = g_m R_S v_{gs} = g_m R_S (v_g - v_s) = g_m R_S (v_{in} - v_{out})$$

$$\therefore v_{out}(1 + g_m R_S) = g_m R_S v_{in} \rightarrow \boxed{\frac{v_{out}}{v_{in}} = \frac{g_m R_S}{1 + g_m R_S}}$$

(c.) $R_{in} = R_G = R_1 \parallel R_2 = \underline{2.4\text{M}\Omega}$, $R_{out} = \frac{8\text{k}\Omega}{1 + 0.707 \cdot 8} = \underline{1.2\text{k}\Omega}$ and $\frac{v_{out}}{v_{in}} = \frac{0.707 \cdot 8}{1 + 0.707 \cdot 8} = \underline{0.85\text{V/V}}$

14.13

$$V_{EQ} = 18 \frac{500\text{k}\Omega}{1.4\text{M}\Omega + 500\text{k}\Omega} = 4.74\text{V} \quad | \quad R_{EQ} = 500\text{k}\Omega \parallel 1.4\text{M}\Omega = 368\text{k}\Omega$$

$$4.74 = V_{GS} + 27000I_{DS} = 1 + \sqrt{\frac{2I_{DS}}{250 \times 10^{-6}}} + 27000I_{DS} \rightarrow I_{DS} = 104\mu\text{A}$$

$$V_{DS} = 18 - I_{DS}(75\text{k}\Omega + 27\text{k}\Omega) = 7.39\text{V} \quad | \quad \text{Saturation region is correct.}$$

$$g_m = \sqrt{2(250 \times 10^{-6})(104 \times 10^{-6})} = 0.228\text{mS}$$

$$v_{th} = v_s \frac{368\text{k}\Omega}{1\text{k}\Omega + 368\text{k}\Omega} = 0.997v_s \quad | \quad R_{th} = 1\text{k}\Omega \parallel 368\text{k}\Omega = 0.997\text{k}\Omega$$

$$R_L = r_o \parallel 75\text{k}\Omega \parallel 470\text{k}\Omega \approx 75\text{k}\Omega \parallel 470\text{k}\Omega = 64.7\text{k}\Omega \quad | \quad A_{vth} = -(0.228\text{mS})(64.7\text{k}\Omega) = -14.8$$

$$A_v = 0.997A_{vth} = -14.7 \quad | \quad A_i = 368\text{k}\Omega(-g_m) \frac{75\text{k}\Omega}{75\text{k}\Omega + 470\text{k}\Omega} = -11.6$$

$$R_{IN} = 368\text{k}\Omega \quad | \quad R_{OUT} = r_o \parallel 75\text{k}\Omega \approx 75\text{k}\Omega$$

$$v_{gs} = 0.997v_s \quad | \quad V_{GS} - V_{TN} = \sqrt{\frac{2(104\mu\text{A})}{250\mu\text{A}/V^2}} = 0.912\text{V} \quad | \quad v_s = 0.2 \frac{0.912\text{V}}{0.997} = 0.183\text{V}$$

$$A_v \approx -\frac{V_{DD}}{V_{GS} - V_{TN}} = -\frac{18}{0.912} = -19.7 \quad | \quad \text{The rule-of-thumb estimate assumes } V_{RL} = \frac{V_{DD}}{2}.$$

$$\text{We have } V_{RL} = 104\mu\text{A}(75\text{k}\Omega) = 7.80\text{V} = 0.433V_{DD}$$

The estimate also doesn't account for the presence of R_g .

14.15

$$V_{GS} = -(11\text{k}\Omega)I_{DS} = -(11\text{k}\Omega)(20\text{mA})\left(1 - \frac{V_{GS}}{-4}\right)^2 \rightarrow V_{GS} = -3.50\text{V}, \quad I_{DS} = -\frac{V_{GS}}{11\text{k}\Omega} = 318\mu\text{A}$$

$$V_{DS} = 20 - I_{DS}(11\text{k}\Omega + 39\text{k}\Omega) = 4.10\text{V} \quad | \quad \text{Saturation region is correct.}$$

$$g_m = \frac{2}{|-4|} \sqrt{20\text{mA}(318\mu\text{A})} = 1.26\text{mS} \quad | \quad v_{th} = v_s \frac{1\text{M}\Omega}{0.5\text{k}\Omega + 1\text{M}\Omega} = 1.00v_s$$

$$R_{th} = 0.5\text{k}\Omega \parallel 1\text{M}\Omega = 0.500\text{k}\Omega \quad | \quad R_L = 39\text{k}\Omega \parallel 500\text{k}\Omega = 36.2\text{k}\Omega$$

$$A_v = A_{vth} = -\frac{1.26\text{mS}(36.2\text{k}\Omega)}{1 + 1.26\text{mS}(11\text{k}\Omega)} = -3.07 \quad | \quad R_{IN} = 1.00\text{M}\Omega \quad | \quad R_{OUT} = 39\text{k}\Omega$$

$$A_i = -R_G \frac{g_m}{1 + g_m R_1} = -(10^6) \frac{1.26\text{mS}}{1 + 1.26\text{mS}(11\text{k}\Omega)} = -84.8$$

$$v_{th} = 1.00v_s \quad | \quad V_{GS} - V_P = -3.5 - (-4) = 0.500\text{V} \quad | \quad v_s = 0.2(0.5)[1 + 1.26\text{mS}(11\text{k}\Omega)] = 1.49\text{V}$$

14.21

$$V_{EQ} = 18 \frac{51k\Omega}{51k\Omega + 100k\Omega} = 6.08V \quad | \quad R_{EQ} = 51k\Omega \parallel 100k\Omega = 33.8k\Omega$$

$$I_B = \frac{(6.08 - 0.7 + 18)V}{33.8k\Omega + (126)(4.7k\Omega)} = 37.3\mu A \quad | \quad I_C = 4.67 \text{ mA} \quad | \quad V_{CE} = 36 - 2000I_C - 4700I_E = 4.54 \text{ V}$$

$$\text{Forward - active region is correct.} \quad | \quad r_{\pi} = \frac{125(0.025V)}{4.67\text{mA}} = 669\Omega \quad | \quad r_o = \frac{(50 + 4.54)V}{4.67\text{mA}} = 11.7k\Omega$$

$$v_{th} = v_s \frac{33.8\Omega}{500\Omega + 33.8k\Omega} = 0.985v_s \quad | \quad R_{th} = 33.8k\Omega \parallel 500\Omega = 493\Omega$$

$$R_L = 24k\Omega \parallel 4.7k\Omega \parallel 11.7k\Omega = 2.94k\Omega \quad | \quad A_{vth} = -\frac{126(2.94k\Omega)}{0.493k\Omega + 0.669k\Omega + 126(2.94k\Omega)} = 0.997$$

$$A_V = 0.985A_{vth} = 0.982 \quad | \quad R_{IN} = 33.8k\Omega \parallel [0.669k\Omega + 126(2.94k\Omega)] = 31.0k\Omega$$

$$A_1 = A_V \frac{R_S + R_{IN}}{R_3} = 0.982 \frac{0.5k\Omega + 31.0k\Omega}{24.0k\Omega} = 1.29 \quad | \quad R_{OUT} = \frac{493\Omega + 669\Omega}{126} \parallel 2.94k\Omega = 9.19 \Omega$$

$$v_{bc} = 0.982v_s \frac{0.669k\Omega}{0.493k\Omega + 0.669k\Omega + 126(2.94k\Omega)} = 0.00177v_s \quad | \quad v_s = \frac{5.00\text{mV}}{0.00177} = 2.83 \text{ V}$$

14.23

$$V_{GS} = 5V \quad | \quad I_{DS} = \frac{4 \times 10^{-4}}{2} (5 - 1)^2 = 3.2\text{mA} \quad | \quad V_{DS} = 5 - (-5) = 10V \quad - \text{ Saturation region}$$

$$\text{operation is correct.} \quad | \quad g_m = \sqrt{2(4 \times 10^{-4})(3.2\text{mA})[1 + 0.02(10)]} = 1.75\text{mS}$$

$$r_o = \frac{1}{3.2\text{mA}} + 10 = 18.8k\Omega \quad - \text{ Cannot neglect!} \quad | \quad R_L = 18.8k\Omega \parallel 100k\Omega = 15.8k\Omega$$

$$A_V = \frac{10^6}{10^6 + 10^4} \frac{1.75\text{mS}(15.8k\Omega)}{1 + 1.75\text{mS}(15.8k\Omega)} = 0.956 \quad | \quad A_1 = 10^6 \frac{1.75\text{mS}(15.8k\Omega)}{1 + 1.75\text{mS}(15.8k\Omega)} \frac{1}{10^5} = 9.56$$

$$R_{IN} = R_G = 1 \text{ M}\Omega \quad | \quad R_{OUT} = \frac{1}{g_m} \parallel r_o = 555 \Omega$$

$$v_{gs} = v_s \frac{10^6}{10^6 + 10^4} \frac{1}{1 + 1.75\text{mS}(15.8k\Omega)} = 0.0346v_s \quad | \quad v_s \leq \frac{0.2(5 - 1)}{0.0346} = 23.2 \text{ V} \quad \text{But,}$$

v_{DS} must exceed $v_{GS} - V_{TN} \equiv V_{GS} - V_{TN} = 4V$ for saturation.

$$V_{DS} = 10 - v_o = 10 - 0.956v_s \geq 4 \rightarrow v_s \leq 6.28 \text{ V} \quad - \text{ Limited by the Q - point voltages}$$