

Homework Assignment No. 8 - Solutions


15.9 Note that the dc equivalent circuits are identical for Q₁ and Q₂.

$$V_{EQ} = \frac{180\text{k}\Omega}{180\text{k}\Omega + 300\text{k}\Omega} 15\text{V} = 5.63\text{V} \quad | \quad R_{EQ} = 180\text{k}\Omega \parallel 300\text{k}\Omega = 113\text{ k}\Omega$$

$$I_B = \frac{5.63 - 0.7}{113 + 101(20)} \frac{\text{V}}{\text{k}\Omega} = 2.31\mu\text{A} \quad | \quad I_C = 100I_{B1} = 232\mu\text{A} \quad | \quad I_E = 101I_{B1} = 234\mu\text{A}$$

$$V_{CE} = 15 - 2 \times 10^4 I_E - 2 \times 10^4 I_C = 5.71\text{V}$$

$$r_{\pi} = \frac{100(0.025\text{V})}{232\mu\text{A}} = 10.8\text{k}\Omega \quad | \quad r_o = \frac{(70 + 5.71)\text{V}}{232\mu\text{A}} = 326\text{k}\Omega \quad - \text{Neglected}$$

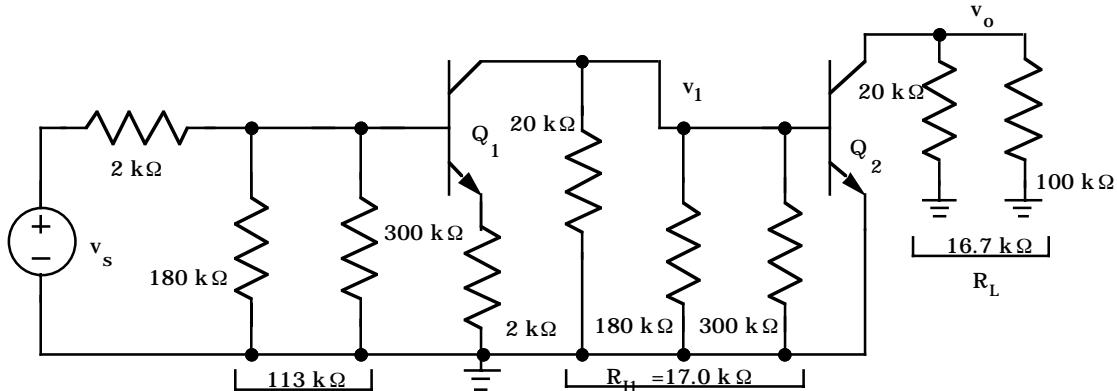

$$\mathbf{v_{th}} = \mathbf{v_s} \frac{113\text{k}\Omega}{113\text{k}\Omega + 2\text{k}\Omega} = 0.983\mathbf{v_s} \quad | \quad R_{th} = 113\text{k}\Omega \parallel 2\text{k}\Omega = 1.97\text{k}\Omega$$

$$\frac{\mathbf{v_1}}{\mathbf{v_s}} = -0.983 \frac{\beta_{o1}(R_{II} \parallel r_{\pi 2})}{R_{th} + r_{\pi 1} + (\beta_{o1} + 1)R_5} = -0.983 \frac{100(17\text{k}\Omega \parallel 10.8\text{k}\Omega)}{1.97\text{k}\Omega + 10.8\text{k}\Omega + (101)2\text{k}\Omega} = -3.02\mathbf{v_s}$$

$$\frac{\mathbf{v_o}}{\mathbf{v_1}} = -g_{m2}R_L \quad | \quad R_L = 100\text{k}\Omega \parallel 20\text{k}\Omega = 16.7\text{k}\Omega \quad | \quad \frac{\mathbf{v_o}}{\mathbf{v_1}} = -40(232\mu\text{A})(16.7\text{k}\Omega) = -154\mathbf{v_1}$$

$$A_v = \frac{\mathbf{v_o}}{\mathbf{v_s}} = (-3.02)(-154) = +465 \quad | \quad R_{OUT} = 20\text{k}\Omega \parallel r_{o2} \approx 20\text{k}\Omega$$

$$R_{IN} = R_{B1} \parallel (r_{\pi 1} + (\beta_{o1} + 1)R_5) = 113\text{k}\Omega \parallel [10.8\text{k}\Omega + (101)2\text{k}\Omega] = 73.8\text{k}\Omega$$

15.14


$$I_{C1} = 80 \frac{0.7 - (-9)}{100 + 81(24)} \frac{V}{k\Omega} = 325\mu A \quad | \quad V_{EQ2} = 9 - 9100I_{C1} = 6.04V \quad | \quad R_{EQ2} = 9.1k\Omega$$

$$I_{C2} = 80 \frac{9 - 0.7 - 6.04}{9.1 + 81(12)} \frac{V}{k\Omega} = 184\mu A \quad | \quad V_{C1} = 9 - 9.1k\Omega(I_{C1} - I_{B2}) = 6.06V$$

$$V_{E1} = -9 + I_{E1}(24k\Omega) = -1.10V \quad | \quad V_{CE1} = 6.06 - (-1.10) = 7.16V$$

$$V_{C2} = -9 + I_{C2}(43k\Omega) = -1.09V \quad | \quad V_{E2} = V_{C1} + 0.7 = 6.76V \quad | \quad V_{EC2} = 7.85V$$
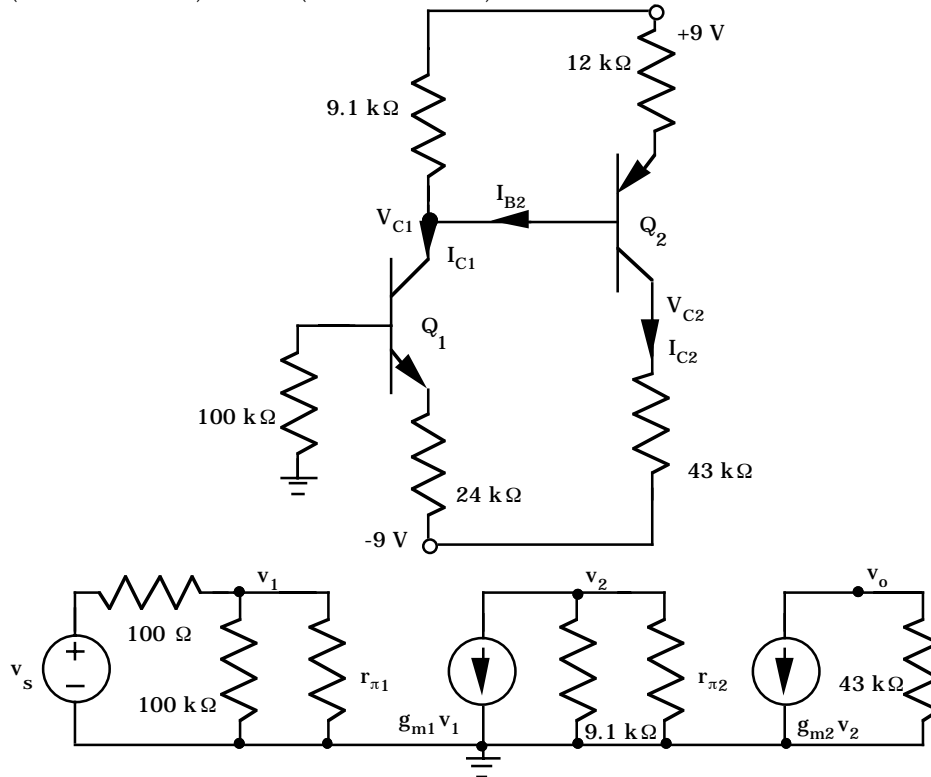
$$Q_1: (325\mu A, 7.16V) \quad Q_2: (184\mu A, 7.85V)$$



$$g_{m1} = 40(325\mu A) = 13.0mS \quad | \quad r_{\pi 1} = \frac{80}{13.0mS} = 6.15k\Omega$$

$$g_{m2} = 40(184\mu A) = 7.36mS \quad | \quad r_{\pi 2} = \frac{80}{7.36mS} = 10.9k\Omega$$


$$v_{th} = v_s \frac{100k\Omega}{100\Omega + 100k\Omega} = 0.999v_s \quad | \quad R_{th} = 100k\Omega \parallel 100\Omega = 99.9\Omega$$

$$v_o = -g_{m2}R_{C2}v_2 = -(7.36mS)(43k\Omega)v_2 = -317v_2$$

$$v_2 = -v_{th} \frac{80(R_{C1} \parallel r_{\pi 2})}{R_{th} + r_{\pi 1}} = -0.999v_s \frac{80(9.1k\Omega \parallel 10.9k\Omega)}{99.9\Omega + 6.15k\Omega} = -63.5v_s$$

$$A_v = \frac{v_o}{v_s} = -317(-63.5) = +2.01 \times 10^4 \quad \text{or} \quad 86.1 \text{ dB}$$

15.17 dc equivalent circuit:

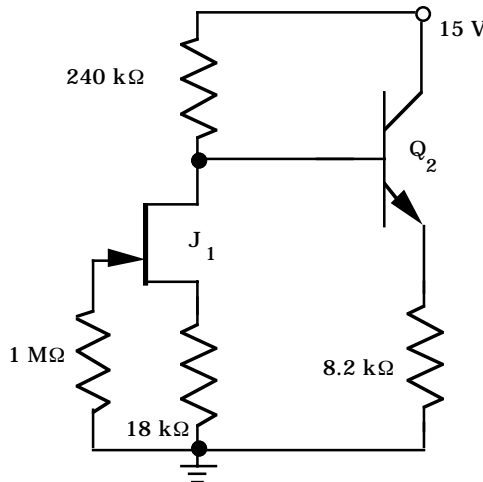

We assume saturation for J_1 and forward-active region operation for Q_2 .


$$I_{DS1} = I_{DSS} \left(1 - \frac{V_{GS1}}{V_P}\right)^2 \quad | \quad I_{DS1} = 0.005 \left(1 - \frac{-18000 I_{DS1}}{-1}\right)^2 \rightarrow I_{DS1} = 50 \mu\text{A}$$

$$V_{EQ2} = 15 - I_{DS1}(240\text{k}\Omega) = 3.00\text{V} \quad | \quad R_{EQ2} = 240\text{k}\Omega \quad | \quad I_{C2} = 100 \frac{3 - 0.7}{240 + 101(8.2)} \frac{\text{V}}{\text{k}\Omega} = 215 \mu\text{A}$$

$$V_{CE2} = 15 - 8200 I_{E2} = 13.2\text{V} \quad | \quad \text{Checking } V_{DS1}: V_{D1} = 15 - (50 + 2.15)(\mu\text{A})(240\text{k}\Omega) = 2.48\text{V}$$

$$V_{DS1} = 2.48 - (50\mu\text{A})(18\text{k}\Omega) = 1.58\text{V} \quad | \quad V_{GS1} - V_P = -(50\mu\text{A})(18\text{k}\Omega) + 1 = 0.1\text{V} \rightarrow M_1 \text{ is saturated.}$$

ac equivalent circuit:

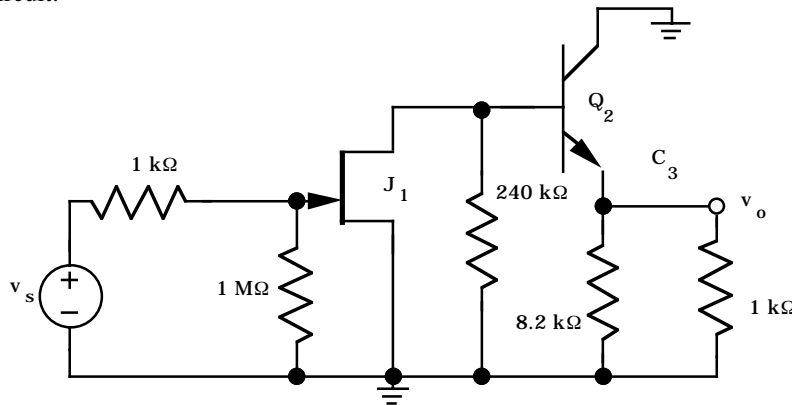

$$g_{m1} = \frac{2}{|-1|} \sqrt{(5\text{mA})50\mu\text{A}} = 1.00\text{mS} \quad | \quad r_{\pi 2} = \frac{100(0.025\text{V})}{215\mu\text{A}} = 11.6\text{k}\Omega$$

$$A_{V1} = \frac{\mathbf{v}_1}{\mathbf{v}_s} = -\frac{10^6}{10^6 + 10^3} g_{m1} R_{L1} = -\frac{10^6}{10^6 + 10^3} g \left[R_{D1} \parallel (r_{\pi 2} + (\beta_{o2} + 1)R_{L2}) \right]$$

$$R_{L2} = R_{E2} \parallel R_L = 8.2\text{k}\Omega \parallel 1\text{k}\Omega = 891\Omega \quad | \quad A_{V1} = (-1.00\text{mS}) \left[240\text{k}\Omega \parallel (11.6\text{k}\Omega + 101(891\Omega)) \right] = -71.4$$

$$A_{V2} = \frac{\mathbf{v}_o}{\mathbf{v}_1} = +\frac{101(0.891\text{k}\Omega)}{11.6\text{k}\Omega + 101(0.891\text{k}\Omega)} = 0.886 \quad | \quad A_V = -71.4(0.866) = -63.2 \quad | \quad R_{IN} = 1\text{M}\Omega$$

$$R_{OUT} = R_{E2} \parallel \left[\frac{R_{th2} + r_{\pi 2}}{\beta_{o2} + 1} \right] = 8.2\text{k}\Omega \parallel \left[\frac{240\text{k}\Omega + 11.6\text{k}\Omega}{101} \right] = 8.2\text{k}\Omega \parallel 2.49\text{k}\Omega = 1.91\text{k}\Omega$$

Note: R_{OUT} and A_V would be lower if r_{o1} were also included.

Problem 15.17 - Continued

$$(b) A_{V1} = \frac{\mathbf{v}_1}{\mathbf{v}_s} = -\frac{10^6}{10^6 + 10^3} \frac{g_{m1}R_{L1}}{1 + g_{m1}R_s}$$

$$A_{V1} = -0.999 \frac{(1.00\text{mS}) \left[240\text{k}\Omega \parallel (11.6\text{k}\Omega + 101(0.891\text{k}\Omega)) \right]}{1 + (1.00\text{mS})(18\text{k}\Omega)} = -3.75$$

$$A_{V2} = \frac{\mathbf{v}_o}{\mathbf{v}_1} = +\frac{101(0.891\text{k}\Omega)}{11.6\text{k}\Omega + 101(0.891\text{k}\Omega)} = 0.886 \quad | \quad A_V = -3.75(0.866) = -3.25$$

15.30

$$(a) I_C = \alpha_F I_E = \frac{1}{2} \frac{\beta_F}{\beta_F + 1} \frac{12 - V_{BE}}{R_{EE}} = \frac{1}{2} \frac{100}{101} \frac{12 - 0.7}{2.7 \times 10^5} = 20.7 \mu\text{A} \quad | \quad V_C = 12 - 3.3 \times 10^5 I_C = 5.17\text{V}$$

$$V_{CE} = V_C - (-0.7\text{V}) = 5.87\text{V} \quad | \quad Q\text{-Point} = (20.7\mu\text{A}, 5.87\text{V})$$

$$(b) A_{dd} = -g_m R_C = -40(20.7\mu\text{A})(330\text{k}\Omega) = -273$$

$$R_{ID} = 2r_\pi = 2 \frac{\beta_o V_T}{I_C} = 2 \frac{100(0.025\text{V})}{20.7\mu\text{A}} = 243 \text{ k}\Omega \quad | \quad R_{OD} = 2R_C = 660 \text{ k}\Omega$$

$$(c) A_{cc} = -\frac{\beta_o R_C}{r_\pi + (\beta_o + 1)2R_{EE}} = -\frac{100(330\text{k}\Omega)}{122\text{k}\Omega + 2(101)270\text{k}\Omega} = -0.604$$

$$A_{dd} = -\frac{g_m R_C}{2} = -137 \quad | \quad A_{cd} = A_{cc} \quad | \quad \text{CMRR} = \left| \frac{-137}{-0.604} \right| = 227$$

$$R_{IC} = \frac{r_\pi + (\beta_o + 1)2R_{EE}}{2} = \frac{122\text{k}\Omega + 2(101)270\text{k}\Omega}{2} = 27.3 \text{ M}\Omega$$

15.32

$$(a) I_E = \frac{1}{2} \frac{1.5 - 0.7 \text{ V}}{75 \times 10^3 \Omega} = 5.33\mu\text{A} \quad | \quad I_C = \alpha_F I_E = \frac{60}{61} I_E = 5.25\mu\text{A}$$

$$V_{CE} = 1.5 - 10^5 I_C - (-0.7) = 1.68\text{V} \quad | \quad Q\text{-Pt: } (5.25\mu\text{A}, 1.68\text{V})$$

$$(b) g_m = 40I_C = 0.210\text{mS} \quad | \quad r_\pi = \frac{60}{g_m} = 286\text{k}\Omega \quad | \quad A_{dd} = -g_m R_C = -0.210\text{mS}(100\text{k}\Omega) = -21.0$$

$$A_{cc} = -\frac{\beta_o R_C}{r_\pi + (\beta_o + 1)2R_{EE}} = -\frac{60(100\text{k}\Omega)}{286\text{k}\Omega + 61(150\text{k}\Omega)} = -0.636$$

$$\text{For differential output: CMRR} = \left| \frac{-21.0}{0} \right| = \infty$$

$$\text{For single-ended output: CMRR} = \left| \frac{-21.0}{-0.636} \right| = 16.5, \text{ a paltry } 24.4 \text{ dB!}$$

$$R_{ID} = 2r_\pi = 572\text{k}\Omega \quad | \quad R_{IC} = \frac{r_\pi + (\beta_o + 1)2R_{EE}}{2} = \frac{286 + 61(150)}{2} \text{ k}\Omega = 4.72 \text{ M}\Omega$$

$$R_{OD} = 2R_C = 200 \text{ k}\Omega \quad | \quad R_{OC} = \frac{R_C}{2} = 50\text{k}\Omega$$