

Homework Assignment No. 9 - Solution

17.1

$$A_V(s) = 25 \frac{s^2}{(s+1)(s+20)} \quad | \quad A_{mid} = 25 \quad | \quad F_L(s) = \frac{s^2}{(s+1)(s+20)} \quad | \quad \text{Poles: } -1, -20 \quad | \quad \text{Zeros: } 0, 0$$

$$\text{yes, } s = -20 \quad | \quad A_V(s) \approx 25 \frac{s}{(s+20)} \quad | \quad \omega_L = 20 \frac{\text{rad}}{s} \quad | \quad f_L = \frac{\omega_L}{2\pi} \approx \frac{20}{2\pi} = 3.18\text{Hz}$$

$$f_L = \frac{1}{2\pi} \sqrt{20^2 + 1^2 - 2(0)^2 - 2(0)^2} = 3.19\text{Hz}$$

$$|A_V(j\omega)| = \frac{25\omega^2}{\sqrt{\omega^2 + 1^2} \sqrt{\omega^2 + 20^2}} \quad | \quad \text{MATLAB: } -3.19 \text{ Hz}$$

17.4


$$A_V(s) = \frac{(2 \times 10^{11})(10^{-4})(10^{-5})}{\left(\frac{s}{10^4} + 1\right)\left(\frac{s}{10^5} + 1\right)} = \frac{200}{\left(\frac{s}{10^4} + 1\right)\left(\frac{s}{10^5} + 1\right)} \quad | \quad A_{mid} = 200 \quad | \quad F_H(s) = \frac{1}{\left(\frac{s}{10^4} + 1\right)\left(\frac{s}{10^5} + 1\right)}$$

$$\text{Poles: } -10^4, -10^5 \frac{\text{rad}}{s} \quad | \quad \text{Yes: } A_V(s) \approx \frac{200}{\frac{s}{10^4} + 1} \quad | \quad \omega_H \approx 10^4 \frac{\text{rad}}{s} \quad | \quad f_H \approx \frac{10^4}{2\pi} = 1.59\text{kHz}$$


$$f_H \approx \frac{1}{2\pi} \left(\sqrt{\left(\frac{1}{10^4}\right)^2 + \left(\frac{1}{10^5}\right)^2 - 2\left(\frac{1}{\infty}\right)^2 - 2\left(\frac{1}{\infty}\right)^2} \right)^{-1} = 1.58 \text{ kHz}$$

$$|A_V(j\omega)| = \frac{2 \times 10^{11}}{\sqrt{\omega^2 + (10^4)^2} \sqrt{\omega^2 + (10^5)^2}} \quad | \quad \text{MATLAB: } 1.58 \text{ kHz}$$

17.10

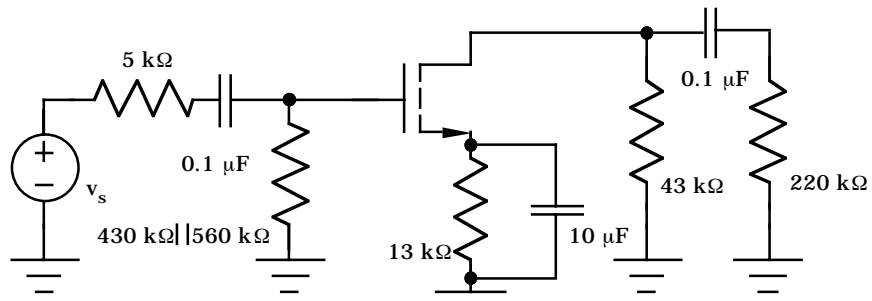

Low frequency:

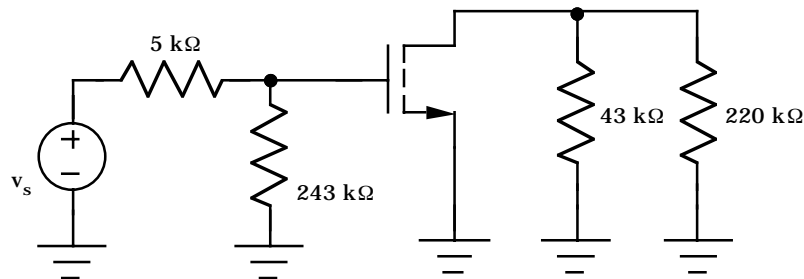

Mid-band:

17.10 - Continued

$$g_m = \frac{2I_{DS}}{V_{GS} - V_{TN}} = \frac{2(0.2\text{mA})}{1\text{V}} = 0.400\text{mS}$$


$$A_{\text{mid}} = -\frac{243\text{k}\Omega}{243\text{k}\Omega + 5\text{k}\Omega} (0.400\text{mS})(43\text{k}\Omega \parallel 220\text{k}\Omega) = -14.1$$

$$\omega_1 = \frac{1}{(10^{-7}\text{F})(243\text{k}\Omega + 5\text{k}\Omega)} = 40.3 \frac{\text{rad}}{\text{s}} \quad | \quad \omega_2 = \frac{1}{(10^{-7}\text{F})(43\text{k}\Omega + 220\text{k}\Omega)} = 38.0 \frac{\text{rad}}{\text{s}}$$

$$\omega_3 = \frac{1}{(10^{-5}\text{F})\left(13\text{k}\Omega \parallel \frac{1}{g_m}\right)} = \frac{1}{(10^{-5}\text{F})(13\text{k}\Omega \parallel 2.5\text{k}\Omega)} = 47.7 \frac{\text{rad}}{\text{s}} \quad | \quad \omega_z = \frac{1}{(10^{-5}\text{F})(13\text{k}\Omega)} = 7.69 \frac{\text{rad}}{\text{s}}$$

$$\text{Using Eq. (17.16): } f_L \approx \frac{1}{2\pi} \sqrt{(40.3)^2 + (38.0)^2 + (47.7)^2 - 2(7.69)^2} = 11.5 \text{ Hz}$$

17.16

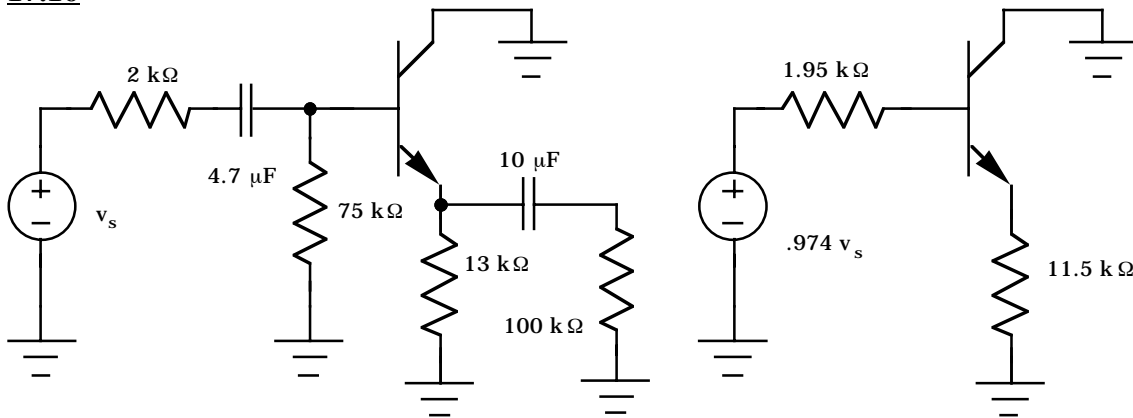

Low frequency

Mid-band

$$(b) \mathbf{v}_{\text{th}} = \frac{75\text{k}\Omega}{75\text{k}\Omega + 2\text{k}\Omega} \mathbf{v}_s = 0.974 \mathbf{v}_s \quad | \quad R_{\text{th}} = 75\text{k}\Omega \parallel 2\text{k}\Omega = 1.95\text{k}\Omega \quad | \quad R_L = 13\text{k}\Omega \parallel 100\text{k}\Omega = 11.5\text{k}\Omega$$

$$r_\pi = \frac{100}{40(0.25\text{mA})} = 10.0\text{k}\Omega \quad | \quad A_{\text{mid}} = 0.974 \frac{101(11.5\text{k}\Omega)}{[1.95 + 10.0 + 101(11.5)]\text{k}\Omega} = 0.964$$

$$R_{1S} = R_S + R_B \parallel [r_\pi + (\beta_o + 1)R_L] = 2\text{k}\Omega + 75\text{k}\Omega \parallel [10.0\text{k}\Omega + (101)11.5\text{k}\Omega] = 72.5\text{k}\Omega$$

$$\omega_1 = \frac{1}{(72.5\text{k}\Omega)4.7 \times 10^{-6}} = 2.94 \frac{\text{rad}}{\text{s}}$$

$$R_{3S} = R_7 + R_4 \parallel \frac{R_{\text{th}} + r_\pi}{(\beta_o + 1)} = 100\text{k}\Omega + 13\text{k}\Omega \parallel \frac{1.95\text{k}\Omega + 10.0\text{k}\Omega}{101} = 100\text{k}\Omega$$

$$\omega_3 = \frac{1}{10^{-5}(10^5)} = 1 \frac{\text{rad}}{\text{s}} \quad f_L \approx \frac{(2.94 + 1)}{2\pi} = 0.627\text{Hz}$$


Problem 5

a.) If the g_m of the MOSFET is 0.1mA/V , find the midband gain and the location of all zeros and poles of the circuit shown.

b.) If the amplifier above has two zeros at the origin and a pole at -1 rads/sec and -4 rads/sec. , what is the lower -3dB frequency in Hz?

Solution

1.) Small-signal model:

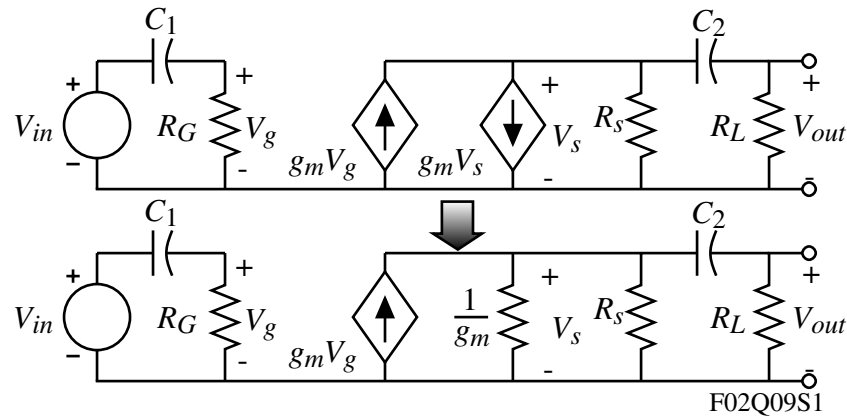

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \left(\frac{g_m (1/g_m) \parallel R_s}{(1/g_m) \parallel R_s + R_L + \frac{1}{sC_2}} \times R_L \right) \left(\frac{R_G}{R_G + \frac{1}{sC_2}} \right) = \left(\frac{5\text{k}}{15\text{k} + \frac{1}{sC_2}} \right) \left(\frac{1\text{M}}{1\text{M} + \frac{1}{sC_1}} \right) \\ &= \left(\frac{1}{3} \right) \left(\frac{s}{s + \frac{1}{15\text{k} C_2}} \right) \left(\frac{s}{s + \frac{1}{1\text{M} C_1}} \right) = \left(\frac{1}{3} \right) \left(\frac{s}{s + 6.67} \right) \left(\frac{s}{s + 1} \right) \end{aligned}$$

\therefore $\text{MGB} = \underline{0.333}$, two zeros at $\underline{0\text{ rads/sec.}}$ and poles at $\underline{-1\text{ rad/sec}}$ and $\underline{-6.67\text{ rads/sec.}}$

$$2.) \omega_L \approx \sqrt{p_1^2 + p_2^2 - 2(z_1^2 + z_2^2)} = \sqrt{1^2 + 4^2 - 2(0)} = \sqrt{17} = 4.123\text{ rads/sec.}$$

$$\therefore f_L = \frac{4.123}{6.28} = \underline{0.656\text{ Hz}}$$