
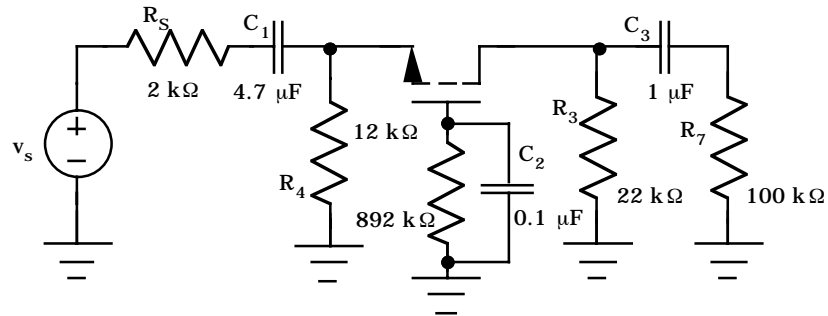


**Homework Assignment No. 10 - Solutions**

1.) Problem 17.14 of the text.

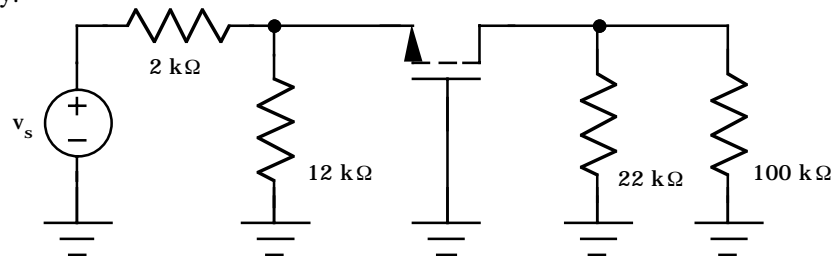

Low Frequency:



Mid-band:

$$g_m = \frac{2(0.1\text{mA})}{1\text{V}} = 0.200\text{mS} \quad \left| \quad \frac{1}{g_m} = 5000\Omega \quad \left| \quad v_{th} = \frac{12\text{k}\Omega}{12\text{k}\Omega + 2\text{k}\Omega} v_s = 0.857 v_s \right.$$

$$R_{th} = 12\text{k}\Omega \parallel 2\text{k}\Omega = 1.71\text{k}\Omega \quad \left| \quad R_L = 22\text{k}\Omega \parallel 100\text{k}\Omega = 18.0\text{k}\Omega$$

$$A_{mid} = 0.857 \frac{R_L}{R_{th} + \frac{1}{g_m}} = 0.857 \frac{18.0\text{k}\Omega}{1.71\text{k}\Omega + 5\text{k}\Omega} = 2.30 \quad (7.24\text{dB})$$

$$\omega_1 = \frac{1}{4.7 \times 10^{-6} (2\text{k}\Omega + 12\text{k}\Omega \parallel 5\text{k}\Omega)} = 38.5 \frac{\text{rad}}{\text{s}} \quad \left| \quad \omega_2 = \text{doesn't matter since } i_g = 0! \right.$$

$$\omega_3 = \frac{1}{10^{-7} (100\text{k}\Omega + 22\text{k}\Omega)} = 82.0 \frac{\text{rad}}{\text{s}} \quad \left| \quad f_L \approx \frac{1}{2\pi} (38.5 + 82.0) = 19.2\text{Hz} \right.$$

2.) Problem 17.17 of the text.

$$\text{SCTC requires: } \omega_L \approx \sum_{i=1}^3 \frac{1}{R_{is} C_i} = 2\pi(500) = 3140 \frac{\text{rad}}{\text{s}}$$


$$\omega_1 = \frac{1}{(10^{-7}\text{F})(2.43\text{M}\Omega + 1\text{k}\Omega)} = 4.11 \frac{\text{rad}}{\text{s}} \quad \left| \quad \omega_2 = \frac{1}{(10^{-7}\text{F})(43\text{k}\Omega + 1\text{M}\Omega)} = 9.59 \frac{\text{rad}}{\text{s}} \right.$$

$$\omega_1 + \omega_2 \ll \omega_L \quad \left| \quad \omega_3 \text{ will be dominant} \rightarrow \omega_3 \approx \omega_L \right.$$

$$\omega_3 = \frac{1}{C_3 \left( R_4 \parallel \frac{1}{g_m} \right)} \quad \left| \quad g_m = \frac{2I_{DS}}{V_{GS} - V_{TN}} = \frac{2(0.2\text{mA})}{1\text{V}} = 0.400\text{mS} \quad \left| \quad \frac{1}{g_m} = 2.50\text{k}\Omega \right.$$

$$C_3 = \frac{1}{3140(13\text{k}\Omega \parallel 2.5\text{k}\Omega)} = 0.152 \mu\text{F} \rightarrow 0.15 \mu\text{F} \text{ from Appendix C}$$

3.) Problem 17.41 of the text.

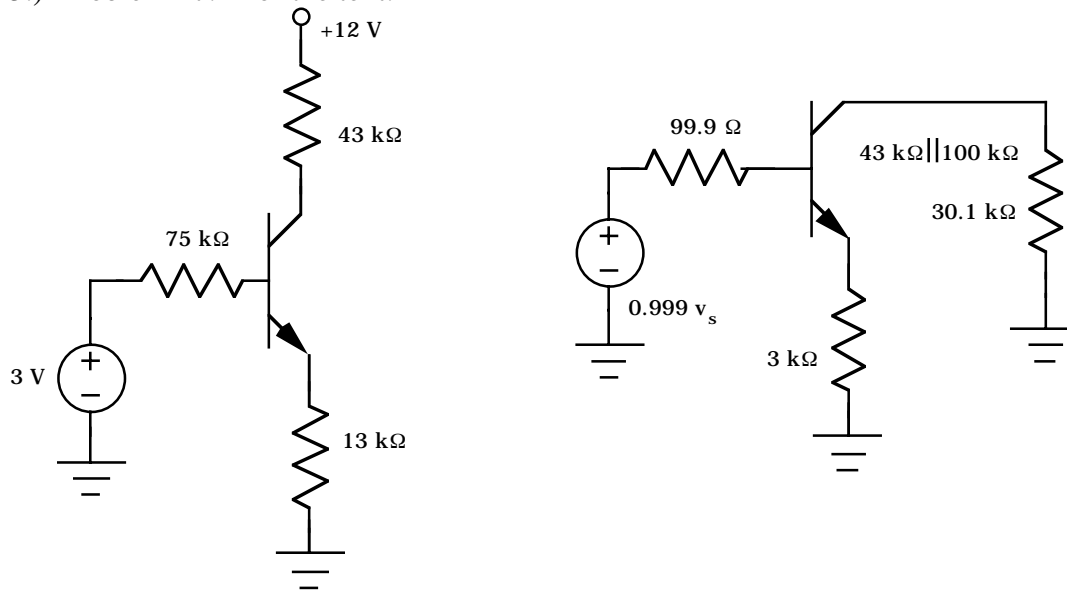

$$I_B = \frac{3 - 0.7}{75\text{k}\Omega + 101(13\text{k}\Omega)} = 1.657\mu\text{A} \quad | \quad I_C = 166\mu\text{A} \quad | \quad V_{CE} = 12 - 43\text{k}\Omega(I_C) - 13\text{k}\Omega\left(\frac{I_C}{\alpha_F}\right) = 2.70\text{V}$$

$$2.70\text{V} \geq 0.7\text{V} \quad \text{Forward - active region is correct.} \quad | \quad r_\pi = \frac{100(0.025)}{0.166 \text{ mA}} = 15.1 \text{ k}\Omega$$

$$g_m = 40(0.166 \text{ mA}) = 6.63\text{mS} \quad | \quad C_\pi = \frac{6.63\text{mS}}{2\pi(3 \times 10^8)} - 0.5 = 3.02 \text{ pF} \quad | \quad r_x = 300\Omega \quad | \quad C_\mu = 0.5\text{pF}$$

$$\mathbf{v}_{th} = \frac{75\text{k}\Omega}{75\text{k}\Omega + 100\Omega} \mathbf{v}_s = 0.999\mathbf{v}_s \quad | \quad R_{th} = 75\text{k}\Omega \parallel 100\Omega = 99.9\Omega \quad | \quad R_L = 43\text{k}\Omega \parallel 100\text{k}\Omega = 30.1\text{k}\Omega$$

$$A_{mid} = 0.999 \frac{-100(30.1\text{k}\Omega)}{99.9\Omega + 300\Omega + 15.1\text{k}\Omega + 101(3\text{k}\Omega)} = -9.44$$

Short-Circuit Time Constants

$$R_{1S} = 100\Omega + 75\text{k}\Omega \parallel \left[ 300\Omega + 15.1\text{k}\Omega + 101(3\text{k}\Omega) \right] = 60.8\text{k}\Omega$$

$$R_{2S} = 43\text{k}\Omega + 100\text{k}\Omega = 143\text{k}\Omega$$

$$R_{3S} = 10\text{k}\Omega \parallel \left( 3\text{k}\Omega + \frac{15.1\text{k}\Omega + 99.9\Omega}{101} \right) = 2.40\text{k}\Omega$$

$$f_L \approx \frac{1}{2\pi} \left[ \frac{1}{(60.8\text{k}\Omega)(1\mu\text{F})} + \frac{1}{(143\text{k}\Omega)(0.1\mu\text{F})} + \frac{1}{(2.40\text{k}\Omega)(2.2\mu\text{F})} \right] = 43.9\text{Hz}$$


Open-Circuit Time Constants

Using the result in Table 17.2 on page 944:  $R_{th} + r_x = 99.9\Omega + 300\Omega = 400\Omega$ 

$$C_{TB} = \frac{3.02\text{pF}}{1 + (6.63\text{mS})(3\text{k}\Omega)} \left( 1 + \frac{3\text{k}\Omega}{400\Omega} \right) + 0.5\text{pF} \left[ 1 + \frac{(6.63\text{mS})(30.1\text{k}\Omega)}{1 + (6.63\text{mS})(3\text{k}\Omega)} + \frac{30.1\text{k}\Omega}{400\Omega} \right]$$

$$C_{TB} = 44.1\text{pF} \quad f_H = \frac{1}{2\pi(400\Omega)(44.1\text{pF})} = 9.02 \text{ MHz}$$

4.) Problem 17.48 of the text.

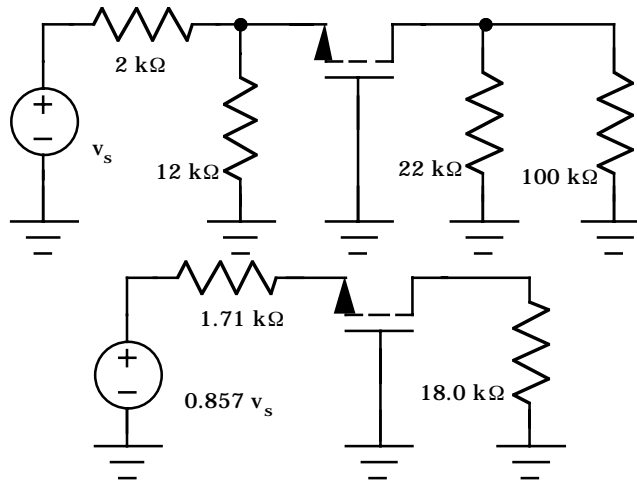

$$\mathbf{v_{th}} = \frac{12\text{k}\Omega}{12\text{k}\Omega + 2\text{k}\Omega} \mathbf{v_s} = 0.857 \mathbf{v_s} \quad | \quad \mathbf{R_{th}} = 12\text{k}\Omega \parallel 2\text{k}\Omega = 1.71\text{k}\Omega \quad | \quad \mathbf{R_L} = 22\text{k}\Omega \parallel 100\text{k}\Omega = 18.0\text{k}\Omega$$

$$\mathbf{g_m} = \frac{2(0.1\text{mA})}{1\text{V}} = 0.2\text{mS} \quad | \quad \mathbf{C_{GS}} = 3.0\text{pF} \quad | \quad \mathbf{C_{GD}} = 0.6\text{pF}$$

$$\mathbf{A_{mid}} = 0.857 \frac{\mathbf{R_L}}{\mathbf{R_{th}} + \frac{1}{\mathbf{g_m}}} = 0.857 \frac{18.0\text{k}\Omega}{1.71\text{k}\Omega + \frac{1}{0.2\text{mS}}} = +2.30$$


$$\mathbf{f_H} = \frac{1}{2\pi} \left( \frac{1}{\frac{\mathbf{C_{GS}}}{\mathbf{G_{th}} + \mathbf{g_m}} + \mathbf{C_{GD}R_L}} \right) = \frac{1}{2\pi} \left( \frac{1}{\frac{3.0\text{pF}}{(0.5848 + 0.2)\text{mS}} + 0.6\text{pF}(18.0\text{k}\Omega)} \right) = 10.9 \text{ MHz}$$


---

5.) A BJT transistor amplifier is shown. If  $g_m = 100\text{mA/V}$ ,  $r_{\pi} = 1\text{k}\Omega$ ,  $C_{\pi} = 20\text{pF}$ , and  $C_{\mu} = 1\text{pF}$ , find numerical values for the midband gain (MBG) and the upper -3dB frequency ( $\omega_H$ ).

Solution

Midband gain: Small signal model-

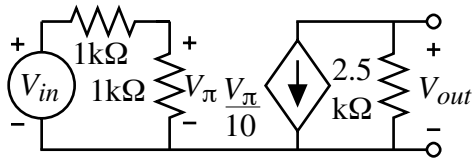

$$\text{MGB} = (0.5) \left( \frac{-2500}{10} \right) = -125 \text{ V/V}$$

High frequency response:

1.) Use the Miller approach.

$$\frac{V_o}{V_{in}} = -g_m(2.5\text{k}\Omega) = -250$$

$$C_{eq} = C_{\mu} + (251)C_{\pi} = 20\text{pf} + 251 \cdot 1\text{pF} = 271\text{pF} \quad \text{and} \quad R_{eq} = 1\text{K} \parallel 1\text{K} = 500\Omega$$

$$\therefore \omega_H = \frac{1}{500 \cdot 271\text{pF}} = 7.38 \times 10^6 \text{ rads/sec} \Rightarrow f_H = 1.175 \text{ MHz}$$

2.) Open-Circuit Time Constant Approach.

$$R_{C\pi} = R_s \parallel r_{\pi} = 500\Omega$$

$R_{C\mu} = ?$  See model.

$$\begin{aligned} v_t &= V_{\pi} + (i_t + g_m V_{\pi}) 2.5\text{k}\Omega \\ &= V_{\pi} (1 + g_m 2.5\text{k}\Omega) + i_t 2.5\text{k}\Omega \\ &= i_t (R_s \parallel r_{\pi}) (1 + g_m 2.5\text{k}\Omega) + i_t 2.5\text{k}\Omega \end{aligned}$$

$$\therefore R_{C\mu} = \frac{v_t}{i_t} = 0.5\text{k}\Omega(251) + 2.5\text{k}\Omega = 128\text{k}\Omega$$

$$\omega_H = \frac{1}{R_{C\pi} C_{\pi} + R_{C\mu} C_{\mu}} = \frac{10^9}{0.5 \times 20 + 128 \times 1} = 7.246 \times 10^6 \text{ rads/sec.} \Rightarrow f_H = 1.15 \text{ MHz}$$

The open-circuit time constant approach agrees reasonably well with the Miller approach.

