

Homework Assignment No. 10Due on Wednesday, March 26, 2003

- 1.) Problem 17.14 of the text. ($V_{DD} = 12V$)
- 2.) Problem 17.17 of the text.
- 3.) Problem 17.41 of the text.
- 4.) Problem 17.48 of the text.
- 5.) A BJT transistor amplifier is shown. If $g_m = 100\text{mA/V}$, $r_e = 1\text{k}\Omega$, $C_v = 1\text{pF}$, and $C_a = 20\text{pF}$, find numerical values for the midband gain (MBG) and the upper -3dB frequency (ω_H).

