

Homework Assignment No. 13 - Solutions



Problem 1

Use the method of feedback analysis to find v_2/v_1 , $R_{in} = v_1/i_1$, and $R_{out} = v_2/i_2$. Assume that all transistors are matched and that $g_{m1} = g_{m2} = 1\text{mS}$. Neglect r_{ds} .

Solution

The topology is series-series.

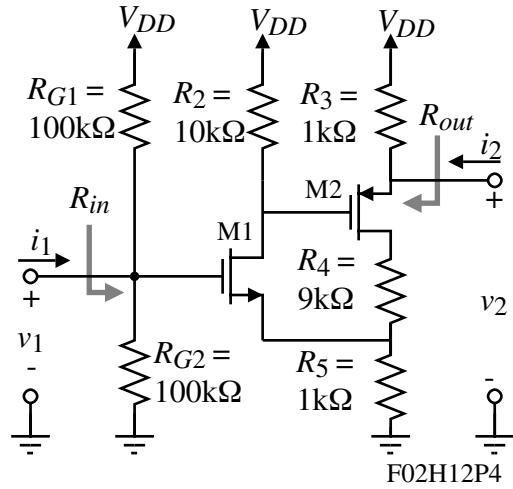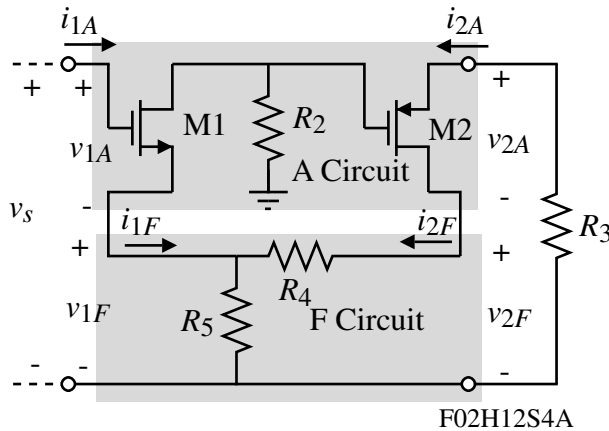The circuit is redrawn below in order to help identify the various terms for the analysis:




$$z_{11F} = \left. \frac{v_{1F}}{i_{1F}} \right|_{i_{2F}=0} = R_5 = 1\text{k}\Omega$$

$$z_{22F} = \left. \frac{v_{2F}}{i_{2F}} \right|_{i_{1F}=0} = R_4 + R_5 = 10\text{k}\Omega$$

$$z_{12F} = \beta = \left. \frac{v_{1F}}{i_{2F}} \right|_{i_{1F}=0} = R_5 = 1\text{k}\Omega$$

Calculation of the A circuit:

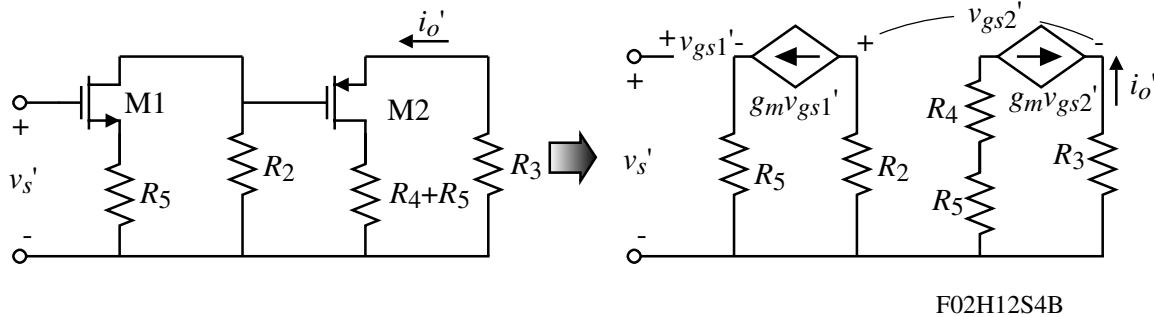

$$A = \frac{i_o'}{v_s'} = \left(\frac{i_o'}{v_{gs2'}} \right) \left(\frac{v_{gs2'}}{v_{gs1'}} \right) \left(\frac{v_{gs1'}}{v_s'} \right) = (-g_m) \left(\frac{-g_m R_2}{1 + g_m R_3} \right) \left(\frac{1}{1 + g_m R_5} \right) = (10^{-3})(-5)(-0.5) = 2.5 \text{ mS}$$

$$\therefore \frac{i_o}{v_s} = \frac{A}{1 + A\beta} = \frac{2.5\text{mS}}{1 + 2.5} = 0.714\text{mS}$$

Since, $z_{11A} = \infty$, then $R_{in} = 50\text{k}\Omega \parallel \infty = \underline{50\text{k}\Omega}$

$$\frac{v_2}{v_1} = \frac{-i_o R_3}{v_s} = \frac{-i_o}{v_s} R_3 = -0.714\text{mS}(1\text{k}\Omega) = \underline{-0.714 \text{ V/V}}$$


$$R_o = (z_{22T} + R_3)(1 + A\beta) = \left(\frac{1}{g_m} + R_3 \right) (1 + A\beta) = 2\text{k}\Omega(3.5) = 7\text{k}\Omega$$

However, the output resistance specified by the problem, R_{out} , is found as

$$R_{out} = (R_o - R_3) \parallel R_3 = 6\text{k}\Omega \parallel 1\text{k}\Omega = \underline{857\Omega}$$

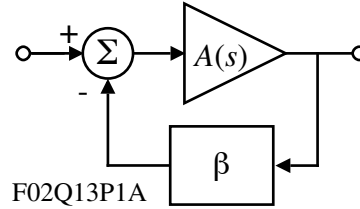2.) The amplifier in the feedback circuit shown has a transfer function of

$$A(s) = \frac{100}{\frac{s}{10^5} + 1}$$



What value of β will increase the upper -3dB frequency by a factor of 10 for the closed loop gain? What is the closed loop, low frequency gain?

Solution


$$A_F = \frac{A}{1+A\beta} = \frac{1}{\frac{1}{A} + \beta} = \frac{1}{\frac{s/10^5 + 1}{100} + \beta} = \frac{100}{\frac{s}{10^5} + 1 + 100\beta} = \left(\frac{100}{1+100\beta}\right) \frac{1}{\frac{s}{10^5(1+100\beta)} + 1}$$

$$\therefore 10^5(1+100\beta) = 10^6 \quad \rightarrow \quad 1+100\beta = 10 \quad \rightarrow \quad \underline{\underline{\beta = 9/100 = 0.09}}$$

The closed-loop, low frequency gain is,


$$A_F(0) = \frac{100}{1+100\beta} = \frac{100}{1+9} = 10 \quad \rightarrow \quad \underline{\underline{A_F(0) = 10}}$$

3.) Problem 18.30 of the text.

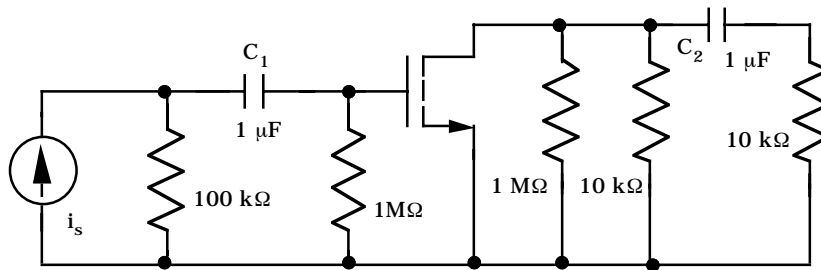

$$\omega_1 = \frac{1}{10^{-6}(100\text{k}\Omega + 1\text{M}\Omega)} = 0.909 \frac{\text{rad}}{\text{s}} \quad | \quad \omega_2 = \frac{1}{10^{-6}(10\text{k}\Omega + 25\text{k}\Omega \parallel 10\text{k}\Omega \parallel 1\text{M}\Omega)} = 58.5 \frac{\text{rad}}{\text{s}}$$

$$\text{Separate widely spaced poles} \rightarrow f_L^A = f_2 = \frac{58.5}{2\pi} = 9.31 \text{ Hz}$$

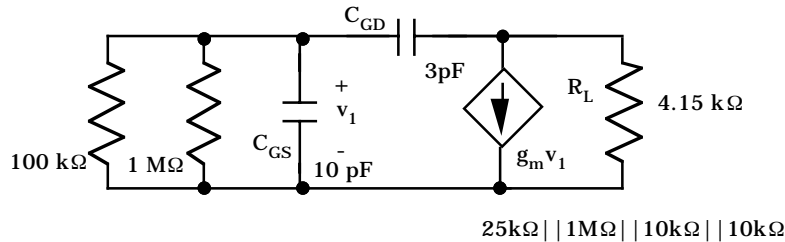

Problem 18.30 - Continued

$$\omega_H^A = \frac{1}{r_{\pi o} C_T} = \frac{1}{(100\text{k}\Omega \parallel 1\text{M}\Omega) \left[10\text{pF} + 3\text{pF} \left(1 + 2\text{mS}(4.15\text{k}\Omega) + \frac{4.15\text{k}\Omega}{100\text{k}\Omega \parallel 1\text{M}\Omega} \right) \right]}$$

$$f_H^A = \frac{1}{2\pi} \frac{1}{(90.9\text{k}\Omega)(38.0\text{pF})} = 46.1 \text{ kHz}$$

$$\mathbf{v}_{gs} = \mathbf{i}_s (100\text{k}\Omega \parallel 1\text{M}\Omega) = (90.9\text{k}\Omega) \mathbf{i}_s \quad | \quad \mathbf{v}_o = -(2 \times 10^{-3}) \mathbf{v}_{gs} (25\text{k}\Omega \parallel 10\text{k}\Omega \parallel 10\text{k}\Omega \parallel 1\text{M}\Omega)$$

$$A = \frac{\mathbf{v}_o}{\mathbf{i}_s} = -(2\text{mS})(4.15\text{k}\Omega)(90.9\text{k}\Omega) = -7.55 \times 10^5 \Omega \quad | \quad y_{12}^F = -10^{-5} \text{ S}$$

$$1 + A\beta = 1 + (-7.55 \times 10^5 \Omega)(-10^{-6} \text{ S}) = 1.76$$

$$f_L = \frac{9.31}{1.76} = 5.29 \text{ Hz} \quad f_H = 46.1\text{kHz}(1.76) = 81.0 \text{ kHz}$$

4.) Problem 18.32 of the text.

$$(a) \quad A(s) = \frac{2 \times 10^{14} \pi^2}{(2\pi \times 10^3)(2\pi \times 10^5)} = \frac{5 \times 10^5}{\left(1 + \frac{s}{2\pi \times 10^3}\right) \left(1 + \frac{s}{2\pi \times 10^5}\right)} = \frac{5 \times 10^5}{\left(1 + \frac{s}{2\pi \times 10^3}\right) \left(1 + \frac{s}{2\pi \times 10^5}\right)}$$

A(s) represents a low - pass amplifier with two widely - spaced poles

Open - loop: $A_o = 5 \times 10^5 = 114\text{dB}$ | $f_L = 0$ | $f_H \approx f_1 = 1000 \text{ Hz}$

(b) A common mistake would be the following:

Closed - loop: $f_H = 1000\text{Hz} \left[1 + 5 \times 10^5 (0.01) \right] = 5\text{MHz}$


Oops! - This exceeds $f_2 = 100 \text{ kHz}$! This is a two - pole amplifier.

$$A_V(s) = \frac{2 \times 10^{14} \pi^2}{(s + 2\pi \times 10^3)(s + 2\pi \times 10^5)} = \frac{2 \times 10^{14} \pi^2}{1 + \frac{2 \times 10^{14} \pi^2}{(s + 2\pi \times 10^3)(s + 2\pi \times 10^5)} (0.01)} = \frac{2 \times 10^{14} \pi^2}{s^2 + 1.01(2\pi \times 10^5)s + 2 \times 10^{12} \pi^2}$$

Using dominant - root factorization: $f_1 = 101 \text{ kHz}$, $f_2 = 4.95 \text{ MHz}$

So the closed - loop values are $f_H = 101 \text{ kHz}$ and $f_L = 0$.

5.) Problem 18.35 of the text.

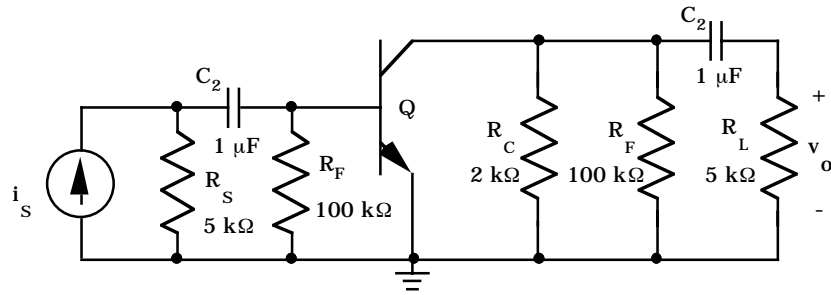

From the Exercise: $g_m = 40.3 \text{ mS}$ | $r_\pi = 3.72 \text{ k}\Omega$ | $r_o = 50.8 \text{ k}\Omega$ | $1 + A\beta = 2.19$

$$r_{o2} = \frac{50 + 1.4}{10^{-4}} = 514 \text{ k}\Omega \quad | \quad r_{o4} = \frac{50 + 11.3}{10^{-4}} = 613 \text{ k}\Omega \quad | \quad r_{\pi5} = \frac{100(0.025)}{0.0012} = 2.08 \text{ k}\Omega$$


$$C_{\pi1} = \frac{40.3 \text{ mS}}{2\pi(500 \text{ MHz})} - 0.75 \text{ pF} = 12.1 \text{ pF}$$

Using the open - circuit time constant approach with $C_1 = C_2 = 1 \mu\text{F}$:

$$R_{1O} = 5 \text{ k}\Omega + 100 \text{ k}\Omega \parallel r_\pi \parallel 5 \text{ k}\Omega + 100 \text{ k}\Omega \parallel 3.72 \text{ k}\Omega = 8.59 \text{ k}\Omega$$

$$R_{2O} = 5 \text{ k}\Omega + 50.8 \text{ k}\Omega \parallel 2 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 6.89 \text{ k}\Omega$$

$$f_L = \frac{1}{2\pi} \left[\frac{1}{1\mu\text{F}(8.59 \text{ k}\Omega)} + \frac{1}{1\mu\text{F}(6.89 \text{ k}\Omega)} \right] = 41.6 \text{ Hz} \quad | \quad f_L^F = \frac{f_L}{1 + A\beta} = 19.0 \text{ Hz}$$

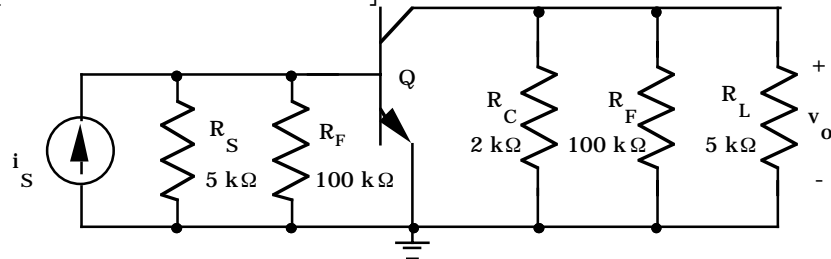

$$r_{\pi o} = 3.72 \text{ k}\Omega \parallel 100 \text{ k}\Omega \parallel 5 \text{ k}\Omega = 2.09 \text{ k}\Omega \quad | \quad R_L = 50.8 \text{ k}\Omega \parallel 2 \text{ k}\Omega \parallel 100 \text{ k}\Omega \parallel 5 \text{ k}\Omega = 1.37 \text{ k}\Omega$$

$$C_T = 12.1 \text{ pF} + 0.75 \text{ pf} \left[1 + 40.3 \text{ mS}(1.37 \text{ k}\Omega) + \frac{1.37 \text{ k}\Omega}{2.09 \text{ k}\Omega} \right] = 54.8 \text{ pF}$$

$$f_H = \frac{1}{2\pi r_{\pi o} C_T} = \frac{1}{2\pi(1.37 \text{ k}\Omega)(54.8 \text{ pF})} = 1.39 \text{ MHz} \quad | \quad f_H^F = f_H(1 + A\beta) = 3.04 \text{ MHz}$$