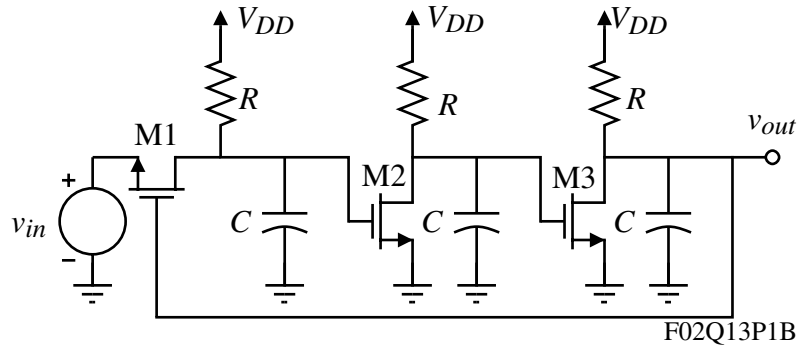



Homework Assignment No. 14 - Solution

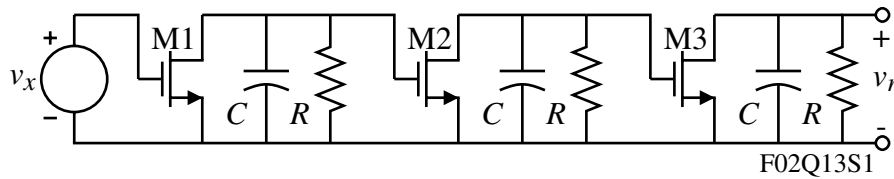1.) Find the loop gain of the amplifier shown. Assume that $g_m = 1\text{mS}$ and $r_{ds} = \infty$ for all MOSFETs and that $R = 10\text{k}\Omega$ and $C = 100\text{nF}$.



Solution

Use the model shown to find the loop gain.



This circuit consists of three identical stages with each transfer function given as

$$A(s) = \frac{-g_m R}{sRC + 1}$$

Therefore,

$$T(s) = -\frac{v_r}{v_x} = -\left(\frac{-g_m R}{sRC + 1}\right)^3 = -\left(\frac{-10}{\frac{s}{10^3} + 1}\right)^3 = \frac{1000}{\left(\frac{s}{10^3} + 1\right)^3} \rightarrow \boxed{T(s) = \frac{1000}{\left(\frac{s}{10^3} + 1\right)^3}}$$

2.) Problem 18.49 of the text.

(a) $T = A\beta = \frac{2 \times 10^{14} \pi^2}{(s + 2 \times 10^3 \pi)(s + 2 \times 10^5 \pi)} \left(\frac{1}{5}\right)$ | Yes, it is a second - order system and will

have some phase margin, although Φ_M may be vanishingly small.

(b) For $\omega \gg 2\pi \times 10^5$, $|T(j\omega)| \approx \frac{4 \times 10^{13} \pi^2}{\omega^2}$ and $|T(j\omega)| = 1$ for $\omega = 1.987 \times 10^7 \frac{\text{rad}}{\text{s}}$

$\angle T(j.987 \times 10^7) = -\tan^{-1} \frac{1.987 \times 10^7}{2000\pi} - \tan^{-1} \frac{1.987 \times 10^7}{2 \times 10^5 \pi} = 178.2^\circ \rightarrow \Phi_M = 1.83^\circ$ | A very small phase margin.

3.) Problem 18.61 of the text.


$$A_{V1} = \frac{\mathbf{V}_{o1}}{\mathbf{V}_{o2}} = -\frac{1}{sRC} \quad \mathbf{V}_{o2} = \left(1 + \frac{2R}{2R}\right) \mathbf{V}_+ = 2\mathbf{V}_+$$

$$(\mathbf{V}_+ - \mathbf{V}_{o1}) \frac{G}{2} + sC\mathbf{V}_+ + (\mathbf{V}_+ - \mathbf{V}_{o2})G_F = 0 \quad \text{Combining these yields}$$

$$A_{V2} = \frac{\mathbf{V}_{o2}}{\mathbf{V}_{o1}} = \frac{G}{sC + \left(\frac{G}{2} - G_F\right)} \quad \text{and} \quad T(s) = A_{V1}A_{V2} = \frac{1}{sRC \left(sRC + \frac{1}{2} - \frac{R}{R_F}\right)}$$

$$\angle T(j\omega_o) = 0 \rightarrow R_F = 2R \quad \text{and} \quad |T(j\omega_o)| = 1 \rightarrow \omega_o = \frac{1}{RC}$$

4.) Problem 18.70 of the text.

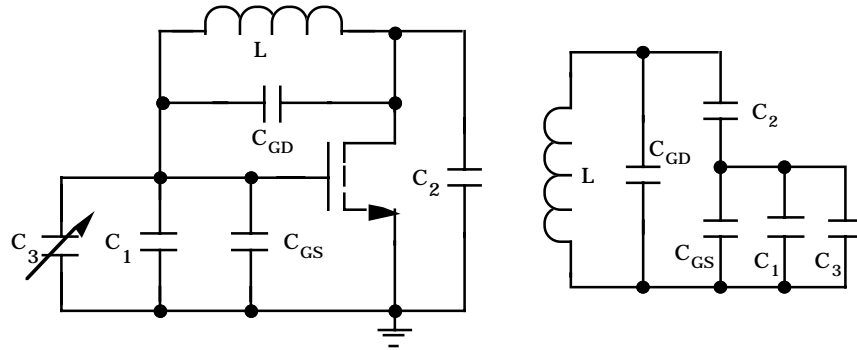

$$C_{TC} = C_{GD} + \frac{1}{\frac{1}{C_2} + \frac{1}{C_1 + C_3 + C_{GS}}} = 4\text{pF} + \frac{1}{\frac{1}{50\text{pF}} + \frac{1}{50\text{pF} + 0 + 10\text{pF}}} = 31.27\text{pF}$$

$$f_o = \frac{1}{2\pi\sqrt{LC_{TC}}} = \frac{1}{2\pi\sqrt{(10^{-5}\text{H})(31.27 \times 10^{-12}\text{F})}} = 9.00\text{MHz}$$

$$g_m r_o \geq \frac{C_1 + C_3 + C_{GS}}{C_2} = \frac{50\text{pF} + 0 + 10\text{pF}}{50\text{pF}} = 1.20 \text{ which is easily met.}$$

5.) Problem 12,123 of the text.

