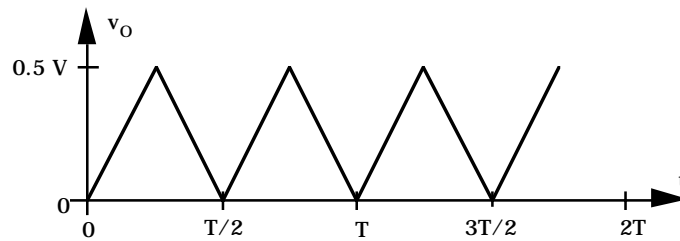


Homework Assignment No. 15 - Solutions

1.) Problem 12.122 of the text.



2.) Problem 12.128 of the text.

$$\text{For } V_O = 4.3 + 0.6 = 4.9\text{V: } V_+ = 4.9 \frac{4.3\text{k}\Omega}{4.3\text{k}\Omega + 39\text{k}\Omega} = 0.487\text{ V}$$

$$\text{For } V_O = -4.3 - 0.6 = -4.9\text{V: } V_+ = -4.9 \frac{4.3\text{k}\Omega}{4.3\text{k}\Omega + 39\text{k}\Omega} = -0.487\text{ V}$$

$$V_N = 0.487 - (-0.487) = 0.974\text{ V}$$

3.) Problem 12.130 of the text.

$$\text{For } v_O = +12\text{V: } V_+ = 6 \frac{24\text{k}\Omega}{3.4\text{k}\Omega + 24\text{k}\Omega} + 12 \frac{3.4\text{k}\Omega}{3.4\text{k}\Omega + 24\text{k}\Omega} = 6.74\text{ V}$$

$$\text{For } v_O = 0\text{V: } V_+ = 6 \frac{24\text{k}\Omega}{3.4\text{k}\Omega + 24\text{k}\Omega} = 5.26\text{ V}$$

$$v(t) = V_F - (V_F - V_I) \exp\left(-\frac{t}{RC}\right)$$

$$6.74 = 12 - (12 - 5.26) \exp\left(-\frac{T_1}{RC}\right) \rightarrow T_1 = 6200(3.3 \times 10^{-8}) \ln \frac{6.74}{5.26} = 50.7\ \mu\text{s}$$


$$5.26 = 0 - (0 - 6.74) \exp\left(-\frac{T_2}{RC}\right) \rightarrow T_2 = 6200(3.3 \times 10^{-8}) \ln \frac{6.74}{5.26} = 50.7\ \mu\text{s}$$

$$f = \frac{1}{50.7\ \mu\text{s} + 50.7\ \mu\text{s}} = 9.86\ \text{kHz}$$

4.) Problem 12.131 of the text.

$f = 0$. The circuit does not oscillate. $V_O = 0$ is a stable state.

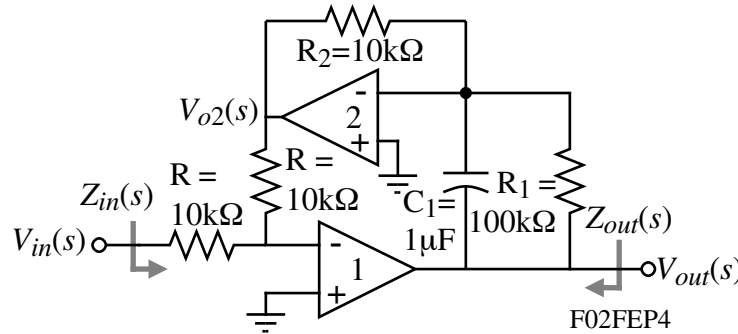5.) If the op amps shown are ideal (infinite voltage gain, infinite differential input resistance, and zero output resistance) find the voltage transfer function, $V_{out}(s)/V_{in}(s)$, the input impedance, $Z_{in}(s)$, and the output impedance, $Z_{out}(s)$. Sketch an asymptotic plot for the magnitude and phase shift of the voltage transfer function, $V_{out}(j\omega)/V_{in}(j\omega)$ as a function of $\log_{10}\omega$.



Solution

$V_{o2}(s)$ can be written as $V_{o2}(s) = -\frac{R_2}{Z_1}v_{out}(s)$. Thus, the currents flowing toward the

inverting terminal of the 1st op amp are, $\frac{V_{in}(s)}{R} + \frac{V_{o2}(s)}{R} = \frac{V_{in}(s)}{R} - \frac{R_2}{Z_1(s)} \frac{V_{out}(s)}{R} = 0$

$$\therefore \frac{V_{out}(s)}{V_{in}(s)} = \frac{Z_1(s)}{R_2} = \frac{1}{R_2} \frac{R_1(1/sC_1)}{R_1+(1/sC_1)} = \frac{R_1}{R_2} \frac{1}{sR_1C_1+1}$$

$\frac{V_{out}(s)}{V_{in}(s)} = \frac{R_1}{R_2} \frac{1}{sR_1C_1+1}$

By inspection, $Z_{in}(s) = R = 10k\Omega$ and $Z_{out}(s) = 0$

For the Bode plot we want to plot the magnitude and phase of $\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{10}{1+j\omega/10}$.

