

More Office Hours

Richard Tarbell - GTA for ECE 3050A

Room E292 VL (outside Dr. Allen's office)


MWF - 12-1pm Tues. 9:30-11am

Continue Review of ECE 3040

1.) Small-signal diode model


$$i_D = I_S \left[ \exp\left(\frac{v_D}{V_T}\right) - 1 \right]$$

Small-signal  $\Rightarrow$  Linear

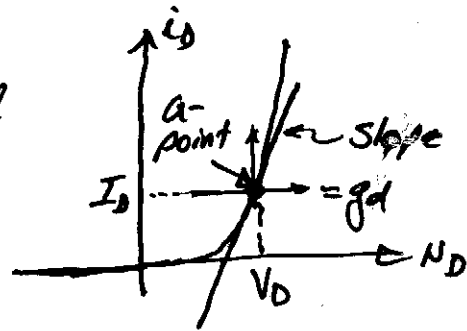


$$\left. \frac{\partial i_D}{\partial v_D} \right|_Q = \frac{I_S}{V_T} \left[ \exp\left(\frac{v_D}{V_T}\right) \right] \approx \frac{I_D}{V_T} \quad I_D \approx I_S \exp\left(\frac{v_D}{nV_T}\right)$$
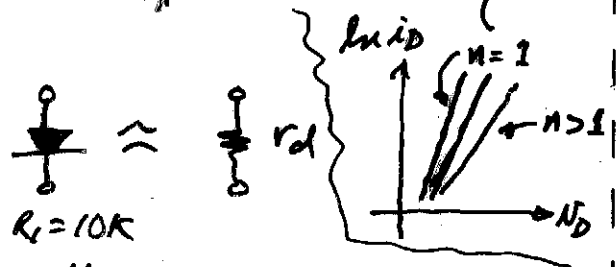
$$\text{d.c. } g_d = \frac{1}{r_d} = \frac{I_D}{V_T}$$



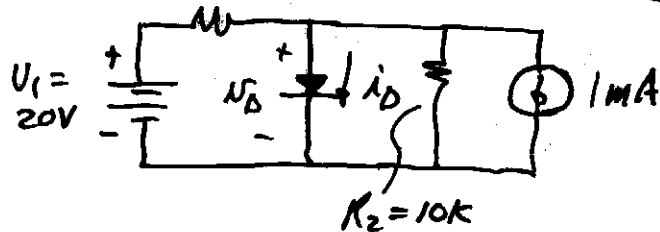2.) Example 1


- a.) Find the dc operating point assuming  $V_T = 25mV$ ,  $n = 1$ , and  $I_S = 100fA$ .



- b.) If the 20V voltage source,  $V_1$ , has a peak-to-peak sinusoidal voltage of 10mV superimposed on it, find the peak-to-peak value of  $v_D$  and  $i_D$ .

Solution -

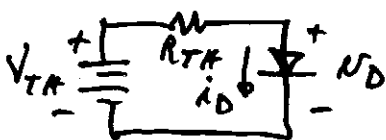
- a.) Find a Thevenin eq. circuit seen from diode



$$V_{TH} = \frac{R_2}{R_1 + R_2} 20V - \left( \frac{R_1 || R_2}{5K} \right) 1mA = 5V$$

$$R_{TH} = R_1 || R_2 = 5K$$

Example - Cont'd

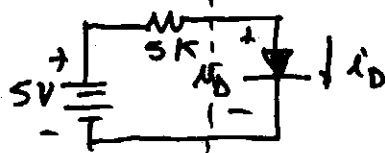



$$5V = i_D 5k + V_D \quad \left. \begin{array}{l} i_D = 100 \mu A \\ \times \exp\left(\frac{V_D}{V_T}\right) \end{array} \right\}$$

$$i_D = \frac{5 - V_D}{5k}$$



$\therefore I_D = 0.855 \text{ mA}$   
 $V_D = 0.573 \text{ V}$

Iteration - Guess for $V_D$	$I_D = \frac{5V - V_D}{5k}$	$100 \mu A \exp\left(\frac{V_D}{25mV}\right)$
0.6	0.85 mA	2.331 mA
0.57	0.826 mA	0.778 mA
↓		
0.5726	0.8554 mA	0.8552 mA

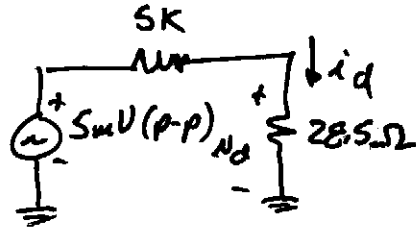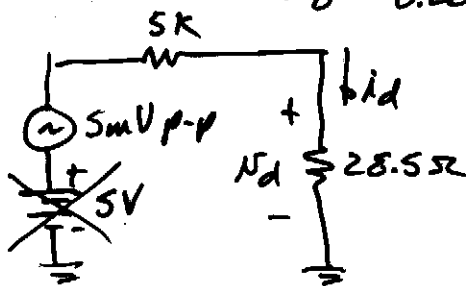b.) Find  $r_d = \frac{V_T}{I_D} = \frac{25 \text{ mV}}{0.855 \text{ mA}} = 28.5 \Omega$



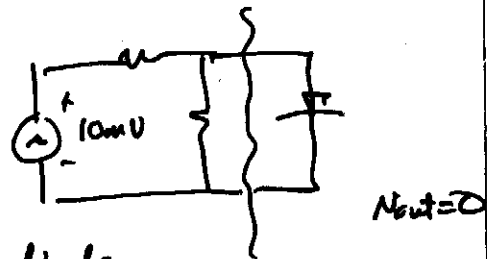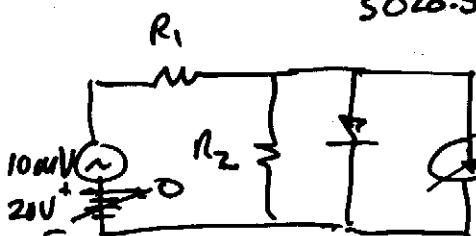
$$V_d = 5 \text{ mV} \frac{28.5 \Omega}{5028.5} = 0.028 \text{ mV} \rightarrow i_d = \frac{5 \text{ mV}}{5028.5} = 0.994 \mu A$$



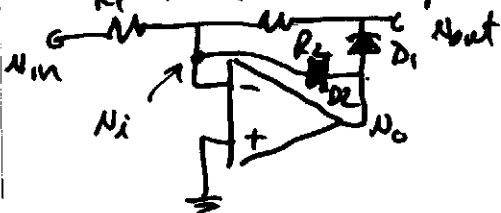3.) Circuits with more than 1 diode

Examine all possible states (ON or OFF) and

Then use a-priori to indentify the valid states



$N_i > 0 \rightarrow N_o < 0 \rightarrow D2 \text{ ON} \wedge D1 \text{ OFF}$


$N_i < 0 \rightarrow N_o > 0 \rightarrow D2 \text{ OFF} \wedge D1 \text{ ON}$

$N_{out} = -\frac{R_2}{R_1} N_{in}$


Other topics

- 1.) Voltage regulation
- 2.) Rectification  
 Half-wave  
 Full-wave

- 3.) Dynamic (time dependence) of diodes

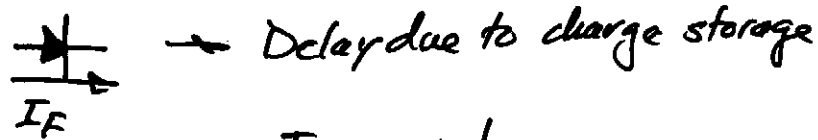

Chapter 4 - Jaeger - Transistor

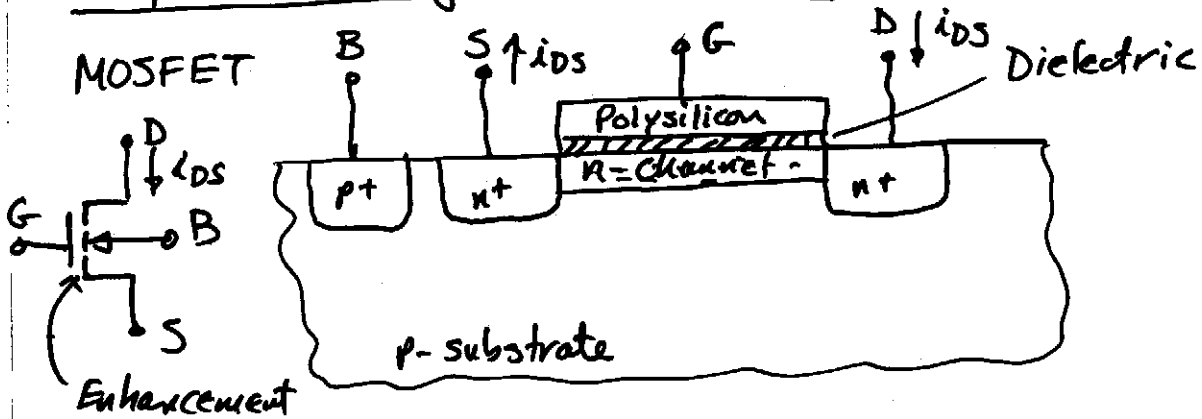


Regions of operation-

- a.) Linear

$$i_{DS} = \kappa'_n \frac{W}{L} \left( V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS}$$

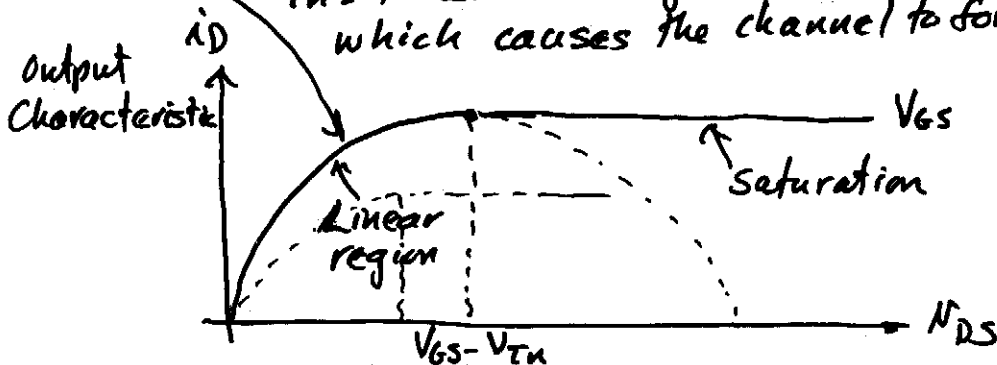$\kappa'_n$  = gain constant with units of  $A/V^2$   
 $V_{TN}$  = threshold voltage (the value of  $V_{GS}$  which causes the channel to form)




b.) Saturation

$$\text{Let } N_{DS} = N_{DS}(\text{sat}) = V_{GS} - V_{TN}$$

$$I_{DS} = K_n \frac{W}{L} \left( \frac{N_{GS} - V_{TN}}{2} \right) (N_{GS} - V_{TN}) = \frac{K_n W}{2L} (N_{GS} - V_{TN})^2$$

Depletion -

The channel always ~~exists~~ exists.

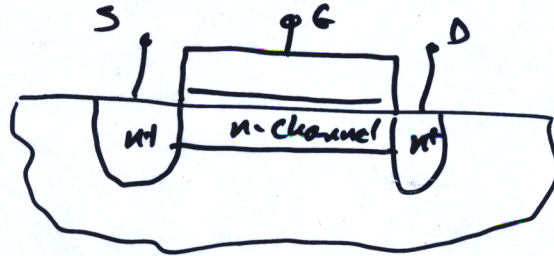

Use the same model as for enhancement let  $V_{TN} < 0$