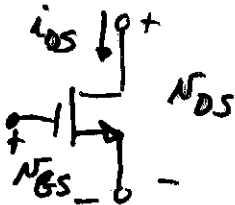


Review - Cont'd

MOSFET:



Cutoff:

$$i_{DS} = 0, V_{GS} < V_T$$

Active (Ohmic - GHLM-sat.):

$$V_{DS} < V_{GS} - V_T, V_{GS} > V_T$$

$$i_{DS} = \frac{\kappa' W}{L} \left[(V_{GS} - V_T) + \frac{V_{DS}}{2} \right] V_{DS} (1 + \lambda V_{DS})$$

Saturation (GHLM-active):



$$V_{DS} > V_{GS} - V_T, V_{GS} > V_T$$

$$i_{DS} = \frac{\kappa' W}{2L} (V_{GS} - V_T)^2 (1 + \lambda V_{DS})$$

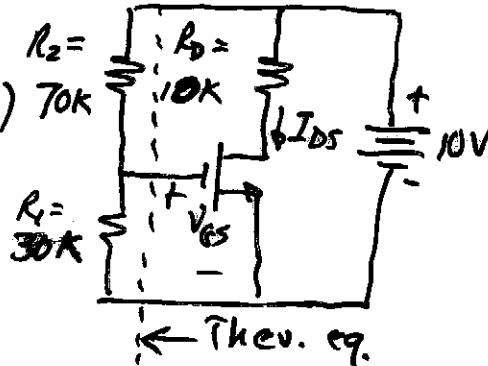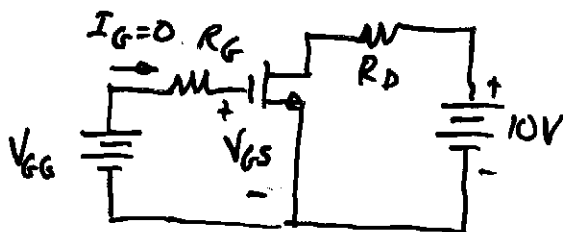Example 1

Find the dc operating point of the NMOS transistor (enh) assuming $\kappa'_N = 25 \mu A/V^2$

$W/L = 10$, $V_{TN} = 1V$ and $\lambda = 0$.



$$V_{GG} = \frac{R_1}{R_1 + R_2} 10V = 3V$$

$$R_G = R_1 || R_2 = 21K$$

Since $I_G = 0$, $V_{GS} = V_{GG} = \underline{3V}$

ASSUME the MOSFET is in saturation,


$$\therefore I_D = \frac{\kappa'_N W}{2L} (V_{GS} - V_T)^2 = \frac{25 \cdot 10}{2} (3 - 1)^2 \mu A = \underline{500 \mu A}$$

$$V_{DS} = 10 - I_D 10K = 10 - 5 = \underline{5V} ??$$

$$I_B \quad V_{DS} > V_{GS} - V_{TN} ? \quad 5 > 3 - 1 = 2 \quad \text{Yes.}$$

Example 2

Repeat Ex. 1 for the circuit shown.

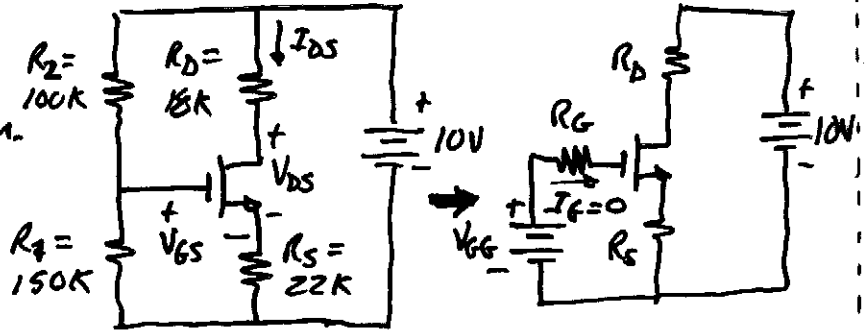


$$V_{GG} = 10 \frac{R_1}{R_1 + R_2} = 10 \frac{150}{250} = 6V$$

$$R_G = R_1 || R_2 = 60k$$

Gate source loop: $V_{GG} = V_{GS} + I_{DS} R_S$

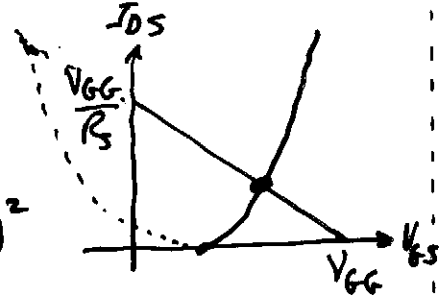Saturation eq: $I_{DS} = \frac{K_N'}{2} \frac{W}{L} (V_{GS} - V_T)^2$



$$I_{DS} = \frac{K_N}{2} (V_{GS} - V_T)^2 \quad \therefore K_N = K_N' \frac{W}{L}$$

$$V_{GG} = V_{GS} + R_S \frac{K_N}{2} (V_{GS} - V_T)^2 \rightarrow 6 = V_{GS} + 2.75 (V_{GS} - 1)^2$$


$$V_{GS}^2 - 1.636 V_{GS} - 1.182 = 0 \rightarrow V_{GS} = 0.8182 \pm 1.361$$

$$\therefore V_{GS} = \underline{2.179V} \rightarrow I_{DS} = \frac{125 \mu A}{V^2} (2.179 - 1)^2 = \underline{174 \mu A}$$

$$V_{DS} = 10V - I_{DS} (R_D + R_S) = 10V - 174 \mu A \cdot 40k = \underline{3.05V}$$

$$V_{DS} \stackrel{?}{>} V_{GS} - V_T \rightarrow 3.05V \stackrel{?}{>} 2.179 - 1 = 1.179 \text{ Yes}$$

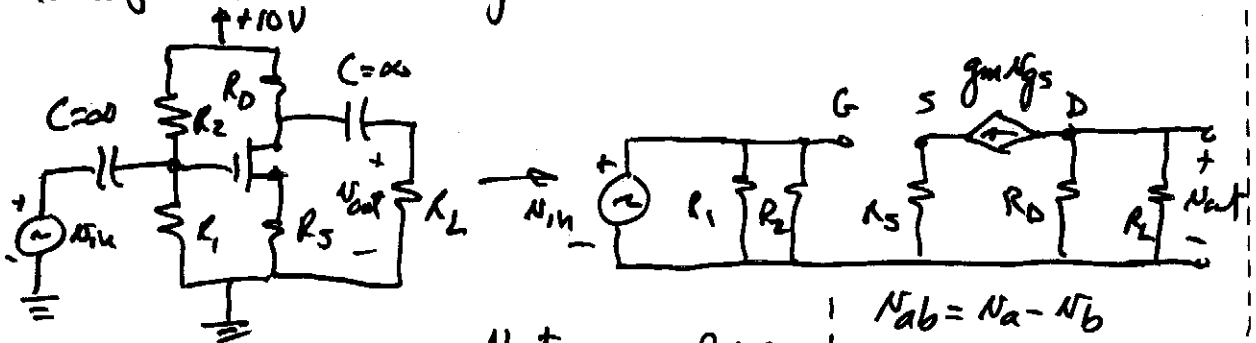To inject the small signal we modify the circuit as




$$\frac{N_{out}}{N_{in}} = \frac{-g_m R_D || R_L}{1 + g_m R_S}$$


$$\begin{aligned} N_{ab} &= N_a - N_b \\ N_{gs} &= N_g - N_s \\ N_{gs} &= N_{in} - R_S g_m i_{gs} \\ \frac{N_{gs}}{N_{in}} &= \frac{1}{1 + R_S g_m} \end{aligned}$$

BJT - Bipolar Junction Transistors

Schematic:

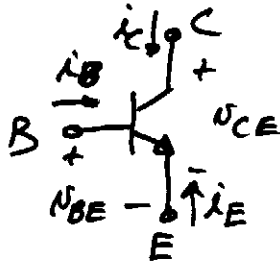

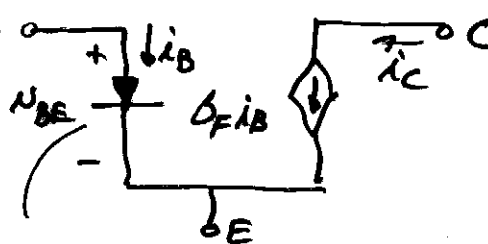Forward-Active Region: ($V_{BE} > 0, V_{BC} < 0$)



$$i_B = \frac{I_S}{\beta_F} \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right]$$

Key relationships:

$$i_B = \frac{I_S}{\beta_F} \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right] \approx \frac{I_S}{\beta_F} \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$i_C = \beta_F i_B = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A} \right)$$


Small signal model:

$$i_b = k_1 v_{be} = g_{\pi} v_{be}$$


$$i_c = k_2 v_{be} = g_m v_{be}$$

$$g_{\pi} = \frac{1}{r_{\pi}} = \frac{g_m}{\beta_F}$$

$$g_m = \frac{I_C}{V_T}$$

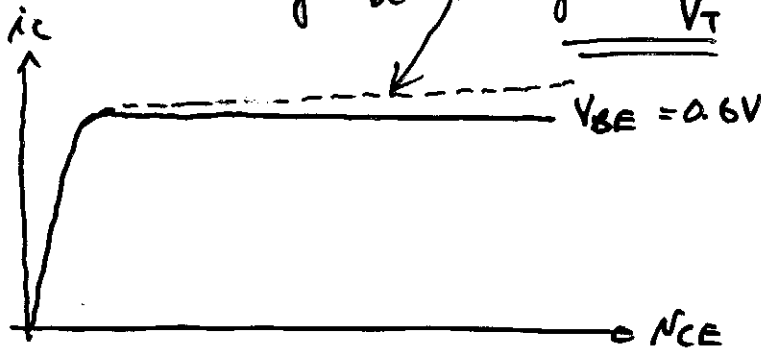

$$i_c = k_2 v_{be} + k_3 v_{ce} = g_m v_{be} + g_o v_{ce} \quad g_o = \frac{1}{r_o} = \frac{I_C}{V_A}$$

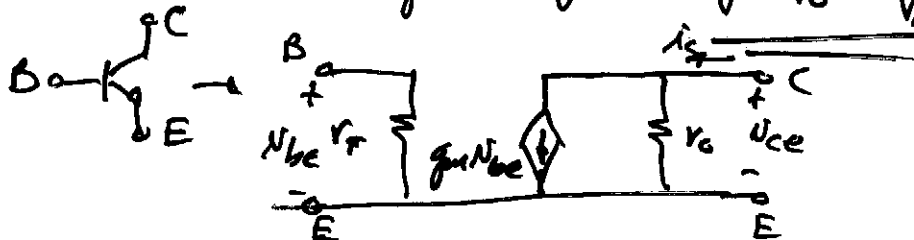


Example 3


Find the Q point if
 $\beta_F = 100$ and $V_{BEQ} = 0.65V$

$$R_{B1} = 315K$$

$$R_{B2} = 146K$$

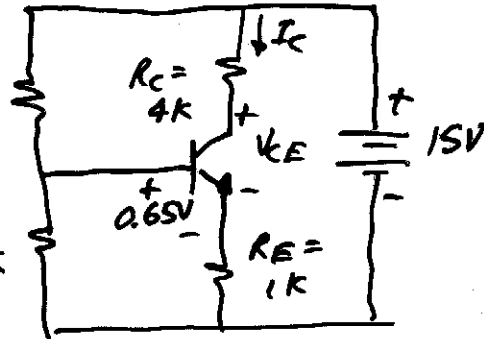

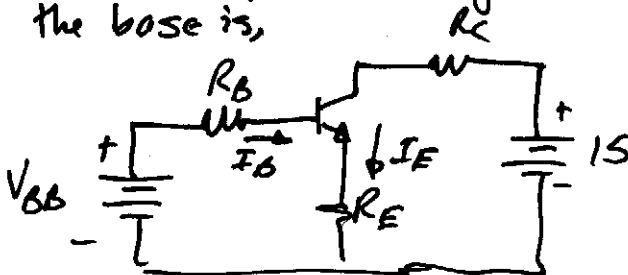Thevenin eq. of looking out
 the base is,



$$V_{BB} = 15 \frac{R_{B2}}{R_{B1} + R_{B2}} = 4.72V$$

$$R_B = R_{B1} || R_{B2} = 100k\Omega$$

~~$$I_B = \frac{V_{BB} - 0.65}{R_B}$$~~

$$V_{BB} = I_B R_B + V_{BE} + I_B (\beta_F) R_E$$

$$I_B = \frac{V_{BB} - 0.65}{R_B + (\beta_F) R_E} = \underline{20\mu A} \quad I_C = \underline{2mA}$$

$$I_E = I_C + I_B = \underline{2.02mA}$$

$$V_{CE} = 15 - 2mA (R_C + R_E) = \underline{4.88V}$$