

CHAPTER 11 - ANALOG SYSTEMS → AMPLIFIERS

1.) Linearity vs. nonlinearity



A system is linear iff


$$u_1(t) \rightarrow y_1(t)$$

$$u_2(t) \rightarrow y_2(t)$$

and $u_1(t) + u_2(t) \rightarrow y_1(t) + y_2(t)$ for all $u(t)$.

"A system is linear if the relationship between $y(t)$ and $u(t)$ is constant for all value $u(t)$."

2.) Linear Amplifier

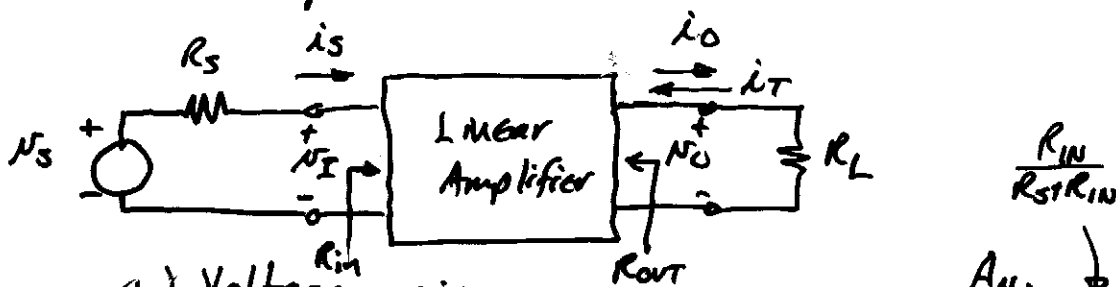

a.) Voltage gain

$$A_N = \frac{N_O}{N_I} \quad (R_S=0) \quad \text{or} \quad A_V = \frac{N_O}{N_S} = \frac{N_O}{N_I} \times \frac{N_I}{N_S}$$

$$A_V = A_N \frac{R_{IN}}{R_S + R_{IN}}$$

b.) Current gain


$$A_I = \frac{i_O}{i_S} = \frac{N_O/R_L}{N_S} = \frac{N_O}{N_S} \frac{R_S + R_{IN}}{R_L} = A_V \frac{R_S + R_{IN}}{R_L}$$

c.) Power gain

$$A_P = A_V A_I$$

$$d.) R_{IN} = \frac{N_I}{i_S}$$

$$\text{and} \quad R_{OUT} = \left. -\frac{N_O}{i_T} \right|_{N_S=0} = \left. -\frac{N_O}{i_T} \right|_{N_S=0}$$

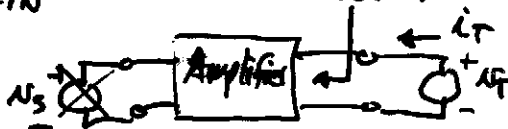

3.) Decibels

$$A_p(\text{dB}) \equiv 10 \log_{10}(A_p) \quad \text{If } A_p = 10, \text{ then } \log_{10} 10 = 1$$

$$\therefore A_p = 10 \text{ dB}$$

$$A_p(\text{dB}) = 10 \log_{10}[A_v A_z]$$

Suppose that $R_s = 0$ and $R_L = R_{in}$ from the previous

page $A_z = \frac{R_s + R_{in}}{R_L} A_v = A_v \rightarrow A_z = A_v$


$$A_v(\text{dB}) = 10 \log_{10}(A_z A_v) = 10 \log_{10}(A_v^2) = 20 \log_{10}(A_v)$$

If $R_s = 0$ and $R_{in} = R_L$, then

$$\underline{A_v(\text{dB}) = 20 \log_{10}(A_v)} \quad \text{If } A_v = 10, \text{ then } A_v(\text{dB}) = 20 \text{ dB}$$

A_v V/V	10	100	1000	...	30	20	40
$A_v(\text{dB})$	20	40	60	-	30	26	32

4.) Amplifier - Power Viewpoint

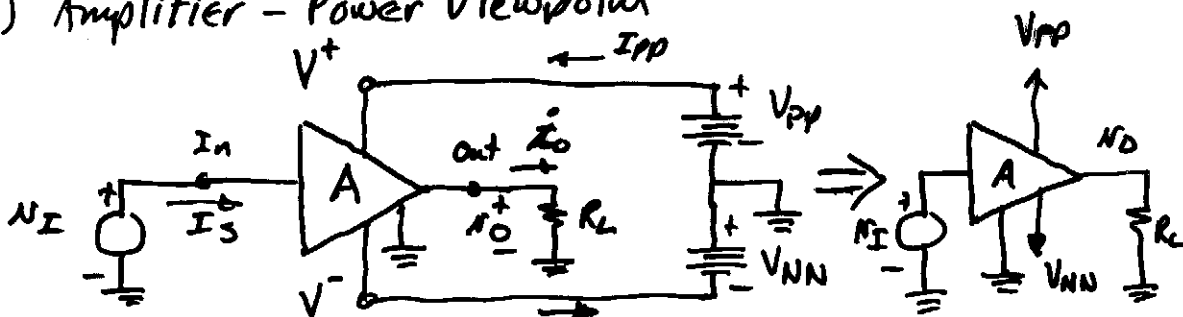

What types of power exist?


- 1.) DC power delivered to the amplifier, $P_{DC} = V_{PP} I_{PP} + V_{NN} I_{NN}$
- 2.) Power $P_{in} = v_i i_s$
- 3.) Power out: $P_{out} = i_o v_o$ (Power to the load)
- 4.) Power lost P_{diss}

Power conservation:

$$P_{DC} + P_{in} = P_{out} + P_{diss} = P_L + P_{diss}$$

$$\text{Efficiency} \equiv \frac{P_L}{P_{DC}} \times 100\%$$

5) Example -

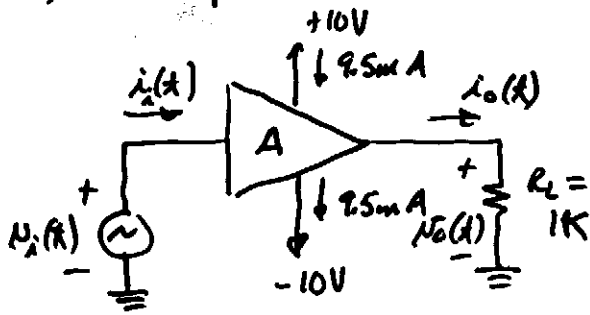

If $N_i(t) = 1 \sin \omega_0 t$, then

$N_o(t) = 9 \sin \omega_0 t$ and

$i_i(t) = 0.1 \sin \omega_0 t$ (mA).

Find the efficiency of this amplifier.

$$\text{Efficiency} = \eta = \frac{P_L}{P_{DC}}$$

$$A_v = 9 \text{ V/V} \rightarrow A_v \text{ (dB)} = 20 \log_{10}(9) = 19.1 \text{ dB}$$

$$i_o(\text{peak}) = \frac{V_o(\text{peak})}{R_L} = \frac{9 \text{ V}}{1 \text{ k}\Omega} = 9 \text{ mA (peak)}$$

$$i_o(t) = 9 \sin \omega_0 t \text{ (mA)} \rightarrow A_i = \frac{9 \text{ mA}}{0.1 \text{ mA}} = 90 \rightarrow A_i \text{ (dB)} = 39.1 \text{ dB}$$

$$P_L = \left(\frac{9}{\sqrt{2}}\right) \left(\frac{9 \text{ mA}}{\sqrt{2}}\right) = \frac{81 \text{ mW}}{2} = \underline{\underline{40.5 \text{ mW}}}$$

$$P_T = \left(\frac{1 \text{ V}}{\sqrt{2}}\right) \left(\frac{0.1 \text{ mA}}{\sqrt{2}}\right) = \frac{0.1 \text{ mW}}{2} = \underline{\underline{0.05 \text{ mW}}}$$

$$A_p = \frac{40.5}{0.05} = 810 \text{ W/W} \\ = 29.1 \text{ dB}$$

$$P_{DC} = (10 \cdot 9.5 \text{ mA}) \times 2 = 190 \text{ mW}$$

$$\eta = \frac{P_L}{P_{DC}} = \frac{40.5 \text{ mW}}{190 \text{ mW}} \times 100\% = 21.39\%$$

$$P_{\text{diss}} = P_{DC} + P_T - P_L = 149.65 \text{ mW}$$