

Bandpass Amplifiers - Wideband ($\omega_H \gg \omega_L$)


The simplest transfer function for a BP amp. $= A_v(s) = \pm A_0 \left(\frac{s}{s + \omega_L} \right) \left(\frac{\omega_H}{s + \omega_H} \right)$

$$A_v(j\omega) = \pm A_0 \left(\frac{j\omega}{1 + j\frac{\omega}{\omega_L}} \right) \left(\frac{1}{1 + j\frac{\omega}{\omega_H}} \right)$$



$$|A_v(j\omega)| = A_0 \frac{\omega/\omega_L}{\sqrt{1 + (\frac{\omega}{\omega_L})^2} \sqrt{1 + (\frac{\omega}{\omega_H})^2}}$$


$$|A_v(j\omega)|_{dB} = 20 \log_{10} A_0 + 20 \log_{10} \left(\frac{\omega}{\omega_L} \right) - 20 \log_{10} \sqrt{1 + \left(\frac{\omega}{\omega_L} \right)^2} - 20 \log_{10} \sqrt{1 + \left(\frac{\omega}{\omega_H} \right)^2}$$

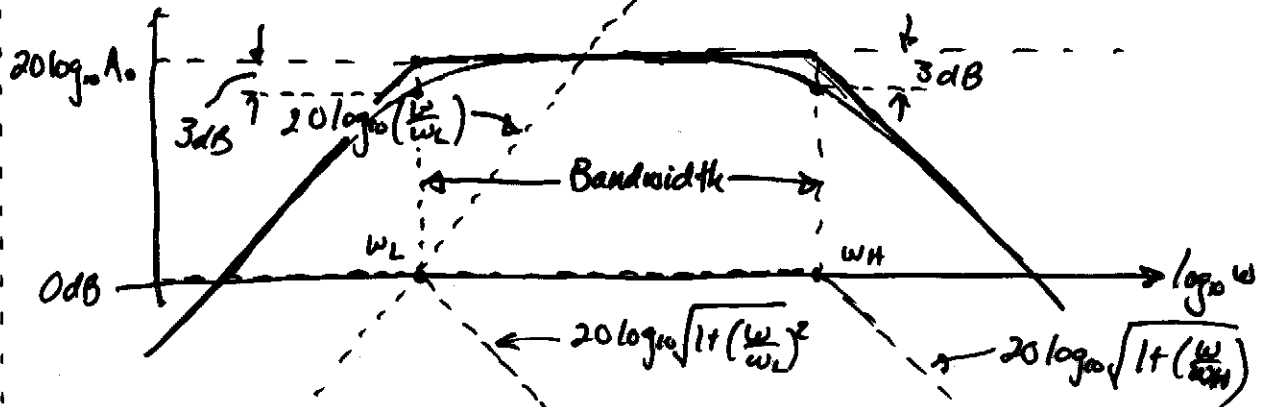


Phase shift -

$$\text{Arg}[A_v(j\omega)] = \pm 180^\circ + 90^\circ - \tan^{-1} \left(\frac{\omega}{\omega_L} \right) - \tan^{-1} \left(\frac{\omega}{\omega_H} \right)$$

If minus sign

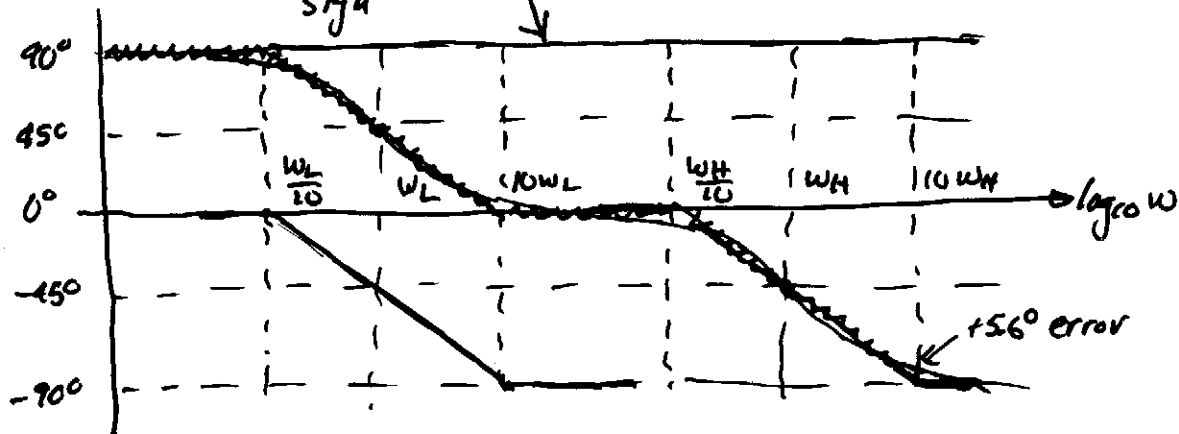


Narrowband Amplifiers

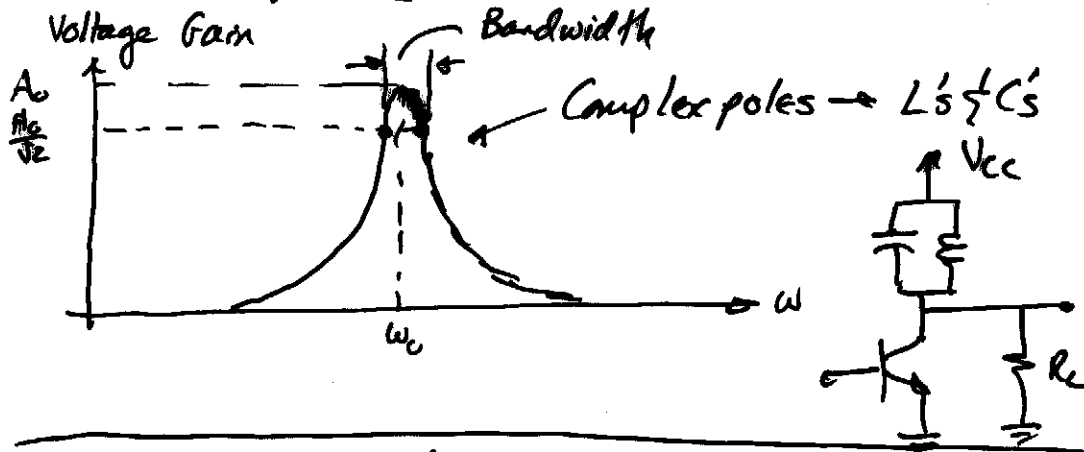

CHAPTER 12 - Operational Amplifiers (op Amp)


1.) Differential Amplifier

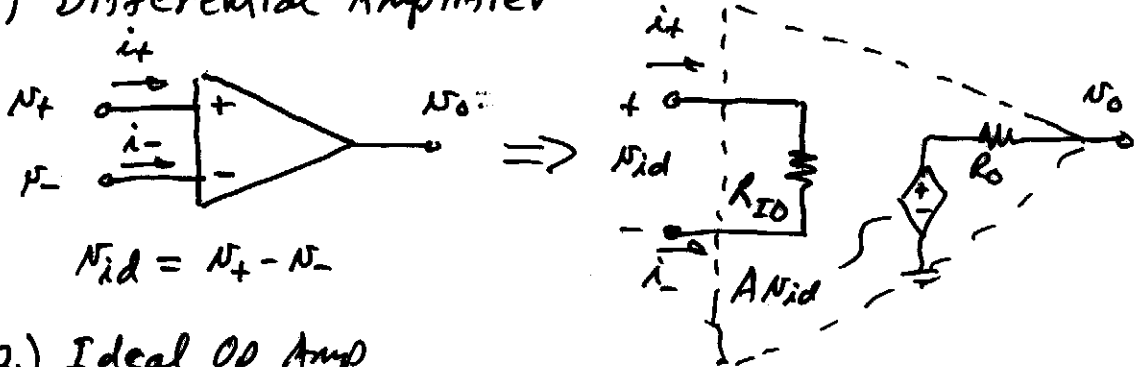

2.) Ideal Op Amp

- 1.) $N_{id} = 0$
 $i_+ = i_- = 0$ } Assume some form of negative feedback from the output back to the input.

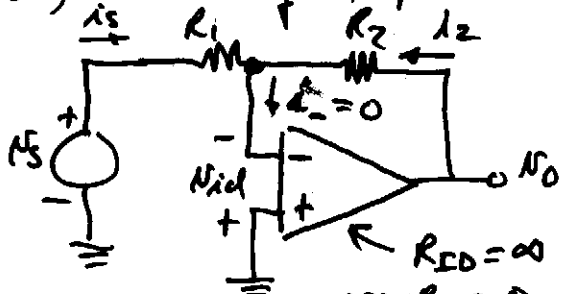3.) Inverting Amplifier - Assume op amp is ideal.



$$i_s = \frac{N_3 + N_{id}}{R_1} \approx \frac{N_3}{R_1}$$

$$i_2 = \frac{N_0 + N_{id}}{R_2} \approx \frac{N_0}{R_2}$$


$$i_s + i_2 = 0$$

$$\therefore \frac{N_0}{R_2} = -\frac{N_3}{R_1} \rightarrow \boxed{\frac{N_0}{N_3} = -\frac{R_2}{R_1}}$$

$R_{in} = \frac{N_3}{i_s} = R_1$

Gain = A = Large
 $R_{out} = 0$

4.) Noninverting Amplifier

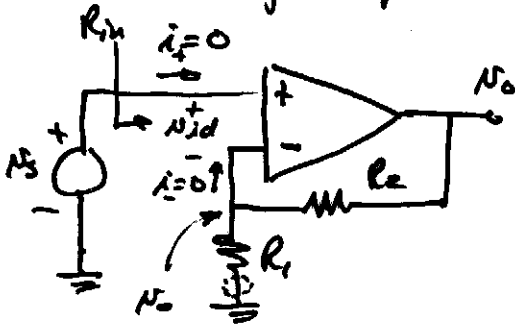

$$N_- = N_o \frac{R_1}{R_1 + R_f}$$


$$N_{id} = N_s - N_- = 0$$

$$N_s = N_o \frac{R_1}{R_1 + R_f} \rightarrow \boxed{\frac{N_o}{N_s} = \frac{R_1 + R_f}{R_1}}$$

$$\underline{R_{in} = \frac{N_s}{i_+} = \infty} \quad \underline{R_{out} = 0}$$

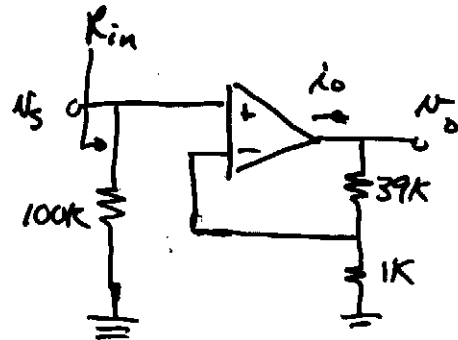5.) Example -

What is the voltage gain in dB and R_{in} ? If $N_s = 0.25V$ what is N_o and i_o ?




$$\frac{N_o}{N_s} = \frac{R_1 + R_f}{R_1} = \frac{1k + 39k}{1k} = 40 \rightarrow 10 \cdot 2 \cdot 2 \rightarrow \underline{\underline{32dB}}$$

$$R_{in} = 100k || \infty = \underline{\underline{100k}}$$

$$\text{If } N_s = \frac{1}{4}V \rightarrow N_o = 10V \rightarrow i_o = \frac{N_o}{R_1 + R_f} = \frac{10V}{40k} = \underline{\underline{0.25mA}}$$


6.) Op Amp Circuits

(a.) +1 gain or buffer (voltage)

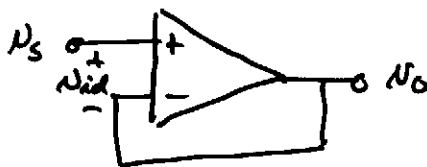

$$N_{id} = N_s - N_o = 0 \rightarrow \underline{\underline{N_o = N_s}}$$

(b.) Summing, inverting amplifier

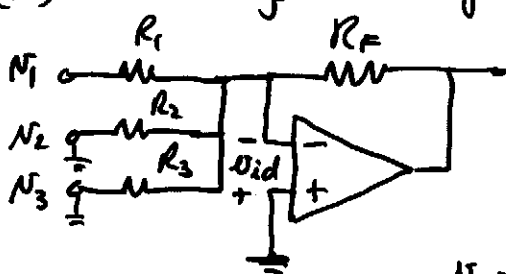


$$N_o = N_o | + N_o | + N_o |$$

$N_2 = N_3 = 0 \quad N_1 = N_3 = 0 \quad N_2 = N_3 = 0$

$$N_o = -\frac{R_f}{R_1} N_1 - \frac{R_f}{R_2} N_2 - \frac{R_f}{R_3} N_3$$

$$N_o = -R_f \left(\frac{N_1}{R_1} + \frac{N_2}{R_2} + \frac{N_3}{R_3} \right)$$

(c.) Difference Amplified

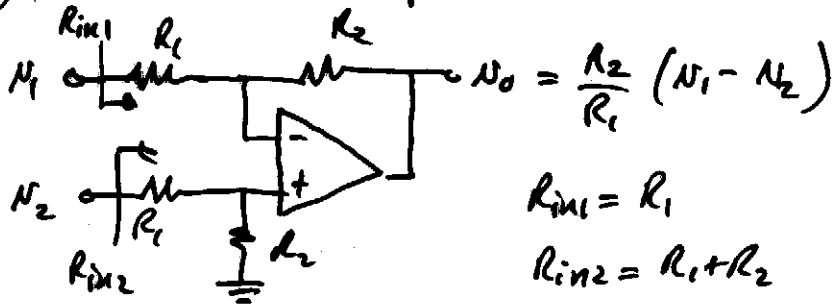

$$N_0 = \frac{R_2}{R_1} (N_1 - N_2)$$

$$R_{in1} = R_1$$

$$R_{in2} = R_1 + R_2$$