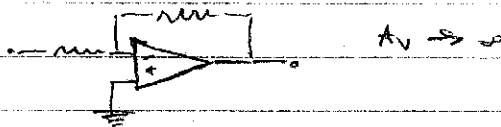


1/24/03
Friday



Frequency Response of Op-Amps

Sec. 12-6


1) Ideal Op-Amp




2) Finite Gain GB

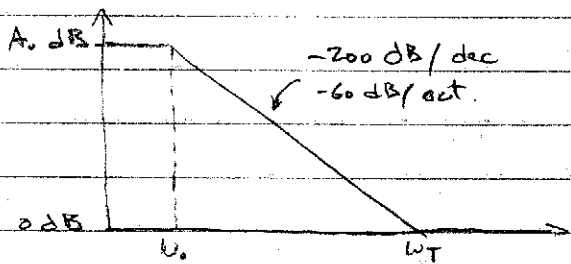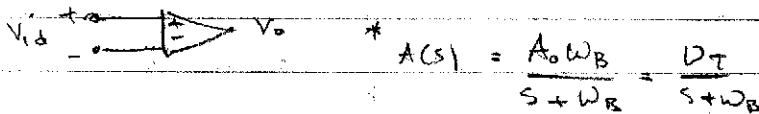

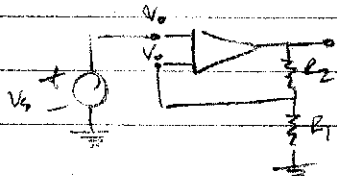$W_T = \text{unity gain}$
 $GB = A_0 W_B$



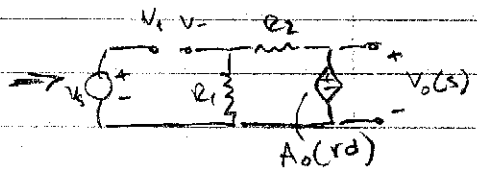$V_o = \frac{R_1 + R_2}{R_1} V_s$
(ideal)



$V_o = A(s) V_{id} = A(s) [V_s - V_o] = A(s) V_s - A(s) \frac{R_1}{R_1 + R_2} V_o$

$V_o = A(s) V_s - A(s) \beta V_o$

$V_o [1 + A(s) \beta] = A(s) V_s \rightarrow \frac{V_o}{V_s} = A_v(s) = \frac{A(s)}{1 + \beta A(s)}$

$A_v(s) = \frac{1}{\frac{1}{A(s)} + \beta} = \frac{1}{\frac{s + W_B}{A_0 W_B} + \beta} = \frac{A_0 W_B}{s + W_B + \beta A_0 W_B} = \frac{A_0 W_B}{s + W_B (1 + A_0 \beta)}$

$\frac{A_0 W_B}{W_B (1 + A_0 \beta)} \left(\frac{1}{\frac{s}{W_B (1 + A_0 \beta)} + 1} \right) = \boxed{\frac{A_v(0)}{\frac{s}{W_T} + 1}}$

* $A_v(0) = \frac{A_0}{1 + A_0 \beta}$

* $W_T = W_B (1 + A_0 \beta)$
 $\approx W_B A_0 \beta$
 $\approx W_T$

Example

GIVEN:



$$A_0 = 10,000$$

$$\beta = \frac{1}{10}$$

$$\omega_B = 10^3 \text{ rad/s}$$

$$R_2 = 9R_1$$

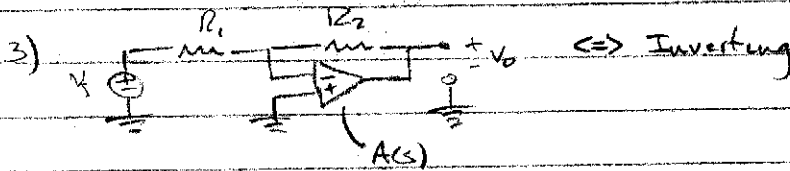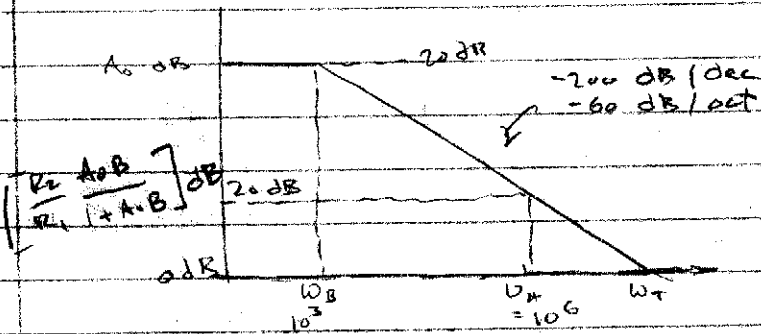
$$A_V(0) = \frac{A_0}{1+A_0\beta} = 10 \quad \omega_H = \omega_B(1+A_0\beta) = 10^3(1+10^3) = 10^6$$



$A_0\beta \gg 1$

$$A_V(0) = -\frac{R_2}{R_1} \frac{A_0\beta}{1+A_0\beta} \approx -\frac{R_2}{R_1}$$

$$\omega_H = \omega_B(1+A_0\beta)$$

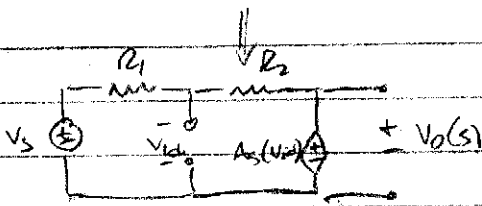

$$V_o(s) = A(s)V_{id} = A(s) \left[-V_s \frac{R_2}{R_1+R_2} - V_o \frac{R_1}{R_1+R_2} \right] \beta$$

$$V_o \left[1 + \frac{A(s)R_1}{R_1+R_2} \right] = -A(s) \frac{R_2}{R_1+R_2} V_s = -A(s) \frac{R_2}{R_1} \frac{R_1}{R_1+R_2} V_s$$

$$A_V(s) = \frac{V_o(s)}{V_s(s)} = \frac{-\frac{R_2}{R_1} A(s) \beta}{1 + A(s) \beta} = \frac{-\frac{R_2}{R_1} \beta}{\frac{1}{A(s)} + \beta} = \frac{-\frac{R_2}{R_1} \beta}{\frac{s + \omega_B}{\omega_B A_0} + \beta} = \frac{-\frac{R_2}{R_1} \beta \omega_B A_0}{s + \omega_B(1+A_0\beta)}$$

$$= \frac{-\frac{R_2}{R_1} \omega_B \beta A_0}{\frac{s}{\omega_B(1+A_0\beta)} + 1} = \frac{A_V(0)}{\frac{s}{\omega_H} + 1} \quad \therefore \omega_H$$