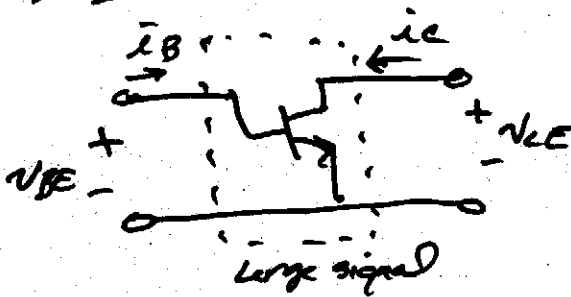


Small signal transistor models

1.) Small signal large signal relationships

$$i_A = i_a + I_A \rightarrow i_a = \dot{I}_A - I_A = \Delta i_A = d i_A$$


2.) CE BJT



FAO active region

$$i_c = I_S \left[\exp\left(\frac{v_{BE}}{V_T}\right) \right] \left[1 + \frac{v_{CE}}{V_A} \right]$$
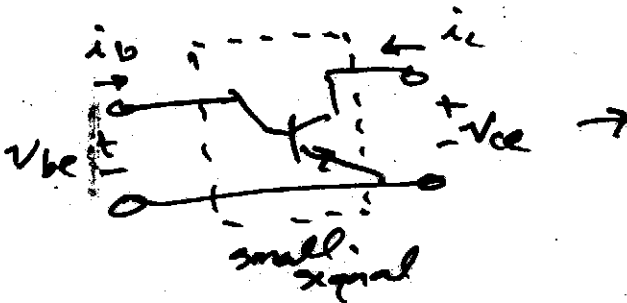
$$i_B = \frac{I_S}{\beta_F} \exp\left(\frac{v_{BE}}{V_T}\right)$$



$$i_c = K_1 v_{be} + K_2 v_{ce}$$

$$i_b = K_3 v_{be}$$

What are K_1, K_2, K_3 ?


$$K_1 = \left. \frac{i_c}{v_{ce}} \right|_{v_{be}=0} = \left. \frac{\partial i_c}{\partial v_{ce}} \right|_Q = \frac{I_c}{V_T} = g_m$$

$$K_2 = \left. \frac{i_c}{v_{be}} \right|_{v_{ce}=0} = \left. \frac{\partial i_c}{\partial v_{be}} \right|_Q = \frac{I_c}{V_A + V_{CE}} \approx \frac{I_c}{V_A} = g_o$$

$$\frac{V_A}{I_c} = r_o$$


$$K_3 = \left. \frac{i_b}{v_{be}} \right|_{v_{ce}=0} = \left. \frac{\partial i_b}{\partial v_{be}} \right|_Q = \frac{I_c}{\beta_0 V_T} = g_{\pi}$$
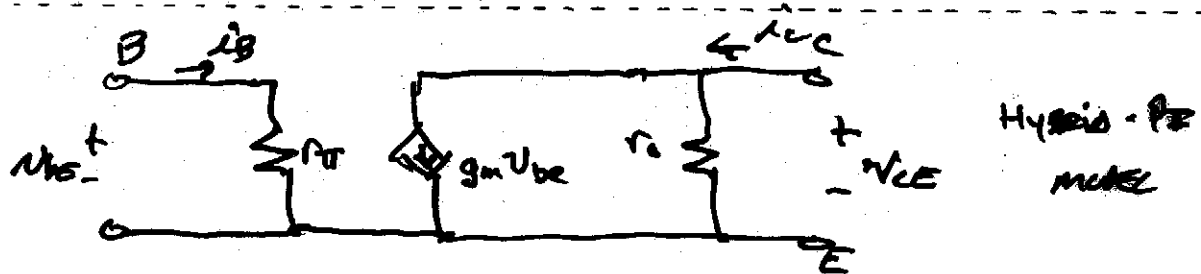
$$\Rightarrow r_{\pi} = \frac{\beta_0 V_T}{I_c}$$



$$i_c = g_m v_{be} + g_o v_{ce} \quad i_b = g_{\pi} v_{be}$$

- β_F is not constant with I_C

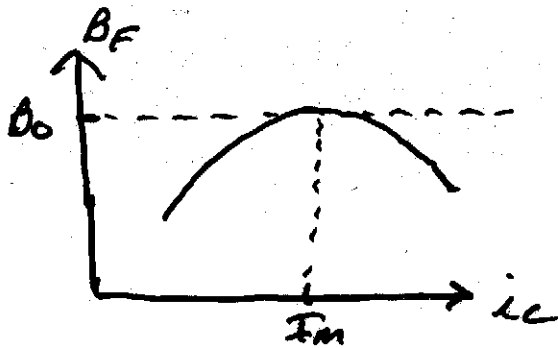


- $g_m = \frac{I_C}{V_T}$ and $g_m \beta_0 = \frac{I_C}{V_T} \Rightarrow g_m = g_m \beta_0 = \frac{\beta_0}{r_{\pi}}$

- Linearity: requires that $v_{be} \ll 2 V_T$

- PNP 2.5 model is identical to NPN.


Example:

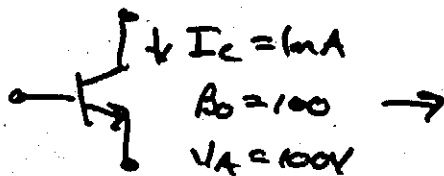


$$g_m = \frac{1 \text{E-3}}{25 \text{E-3}} = 40 \text{ mS}$$

$$g_{\pi} = \frac{1 \text{E-3}}{(25 \text{E-3}) 100} = 0.4 \text{ mS} \quad \rightarrow r_{\pi} = 2.5 \text{ k}\Omega$$
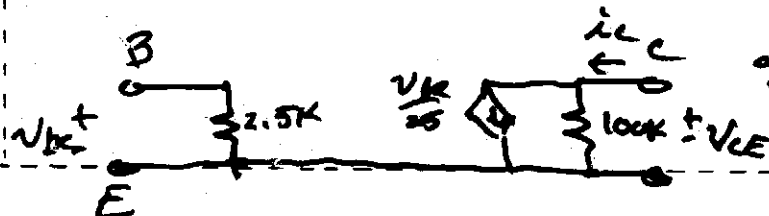
$$g_o = \frac{1}{100 \text{ mS}} \rightarrow r_o = 100 \text{ k}\Omega$$



5.) CURRENT CONTROLLED BJT s.d. MODEL

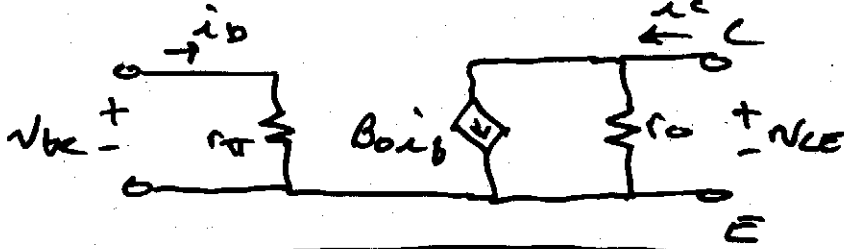


Example: CE BJT AMPLIFIER

GIVEN: $\beta_F = \beta_0 = 100$

$V_A = \infty$


$V_{CC} = 10V$

$V_{BE} = 0.7V$

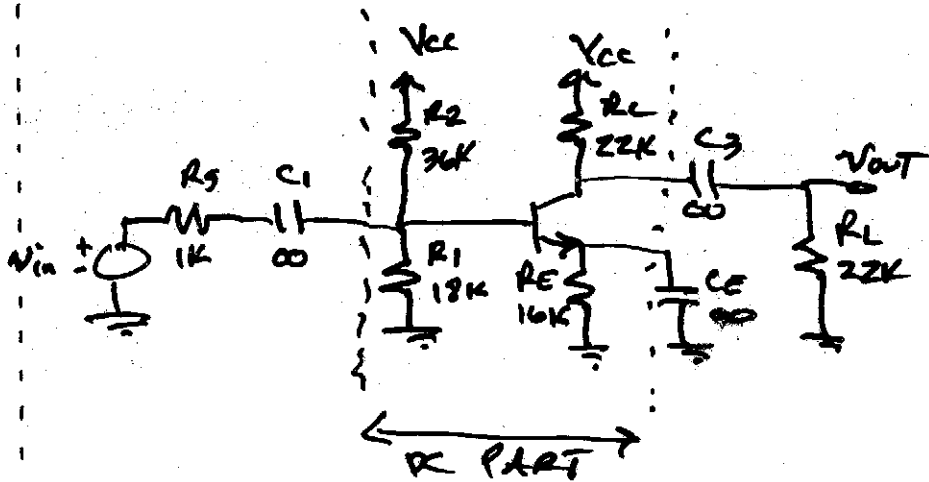

FIND: A_v, R_{in}, R_{out}

Q POINT ($V_C, V_B, V_E, I_C, I_E, I_B$)

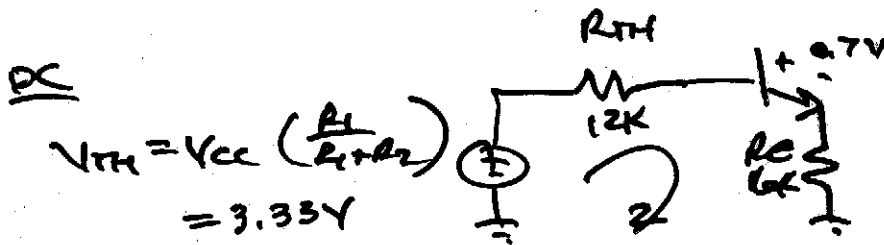

$$V_{TH} = V_{CC} \left(\frac{R_2}{R_1 + R_2} \right) = 3.33V$$


$$3.33 - I_B R_{TH} - 0.7 - (1 + \beta) I_B R_E = 0$$

$$\Rightarrow I_B = 1.62 \mu A, I_C = 162 \mu A, I_E = 164 \mu A$$

$$\Rightarrow V_C = 6.44V, V_E = 2.62V, V_B = 3.32V$$

AC
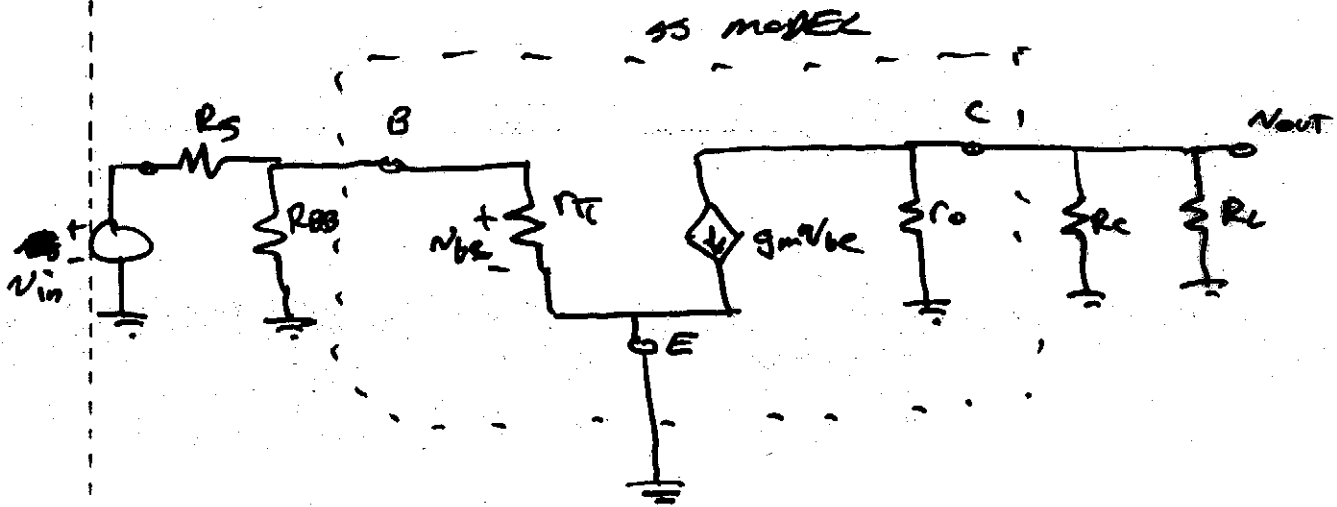
$$g_m = \frac{I_C}{V_T} = 6.48 mS, r_o = \frac{V_A}{I_C} = \infty, r_{\pi} = \frac{\beta_0 V_T}{I_C} = \frac{\beta_0}{g_m} = 15.4 k\Omega$$



$$g_m = 6.48 \text{ mS}$$

$$r_o = \infty$$

$$r_\pi = 15.4 \text{ K}$$

$$A_v = \frac{v_{out}}{v_{in}} = \left(\frac{v_{be}}{v_{in}} \right) \left(\frac{v_{out}}{v_{be}} \right) = \left(\frac{R_{BB} \parallel r_\pi}{R_{BB} \parallel r_\pi + R_S} \right) \left(-g_m [R_C \parallel R_L \parallel r_o] \right)$$

$$= (0.871)(-71.28)$$

$$A_v = -62.1$$

$$R_{in} = R_S + R_{BB} \parallel r_\pi$$

$$= 7.74 \text{ K}\Omega$$

$$R_{out} = R_C \parallel R_L \parallel r_o$$

$$= 11 \text{ K}\Omega$$