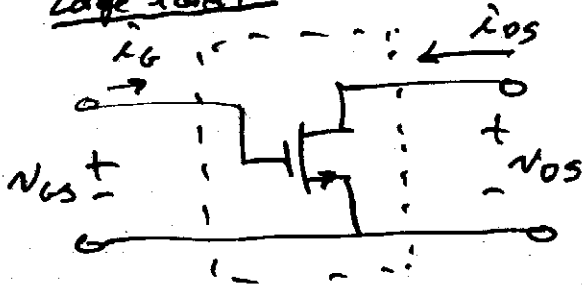
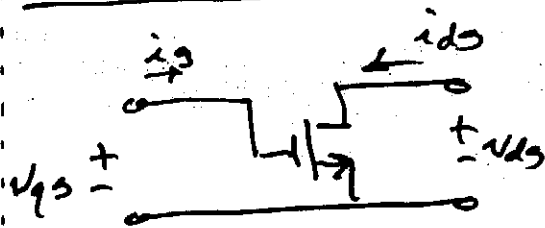


MOSFET SMALL SIGNAL MODELLarge signal

SAT MODE

$$\begin{array}{l} \text{MATH} \quad i_{DS} = \frac{K_n}{2} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \\ \text{MODEL} \quad i_G = 0 \end{array}$$

small signal

$$\begin{array}{l} \text{MATH} \quad i_{DS} = K_1 v_{gs} + K_2 v_{DS} \\ \text{MODEL} \quad i_G = 0 \end{array}$$

$$K_1 = \left. \frac{i_{DS}}{v_{gs}} \right|_{v_{DS}=0} = \left. \frac{\partial i_{DS}}{\partial v_{GS}} \right|_Q = K_n (V_{GS} - V_{TH}) (1 + \lambda V_{DS}) = g_m$$


(generally: $\lambda V_{DS} \approx 0 \rightarrow g_m = \sqrt{K_n I_{DS}} = \sqrt{2K_n' \frac{W}{L} I_{DS}}$)

$$g_m = K_1 = K_n \sqrt{\frac{2I_{DS}}{K_n (1 + \lambda V_{DS})}} (1 + \lambda V_{DS})$$


$$g_m = \sqrt{2I_{DS} K_n (1 + \lambda V_{DS})}$$

$$K_2 = \left. \frac{i_{DS}}{v_{DS}} \right|_{v_{gs}=0} = \left. \frac{\partial i_{DS}}{\partial v_{DS}} \right|_Q = \lambda \frac{K_n}{2} (V_{GS} - V_{TH})^2 = \lambda \frac{K_n}{2} \left(\frac{2I_{DS}}{K_n (1 + \lambda V_{DS})} \right)$$
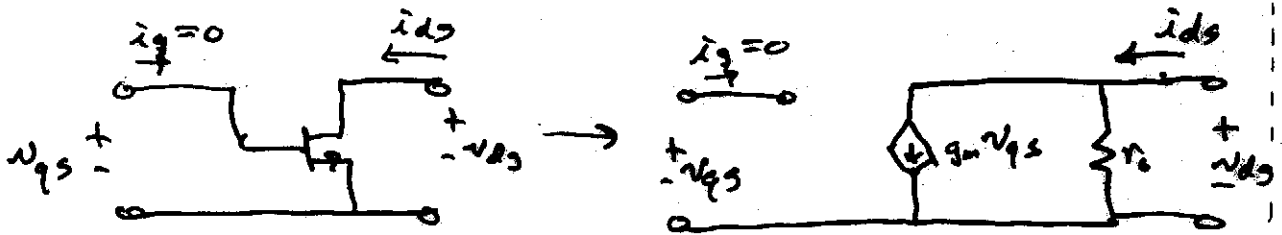
$$\Rightarrow g_o = \frac{1}{r_o} = \frac{\lambda I_{DS}}{1 + \lambda V_{DS}}$$




Example:

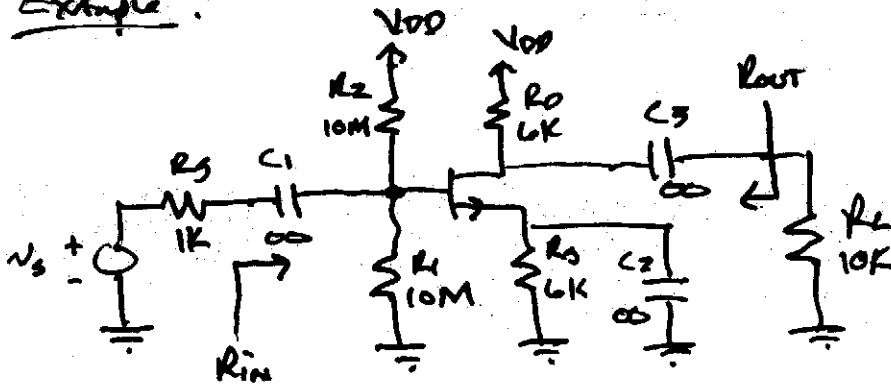

GIVEN:
 $K_n = \frac{0.5 \text{ mA}}{\text{V}^2}$
 $V_{th} = 1 \text{ V}$
 $\lambda = 0.01 \text{ V}^{-1}$
 $V_{DD} = 10 \text{ V}$

FIND
 A_v, R_{in}, R_{out}

FIND Q POINT

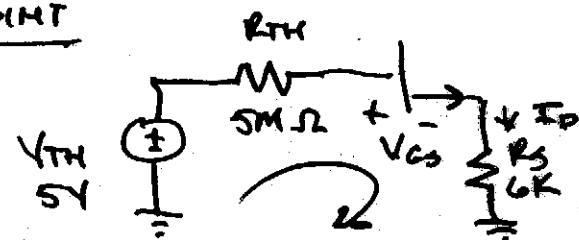

$$5 = v_{gs} + R_S \left[\frac{K_n}{2} (v_{gs} - V_{th})^2 \right] \rightarrow I_D$$

$$0 = \frac{3}{2} v_{gs}^2 - 2 v_{gs} - 7/2$$

$$v_{gs} = 7/3 \text{ OR } -1 \rightarrow v_{gs} = 2.33 \text{ V}$$

$$I_{D_S} = \frac{0.5 \text{ mA}}{2} (2.33 - 1)^2 = 0.442 \text{ mA}$$

$$V_{D_S} = +10 - I_D (R_D + R_S) = 4.70 \text{ V}$$

SAT MODE: $V_{D_S} > V_{gs} - V_{th} = 1.33 \text{ V}$


$$V_{D_S} = 4.70 > 1.33 \rightarrow \text{SAT MODE!}$$

small signal parameters

$$g_m = \sqrt{K_n I_{DQ}} = 0.668 \text{ mS}$$

$$r_o = \frac{V_{A0} + \frac{1}{2}}{I_{DQ}} = 237 \text{ k}\Omega$$

small signal circuit

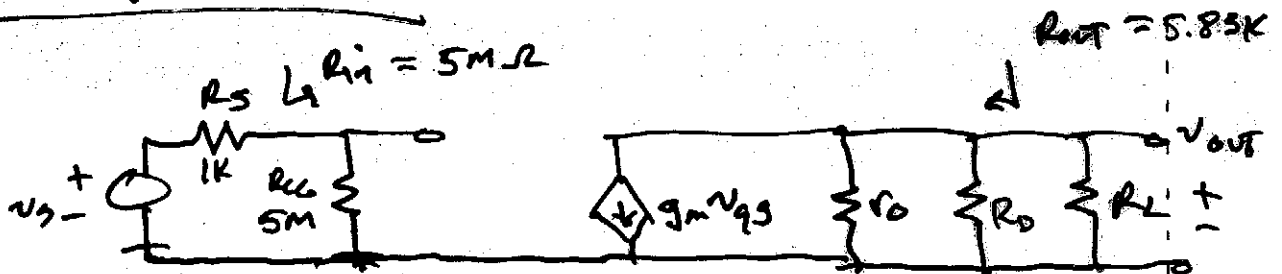

$$\underline{A_v} = \left(\frac{v_{gs}}{v_s} \right) \left(\frac{v_{out}}{v_{gs}} \right) = -2.44 \text{ V/V}$$