
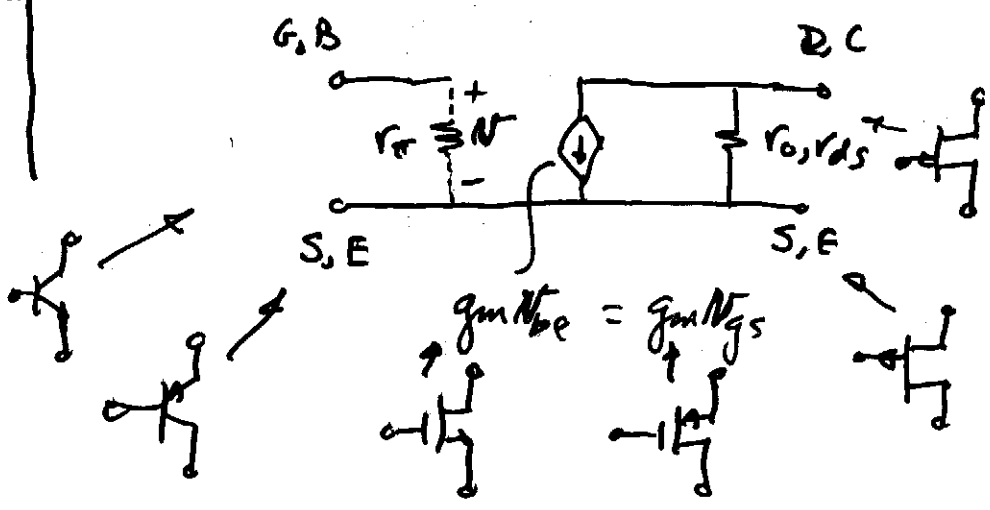


BJT and FET Amplifiers

	BJT	MOSFET	JFET
Large Signal Model	$i_C = I_S \exp \frac{V_{BE}}{V_T} \times (1 + \frac{V_{CE}}{V_A})$	$i_D = \frac{K'}{2L} (V_{GS} - V_T)^2 \times (1 + \lambda V_{DS})$	$i_D = I_{DSS} (1 - \frac{V_{GS}}{V_P})^2 \times (1 + \lambda V_{DS})$
Small-signal model parameters	$g_m = \frac{I_C}{V_T}$ $r_o = \frac{V_A + V_{CE}}{I_C}$ $r_{\pi} = \frac{\beta}{g_m}$	$g_m = \sqrt{2K' \frac{W}{L} I_D} (1 + \lambda V_{DS})$ $r_{ds} = \frac{V_{DS} + \frac{1}{\lambda}}{I_D}$	$g_m = \frac{2}{ V_P } \sqrt{I_{DSS} \cdot I_D} (1 + \lambda V_{DS})$ $r_{ds} = \frac{V_{DS} + \frac{1}{\lambda}}{I_D}$

Small-signal model

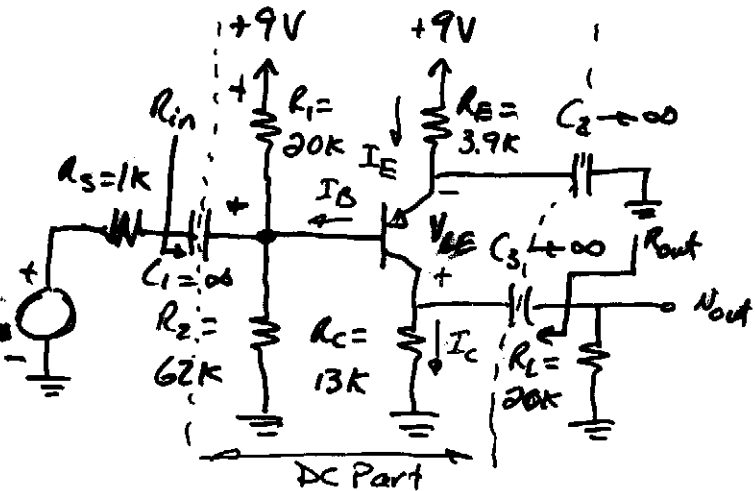

Example 3If $\beta_F = 135$ and $V_A = 100V$, find $\frac{N_{out}}{N_{in}}$, R_{in} , R_{out} 

a.) Find Q point

$$V_{BE} \approx 0.7V$$

$$V_{BB} = 9 \frac{R_2}{R_1 + R_2} = -9 \frac{R_1}{R_1 + R_2} = -9 \frac{20}{82} = -2.195V, R_{BB} = 20k \parallel 62k = 15.12k$$

Treat as if NPN -

$$V_{BB} = I_B R_{BB} + V_{BE} + (1 + \beta_F) I_B R_E$$

$$2.195 = I_B [15.12k + (136) 3.9k] + 0.7$$

$$I_B = \frac{2.195 - 0.7}{15.12k + 136 \times 3.9k} = 2.75\mu A = 7 I_C = 0.37mA$$

$$V_{EC} = 9 - I_C R_C = I_E R_E \quad I_E = 0.373mA$$


$$V_{EC} = 9 - 4.81 - 1.459 = 2.736V$$

b.) Calculate s.s. model parameters

$$g_m = \frac{I_C}{V_T} = \frac{0.37mA}{25mV} = 14.8mS, r_\pi = \frac{135}{14.8mS} = 9.12k$$

$$r_o = \frac{100 + 2.736}{0.37mA} = 278k$$

c.)

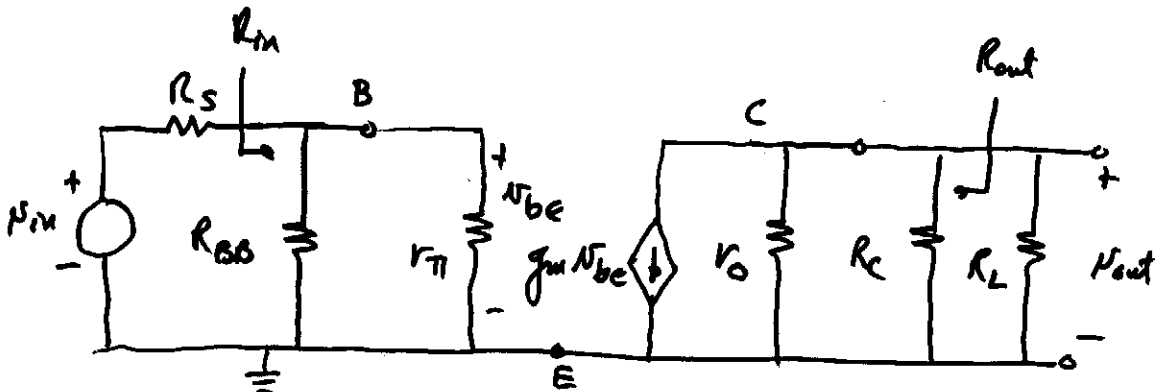

$$R_{in} = R_{BB} \parallel r_{\pi} = \underline{5.689k}$$

$$R_{out} = r_o \parallel R_C = \underline{12.42k}$$

$$\frac{v_{out}}{v_{in}} = \left(\frac{v_{out}}{v_{be}} \right) \left(\frac{v_{be}}{v_{in}} \right)$$

$$= \left(-g_m \times r_o \parallel R_C \parallel R_L \right) \left(\frac{r_{\pi} \parallel R_{BB}}{R_S + r_{\pi} \parallel R_{BB}} \right)$$

$$= \left(-0.0145 \times 7.662k \right) \left(\frac{5.689}{6.689} \right) = \underline{-96.44 V/V}$$

Example 4


If $I_{BSS} = 5\mu A$,

$V_p = -5V$, and

$\lambda = \frac{1}{50V}$ find

R_{in} , R_{out} , and

$$\frac{v_{out}}{v_{in}}$$

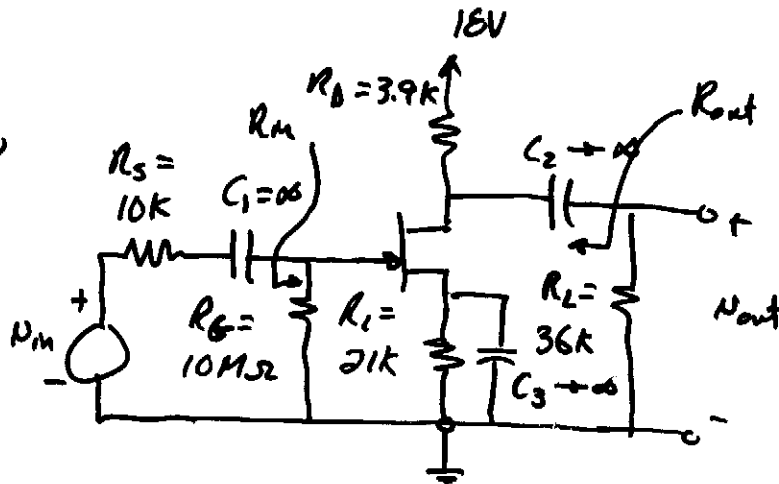

$$R_{in} = 10M\Omega$$

$$R_{out} = 3.61k\Omega$$

$$\frac{v_{out}}{v_{in}} = -3.605 V/V$$