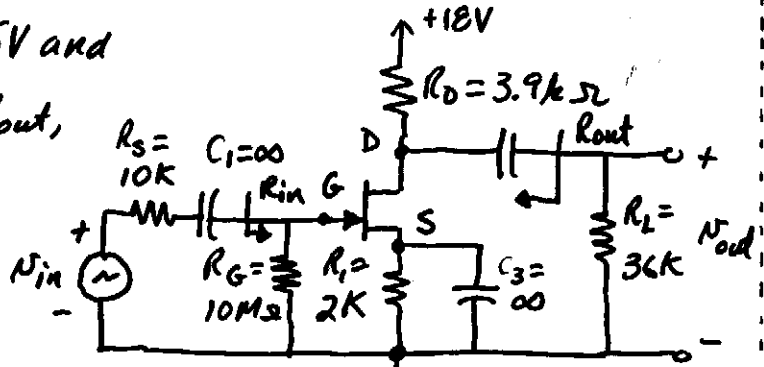


Example 4 - JFET Common Source Amplifier

If $I_{DSS} = 5\text{mA}$, $V_p = -5\text{V}$ and $\lambda = \frac{1}{50\text{V}}$, find R_{in} , R_{out} , and $\frac{N_{out}}{N_{in}}$.




a.) Find the Q-point.

$$0 = V_{GS} + I_S R_1 \rightarrow V_{GS} = -I_S R_1 = -I_D R_1 \rightarrow N_{GS} = -i_D R_1$$

$$0 = \frac{I_D}{\beta} R_G + V_S + I_D R_1 \rightarrow I_D \approx I_{DSS} \left(1 - \frac{N_{GS}}{V_p}\right)^2$$

$$N_{GS} = -R_1 \left[I_{DSS} \left(1 - \frac{N_{GS}}{V_p}\right)^2 \right] \rightarrow N_{GS}^2 + 12.5 N_{GS} + 25 = 0$$

$$V_{GS} = -6.25 \pm 3.75$$

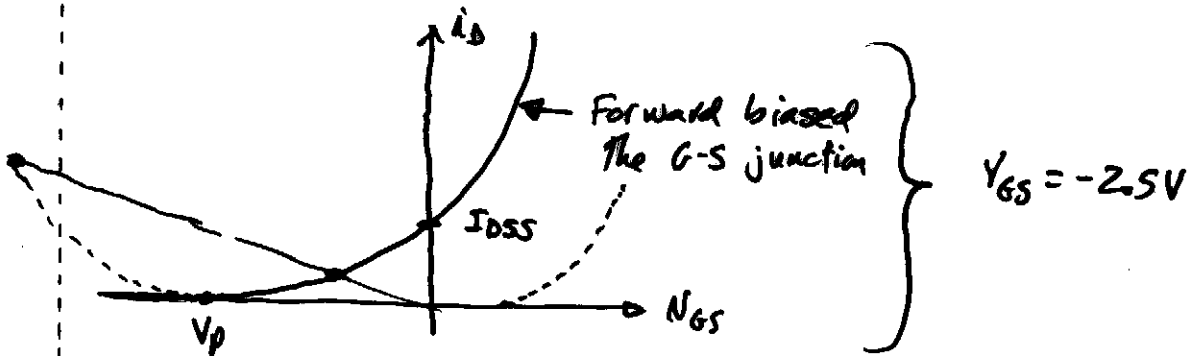

How do you relate a JFET to a MOSFET-


$$i_D = I_{DSS} \left(1 - \frac{N_{GS}}{V_p}\right)^2 = \frac{I_{DSS}}{V_p^2} \left(V_p - N_{GS}\right)^2 = \frac{I_{DSS}}{V_p^2} \left(N_{GS} - V_p\right)^2$$

$$i_{D\text{MOSFET}} = \frac{K'W}{2L} (N_{GS} - V_T)^2$$

$$\therefore \frac{I_{DS}}{V_p^2} = \frac{K'W}{2L} \text{ and } V_p = V_T$$

You cannot forward bias the G-S junction for a JFET

JFET Cont'd

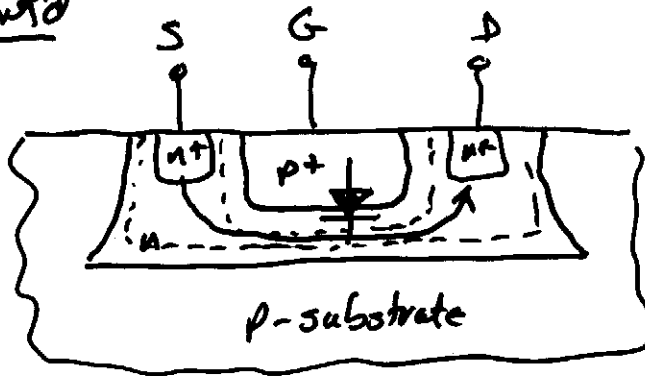

Back to Example -

$$I_D = 5\text{mA} \left(1 - \frac{-2.5}{-5}\right)^2 = 1.25\text{mA} \quad V_{DS} = 18 - 1.25\text{mA}(5.9\text{k})$$

$$V_{DS} = 10.6\text{V}$$

Saturation -

$$V_{DS} \geq V_{GS} - V_P = -2.5 - (-5) = 2.5$$


b.) Small parameter calculation

$$g_m = \frac{2}{|V_P|} \sqrt{I_{DSS} I_D (1 + \lambda V_{DS})} = \frac{2}{5\text{V}} \sqrt{5\text{mA} \cdot 1.25\text{mA} \left(1 + \frac{10.6}{30}\right)}$$

$$= 1.1\text{mS}$$

$$r_o = r_{ds} = \frac{1}{\lambda} + \frac{V_{DS}}{I_D} = \frac{50 + 10.6}{2.5\text{mA}} = 48.5\text{k}\Omega$$

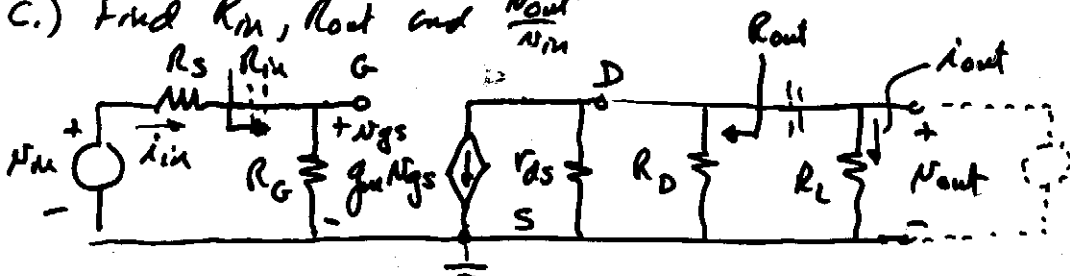c.) Find R_{in} , R_{out} and $\frac{N_{out}}{N_{in}}$



$$R_{in} = R_G = 10\text{M}\Omega$$

$$R_{out} = r_{ds} \parallel R_D = 3.61\text{k}\Omega$$


$$\frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{N_{gs}}\right) \left(\frac{N_{gs}}{N_{in}}\right) = (-g_m r_{ds} \parallel R_D \parallel R_L) \left(\frac{R_G}{R_S + R_G}\right)$$

$$= (-1.1 \cdot 3.28) \left(\frac{10}{10 + 0.01}\right) = -3.605\text{V/V}$$

$$\frac{i_{out}}{i_{in}} = \frac{N_{out}/R_L}{N_{in}/(R_S + R_G)} = \frac{N_{out}}{N_{in}} \left(\frac{R_S + R_G}{R_L}\right)$$

Table 13.5

Signal Flow in Transistors

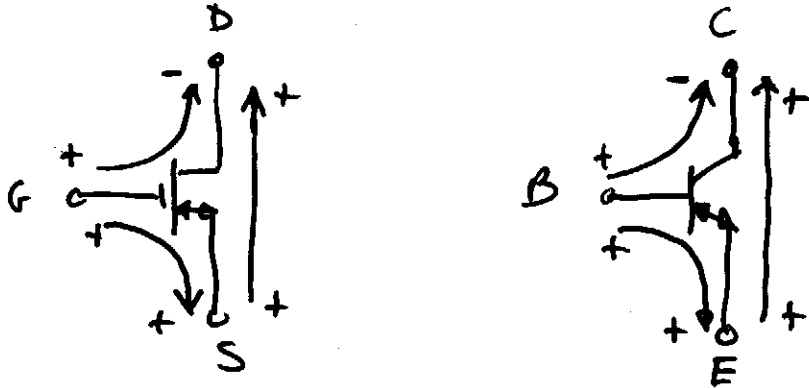

- 1.) You can't apply a signal to the D or C.
- 2.) You can't take an output from the B or G.
- 3.) Signals invert when going from B to C or G to D.

Inverting Amplifier with Unbypassed source resistor

