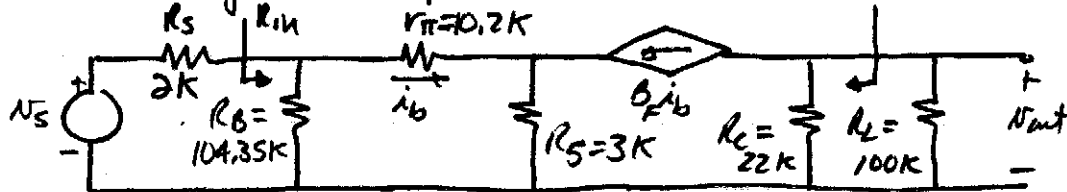


LECTURE 16

1.) Inverting CE Amplifier - Continued




$$R_{in} = R_B \parallel [r_{\pi} + (1+\beta_F)R_E] = 104.35k \parallel 313.2k = \underline{\underline{78.3k\Omega}}$$

$$R_{out} \approx R_C = \underline{\underline{22k\Omega}}$$

$$\frac{N_{out}}{N_s} = \left(\frac{N_{out}}{i_b}\right) \left(\frac{i_b}{N_s}\right) \quad \frac{N_{out}}{i_b} = -g_m(R_C \parallel R_L)$$

$$i_b = \frac{N_s}{R_s + R_{in}} \times \frac{R_B}{R_B + r_{\pi} + (1+\beta_F)R_E}$$

$$\begin{aligned} \therefore \frac{N_{out}}{N_s} &= \frac{-\beta_F(R_C \parallel R_L)R_B}{(R_s + R_{in})[R_B + r_{\pi} + (1+\beta_F)R_E]} \\ &= \frac{-100(18.03k)(104.35k)}{(80.3k)[104.35k + 313.2k]} = \underline{\underline{-5.61 V/V}} \end{aligned}$$

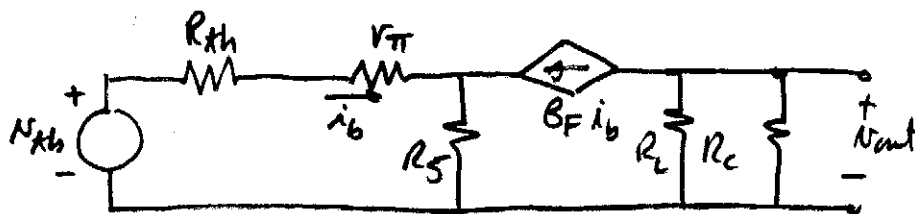
Text: calculates $\frac{N_{out}}{N_{th}}$ What is the difference?

$$R_{th} = R_s \parallel R_B = 1.96k\Omega \approx R_s$$

$$N_{th} = \frac{R_B}{R_s + R_B} N_s = \frac{104.35}{106.35} N_s \approx N_s$$


$$\frac{N_{out}}{N_{th}} = \frac{-\beta(R_C \parallel R_L)}{R_{th} + r_{\pi} + (1+\beta_F)R_E} = \frac{-1803k}{(1.96 + 10.2 + 303)k} = -5.72 V/V$$

Common Drain Amplifier (Source follower)

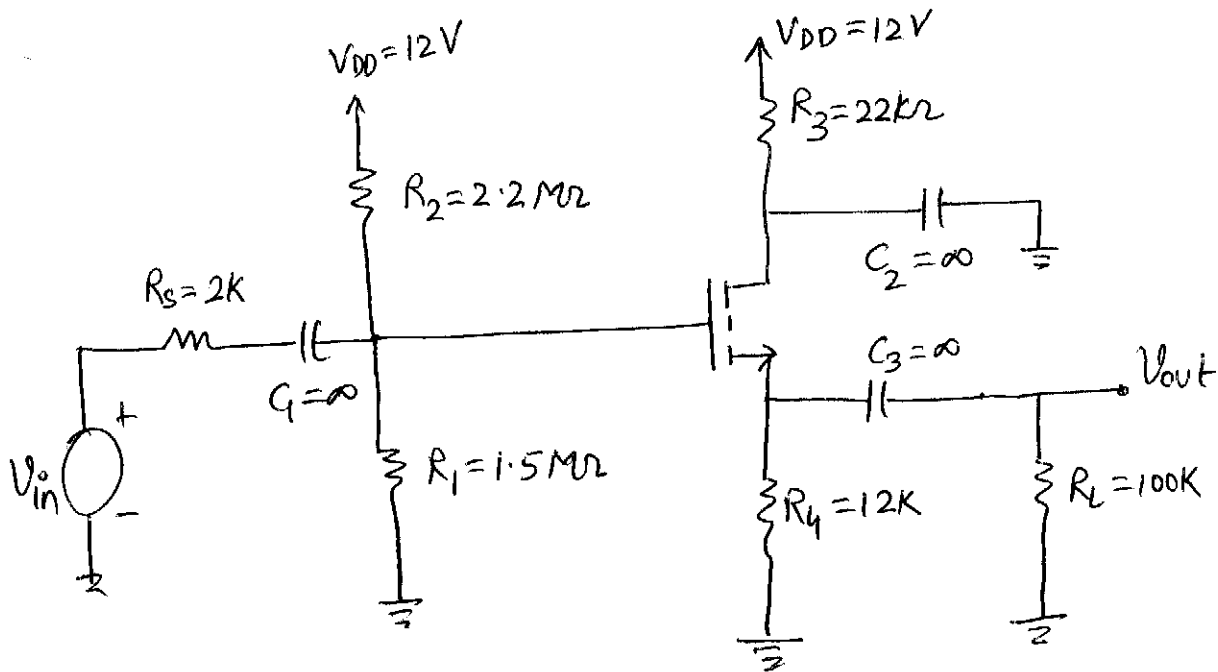

Q point $\Rightarrow I_{DS} = 241 \mu A, V_{DS} = 3.81 V$


Small-signal model

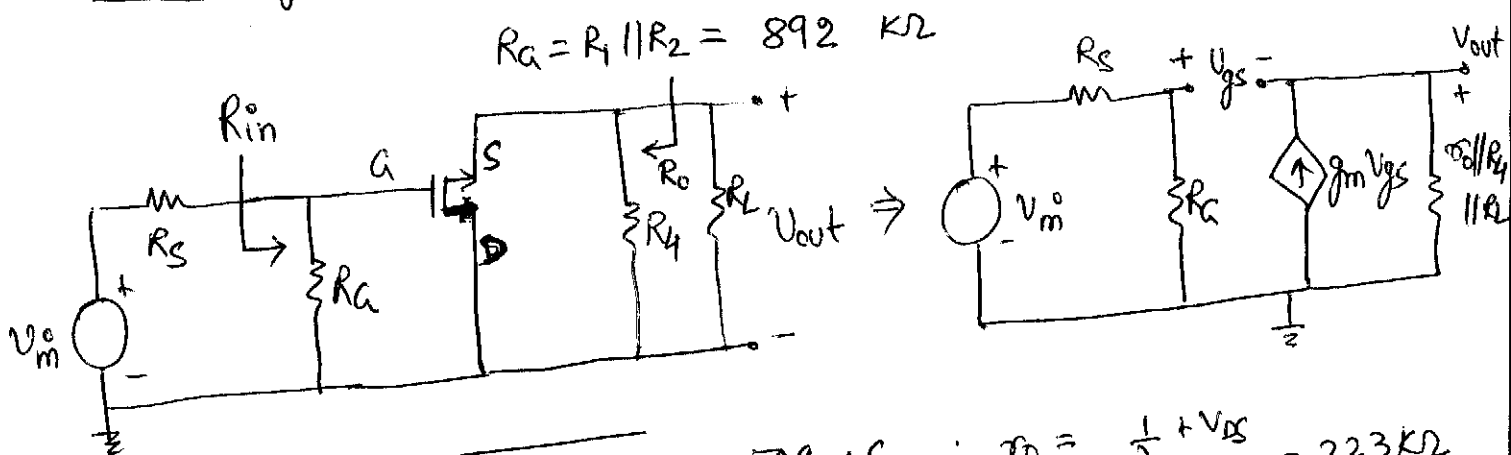

$$g_m = \sqrt{2k_n I_{DS} (1 + \lambda V_{DS})} = 509 \mu S ; r_o = \frac{1}{\lambda} + \frac{V_{DS}}{I_{DS}} = 223 k\Omega$$

$$\underline{\underline{R_{in}}} = R_a = 892 k\Omega$$

$$\underline{\underline{R_{out}}} = ??$$

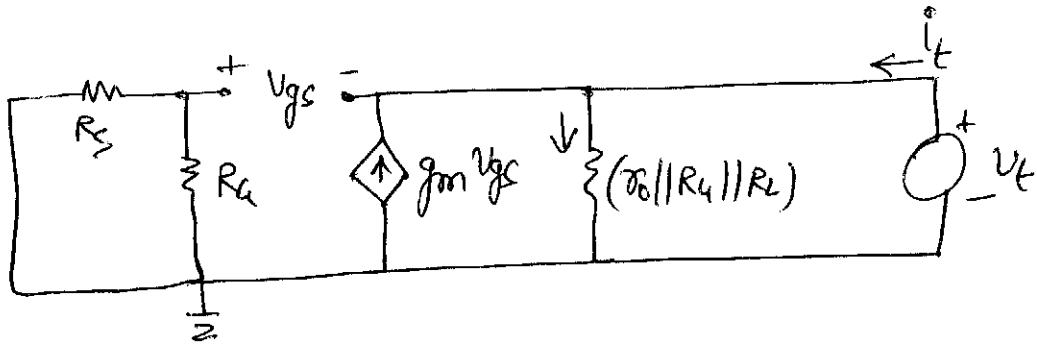


$$V_g = 0, V_s = V_t \Rightarrow V_{gs} = -V_t$$

$$g_m V_{gs} + i_t = \frac{V_t}{(r_o \parallel R_4 \parallel R_L)} = V_t \left(\frac{1}{r_o} + \frac{1}{R_4} + \frac{1}{R_L} \right)$$

$$\text{or, } -g_m V_t + i_t = V_t \left(\frac{1}{r_o} + \frac{1}{R_4} + \frac{1}{R_L} \right)$$

$$\text{or } R_{in} = \frac{V_t}{i_t} = \frac{1}{\left(g_m + \frac{1}{r_o} + \frac{1}{R_4} + \frac{1}{R_L} \right)} \approx \frac{1}{g_m} = 1.96 \text{ k}\Omega$$

$$\frac{V_{out}}{V_m^o} = ??$$

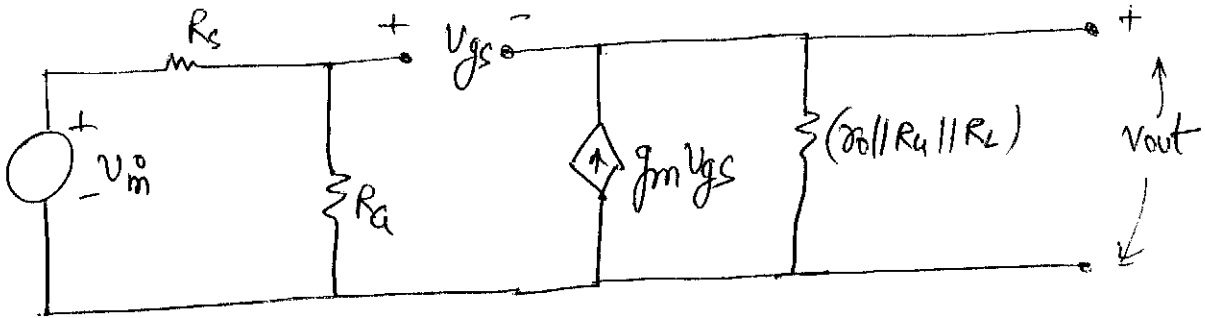

$$\frac{V_{out}}{V_m^o} = \left(\frac{V_{out}}{V_{gs}} \right) \left(\frac{V_{gs}}{V_m^o} \right)$$

$$\left(\frac{V_{out}}{V_{gs}} \right) = \left\{ g_m (r_o \parallel R_4 \parallel R_L) \right\}$$

$$\left(\frac{V_{gs}}{V_m^o} \right) = ??$$



$$V_{gs} = V_g - V_s = \left(\frac{R_g}{R_g + R_s} \right) V_m^o - \left\{ g_m V_{gs} (r_o \parallel R_4 \parallel R_L) \right\}$$

$$V_{gs} \left[1 + g_m (r_o \parallel R_4 \parallel R_L) \right] = \frac{R_g}{R_g + R_s} V_m^o$$

$$\frac{V_{gs}}{V_m^o} = \frac{R_g}{(R_g + R_s) \left\{ 1 + g_m (r_o \parallel R_4 \parallel R_L) \right\}}$$

$$\frac{V_{out}}{V_m^o} = \left(\frac{R_g}{R_g + R_s} \right) \cdot \left[\frac{g_m (r_o \parallel R_4 \parallel R_L)}{1 + g_m (r_o \parallel R_4 \parallel R_L)} \right] = 0.837.$$

Common Collector (Emitter Follower)

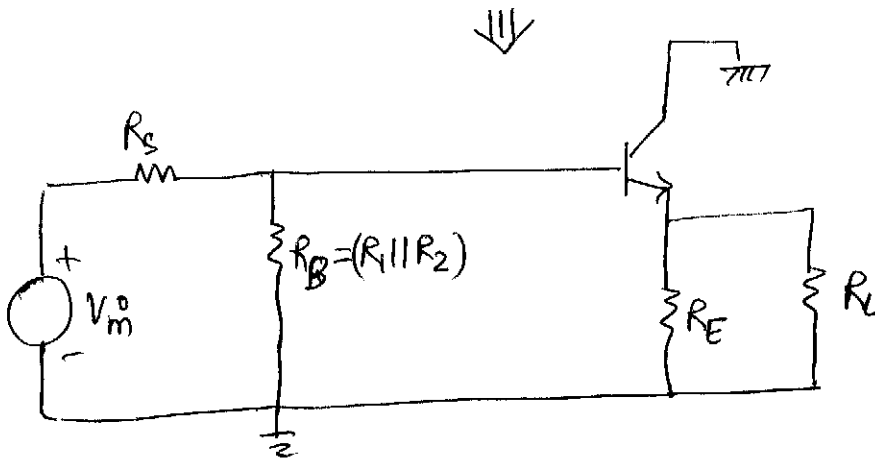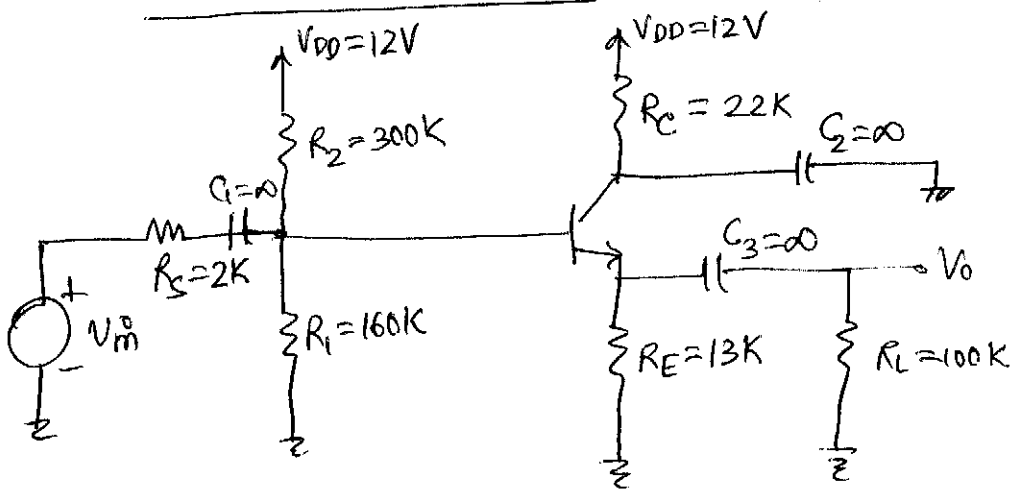

$$R_B = R_1 || R_2 = 104.35 \text{ K}$$

Q point:


$$I_C = 245 \mu\text{A}$$

$$V_{CE} = 3.64 \text{ V}$$

$$g_m = \frac{I_C}{V_T} = 9.8 \text{ mS}; \quad r_{\pi} = \frac{\beta F}{g_m} = 10.2 \text{ k}\Omega$$


$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{103.64}{245 \mu\text{A}} = 423 \text{ k}\Omega$$

Small-signal model

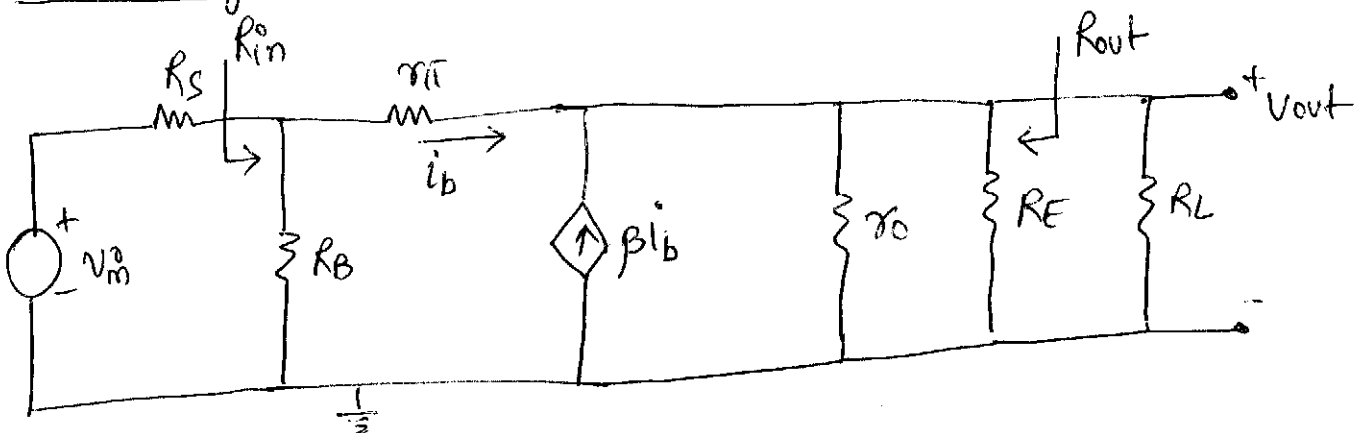

R_{in}

$$\begin{aligned}
 R_{in} &= R_B \parallel \left\{ r_{\pi} + (1 + \beta_F)(r_o \parallel R_E \parallel R_L) \right\} \\
 &= 104.35K \parallel \left\{ 10.2K + (101)(11.2K) \right\} \\
 &= \underline{\underline{95.6K\Omega}}
 \end{aligned}$$

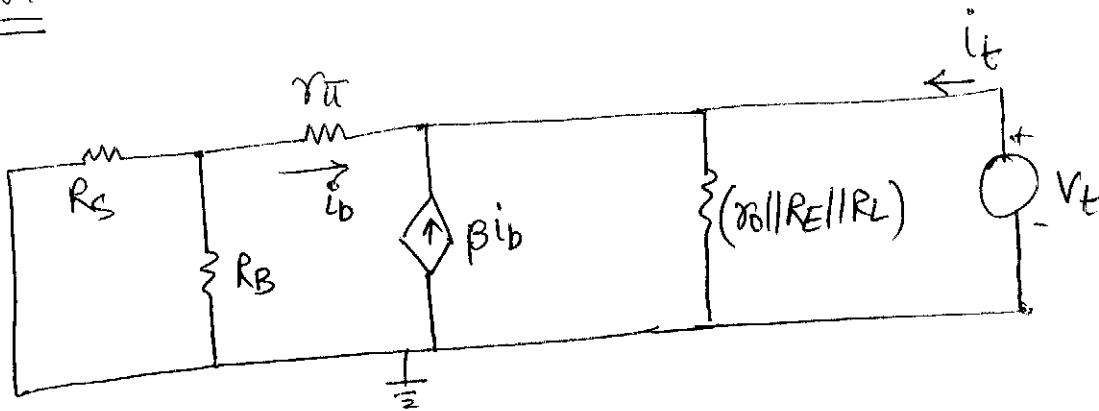 R_{out} 

$$i_t + i_b + \beta i_b = \frac{V_t}{(r_o \parallel R_E \parallel R_L)}$$

$$i_t + (1 + \beta_F) i_b = V_t \left(\frac{1}{r_o} + \frac{1}{R_E} + \frac{1}{R_L} \right)$$

$$i_b = \frac{-V_t}{\{r_{\pi} + (R_S \parallel R_B)\}}$$

$$i_t - \frac{(1 + \beta_F) V_t}{\{r_{\pi} + (R_S \parallel R_B)\}} = V_t \left(\frac{1}{r_o} + \frac{1}{R_E} + \frac{1}{R_L} \right)$$

$$i_t = V_t \left[\frac{1}{r_o} + \frac{1}{R_E} + \frac{1}{R_L} + \frac{(1 + \beta_F)}{\{r_{\pi} + (R_S \parallel R_B)\}} \right]$$