
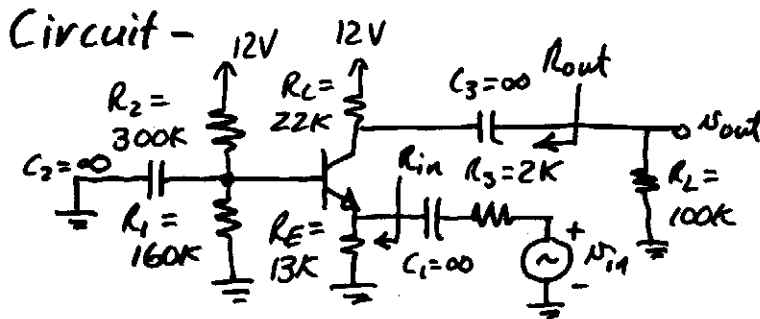



Common Base Amplifier

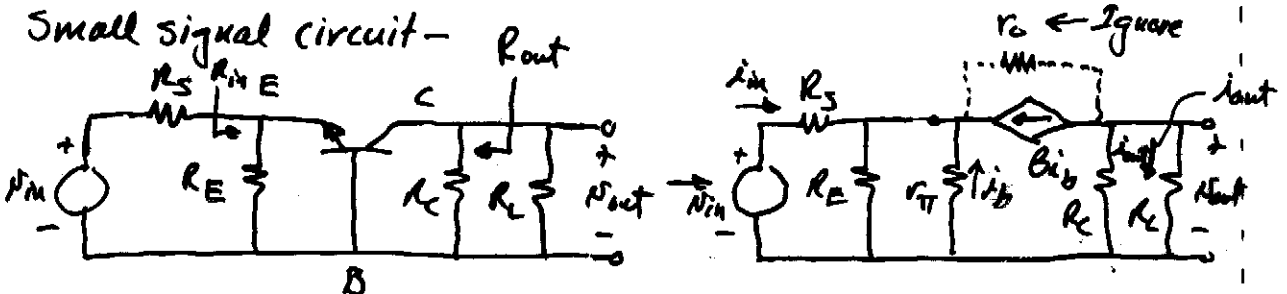

If $\beta_F = 100$ and $V_A = 50V$ find R_{in} , R_{out} , and $\frac{V_{out}}{V_{in}}$ if $I_C = 245\mu A$ and $V_{CE} = 3.4V$



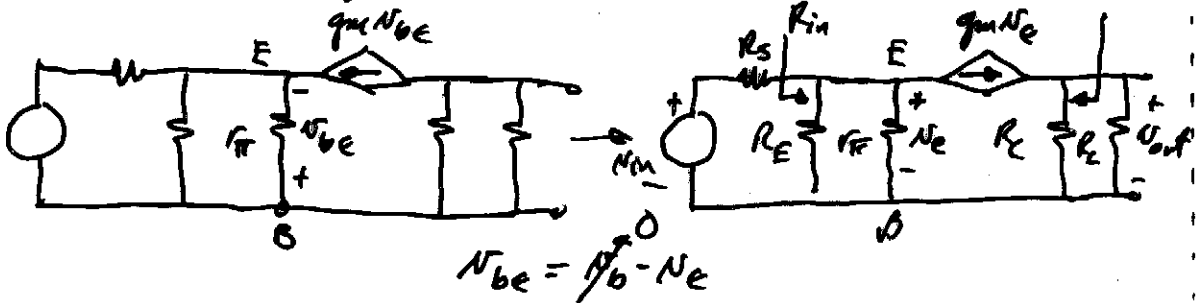
For the heck of it, lets control the source by N_{be} .



$$g_m = \frac{I_C}{V_T} = \frac{245\mu A}{25mV} = 9.8mS, \quad r_{\pi} = \beta \frac{1}{g_m} = 10.2k\Omega \quad (r_o = 204k\Omega)$$

$$R_M = R_E \parallel \frac{r_{\pi}}{1+\beta} = R_E \parallel \frac{1}{g_m} = 13k \parallel 102\Omega = \underline{\underline{101\Omega}}$$

$R_{out} = ?$

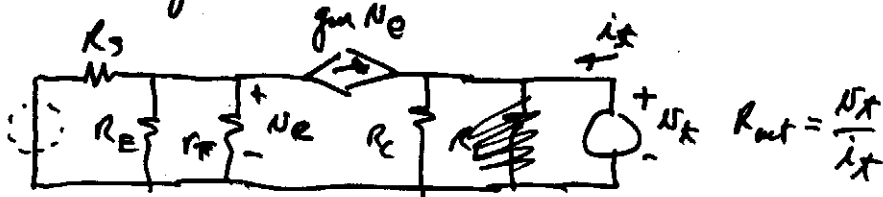

If $r_o = \infty$, then $R_{out} = R_C = 22k$

If $r_o \neq \infty$,

$$R_{out} = \left[r_o + (r_{\pi} \parallel R_E \parallel R_S) (1 + g_m r_o) \right] \parallel R_C = 3.16M\Omega \parallel 22k\Omega$$

CB Amplifier - Cont'd


$$\frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{N_E} \right) \left(\frac{N_E}{N_{in}} \right) = [+ g_m (R_C || R_L)] \left[\frac{R_{in}}{R_S + R_{in}} \right] = (9.8 \times 18) \left(\frac{0.101}{2.101} \right)$$

$$\frac{N_{out}}{N_{in}} = \underline{\underline{8.48 \text{ V/V}}}$$

$$\frac{i_{out}}{i_{in}} = \frac{(V_{out}/R_L)}{V_{in}} = \frac{N_{out}}{N_{in}} \times \frac{R_S + R_{in}}{R_L}$$

$$\frac{i_{out}}{i_{in}} = 8.48 \left(\frac{2.01}{100} \right) = ?$$


Common Gate Amplifier

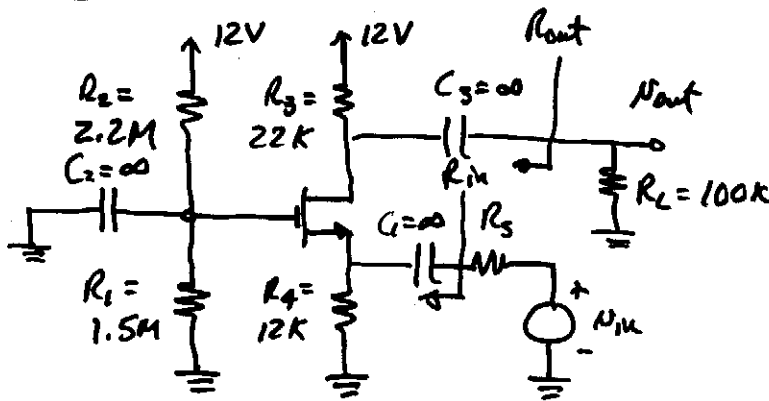

If $K_n = 500 \mu\text{A/V}^2$
 $V_{TN} = 1\text{V}$
 $\lambda = 0.02 \text{V}^{-1}$
 Find R_{in} , R_{out}
 and $\frac{N_{out}}{N_{in}}$

$I_{DQ} = 241 \mu\text{A}$
 $V_{DS} = 3.8\text{V}$


Small-signal model-

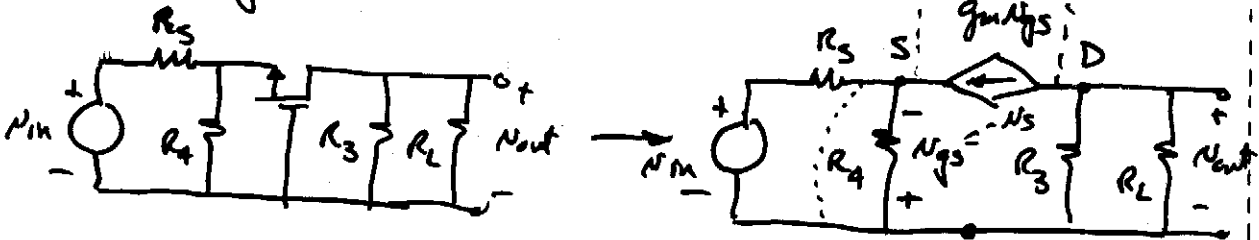

$$g_m = \sqrt{2K_n \frac{W}{L} I_D} = \sqrt{2 \cdot 500 \cdot 1 \cdot 241} \mu\text{S} = 509 \mu\text{S}$$

$$r_{ds} = \frac{1}{\lambda + V_{DS}} = \frac{1}{0.02 + 3.8} = 225 \text{ k}\Omega$$

$$R_{in} = \frac{N_x}{i_x}$$

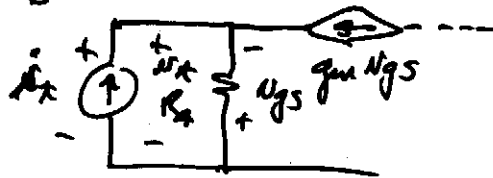

$$\sum i = 0$$

$$i_x = \frac{N_x}{R_1} + g_m N_x$$

$$i_x = -\frac{N_{gs}}{R_1} - g_m N_{gs}$$

$$N_x = -N_{gs}$$

CG Amplifier - Cont'd

$$R_{in} = \frac{v_x}{i_x} = \frac{1}{\frac{1}{R_t} + g_m} = \frac{1}{g_m} \parallel R_t \approx \frac{1}{g_m} \approx \underline{\underline{1.96k\Omega}}$$

$$R_{out}(r_{ds} = \infty) = R_3 = 22k\Omega$$

$$\begin{aligned} \frac{v_{out}}{v_{in}} &= \left(\frac{v_{out}}{v_{gs}} \right) \left(\frac{v_{gs}}{v_{in}} \right) = \left(-g_m \times R_3 \parallel R_c \right) \left(-\frac{R_{in}}{R_s + R_{in}} \right) \\ &= (-.509 \times 18) \left(\frac{-1.96k}{2k + 1.96k} \right) = +4.54 \text{ V/V} \end{aligned}$$

$$R_{out}(r_{ds} \neq \infty) = \underbrace{\left[r_o + (R_3 \parallel R_t)(1 + g_m r_{ds}) \right]}_{416k\Omega} \parallel R_c \quad 22k$$