
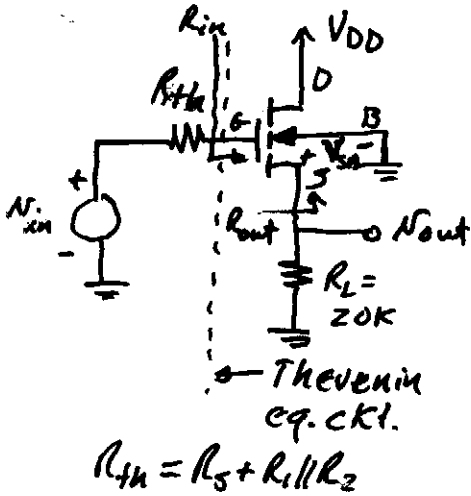


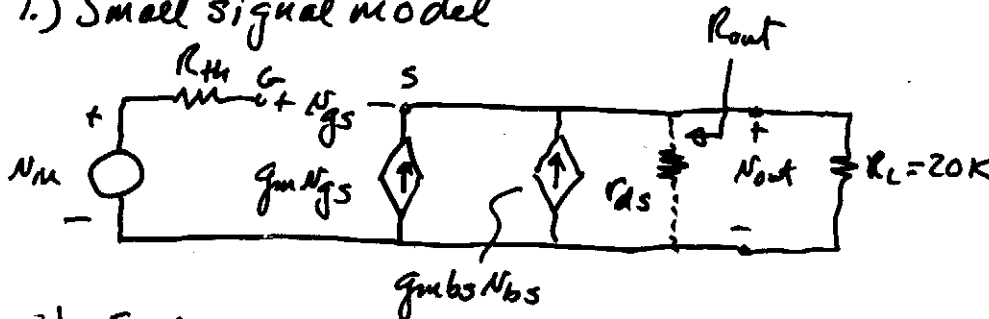Source Follower with Bulk Effect ($V_{BS} \neq 0$)



Find $\frac{N_{out}}{N_{in}}$, R_{in} , & R_{out}
 if $K_n = 500 \mu A/V^2$, $V_{TN} = 1V$, $\lambda = 0$
 $\gamma = 0.75 V^{1/2}$ and $2\phi_F = 0.6V$
 Also, $I_{D5} = 241 \mu A$ & $V_0(OC) = 5V$.
 $\frac{5V}{20K} \approx 0.25 \mu A \approx 241 \mu A$

1.) Small signal model




2.) Find g_m , g_{mbs} , and $r_{ds} = \infty$.


$$g_m = \sqrt{2K_n I_D} = \sqrt{2 \cdot 500 \cdot 241} = 491 \mu S$$

$$g_{mbs} = \frac{g_m \gamma}{2 \sqrt{V_{SB} + 2\phi_F}} = \frac{(491 \mu S)(0.75)}{2 \sqrt{5 + 0.6}} = 77.8 \mu S$$

Everything is positive

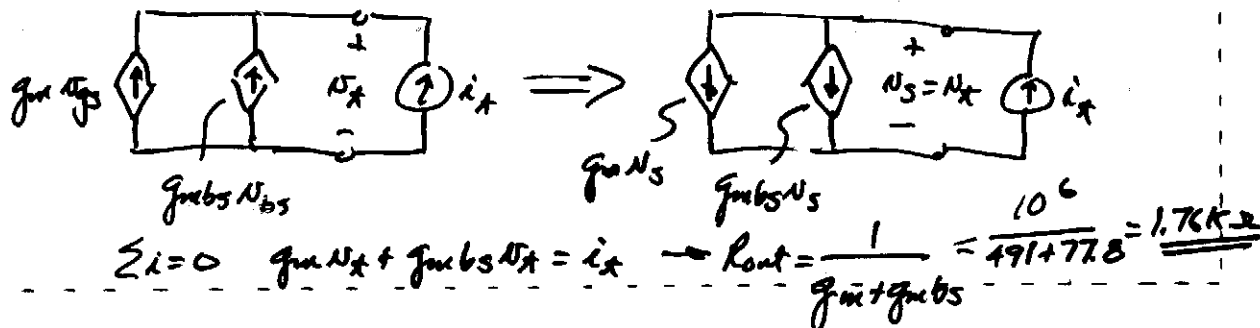3.) $R_{in} = \infty$, $R_{out} = ?$ ($N_{in} = 0 \Rightarrow N_G = 0$) $\Rightarrow N_{GS} = -N_S$



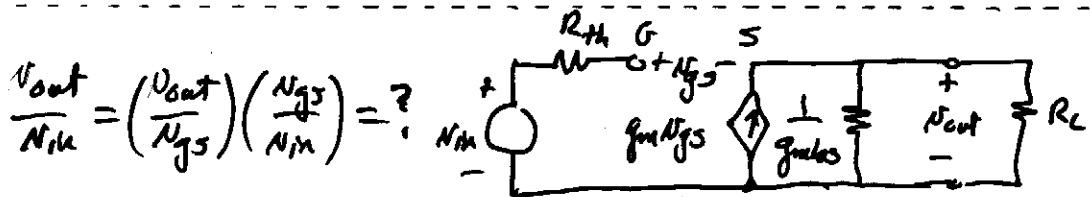

$$\frac{V_{out}}{N_{in}} = \left(\frac{V_{out}}{N_{gs}} \right) \left(\frac{N_{gs}}{N_{in}} \right) = ?$$

$$= \left[g_m \left(\frac{1}{g_m b_s} \parallel R_L \right) \right] \left[\frac{1}{1 + g_m \left(R_L \parallel \frac{1}{g_m b_s} \right)} \right]$$

$$N_{gs} = N_g - N_s = N_{in} - g_m \left(R_L \parallel \frac{1}{g_m b_s} \right) N_{gs}$$

$$N_{gs} \left[1 + g_m \left(R_L \parallel \frac{1}{g_m b_s} \right) \right] = N_{in}$$

$$\frac{R_L \frac{1}{g_m b_s}}{R_L + \frac{1}{g_m b_s}} = \frac{R_L}{1 + g_m b_s R_L}$$


$$\frac{V_{out}}{N_{in}} = \frac{g_m R_L}{1 + g_m b_s R_L} = \frac{g_m R_L}{1 + g_m R_L + g_m b_s R_L} = \frac{(0.491)(20)}{1 + (0.491 \times 20) + (0.0777 \times 20)}$$

$$= \frac{9.82}{12.38} = \underline{\underline{0.793 V/V}}$$

Question -




$$g_m b_s N_s = -g_m b_s N_s$$

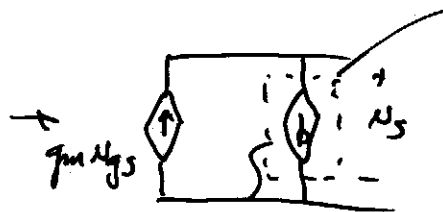

$$g_m b_s N_s$$


$$\frac{N_s}{g_m b_s N_s} = \frac{1}{g_m b_s}$$

Common Gate JFET Amplifier

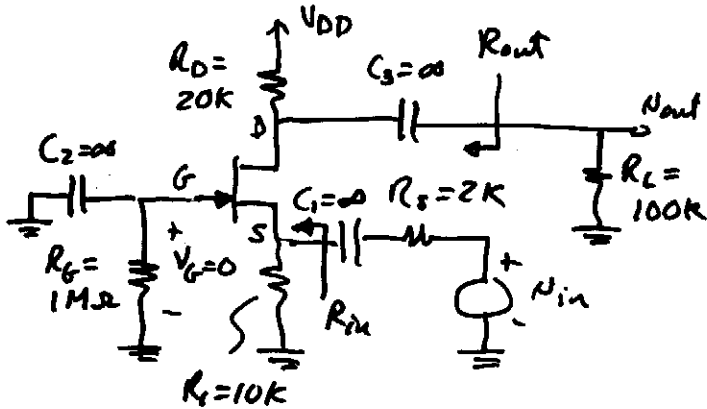

If $I_{DS} = 1\text{mA}$ and $I_{DSS} = 5\text{mA}$, $V_p = -2\text{V}$ and $\lambda = 0$, find R_{in} , R_{out} , and $\frac{N_{out}}{N_{in}}$.

1.) Small-signal model

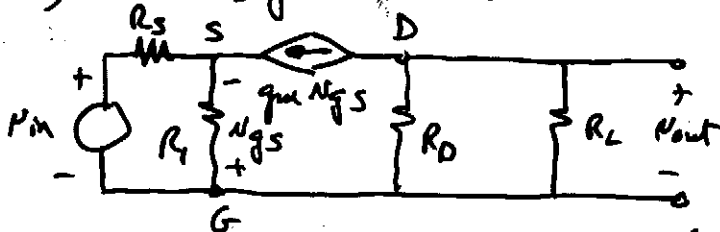


$$i_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p}\right)^2$$

$$g_m = \frac{\partial i_D}{\partial V_{GS}} \Big|_Q$$

2.)
$$g_m = \frac{2}{|V_p|} \sqrt{I_{DS} I_{DSS} (1 + \lambda V_{DS})} = \frac{2}{2} \sqrt{5 \cdot 1} = 2.236\text{mS}$$

 $r_{ds} = \infty$

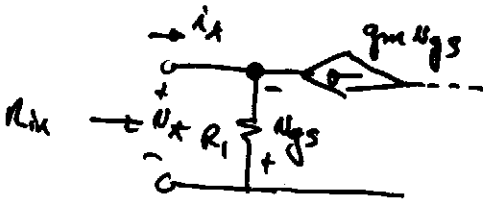3.) $R_{out} = R_D = 20\text{k}$ $R_{in} = ?$



$$i_x + \frac{V_{gs}}{R_g} + g_m V_{gs} = 0$$

But $V_{gs} = -V_x$

$$\therefore i_x = \frac{V_x}{R_g} + g_m V_x \implies \frac{V_x}{i_x} = R_{in} = \frac{1}{g_m + \frac{1}{R_g}} = \frac{1}{g_m} \parallel R_g = \underline{428\Omega}$$

$$\frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{V_{gs}}\right) \left(\frac{V_{gs}}{N_{in}}\right) = (-g_m R_D \parallel R_L) \left(\frac{-R_{in}}{R_s + R_{in}}\right)$$

$$= [-2.236(20 \parallel 100)] \left[\frac{-428}{2428}\right] \approx (-37.27) \left(\frac{-1}{6}\right) \approx \underline{+6\text{ V/V}}$$

Common Noting