

Ex. 14.6 - Cont'd

Design of a buffer.

3.) Range of I_D ?

$R_S = 3K\Omega \rightarrow g_m = 3.72mS$

in order to get a gain of 0.85

$g_m = \sqrt{2K_N I_{D5}} \rightarrow K_N I_{D5} = \frac{g_m^2}{2} = 7.13 \times 10^{-6}$

K_N generally varies from 0.1 to 20 mA/V²

If we choose $K_N = 10 \text{ mA/V}^2$, then $I_{D5} = 0.714 \mu\text{A}$

Choose $I_{D5} = \underline{1 \mu\text{A}}$

4.)

$V_S = 1 \mu\text{A} \times 3K = 3V$


$K_N = 10 \text{ mA/V}^2$ and

$V_{TN} = 1$, then

$V_{GS} = \sqrt{\frac{2I_{D5}}{K_N}} + V_{TN}$

$\frac{N_{out}}{N_{in}} = \frac{g_m R_S || R_L}{1 + g_m R_S || R_L}$

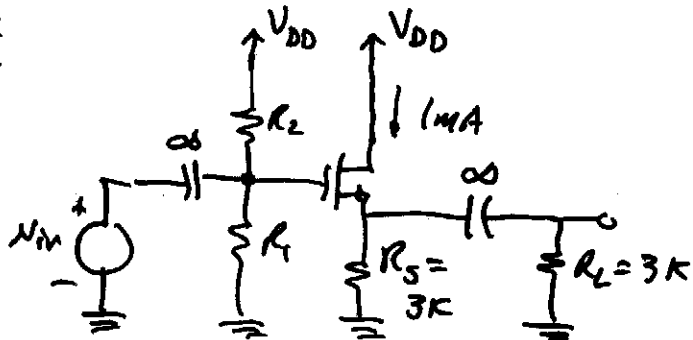$V_{GS} = \sqrt{\frac{2 \cdot 1 \mu\text{A}}{10 \text{ mA/V}^2}} + 1 = 1.45V \rightarrow V_G = V_S + V_{GS} = 4.45V$




5.) Design R_1 , R_2 and V_{DD}


$R_G = R_1 || R_2 \geq 20M\Omega \quad V_G = V_{DD} \frac{R_1}{R_1 + R_2}$

Assume $R_1 = R_2 = 40M\Omega \rightarrow V_{DD} = 2V_G = 8.9V$

Select $V_{DD} = 9V$

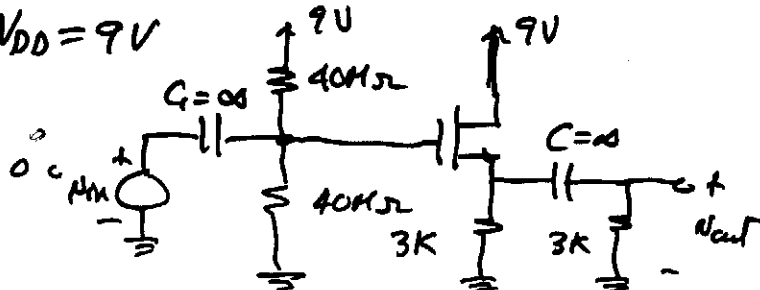


What if the amplifier was $R_{in} \geq 20k\Omega$ and $\frac{V_{out}}{V_{in}} = +10 \frac{V}{V}$?

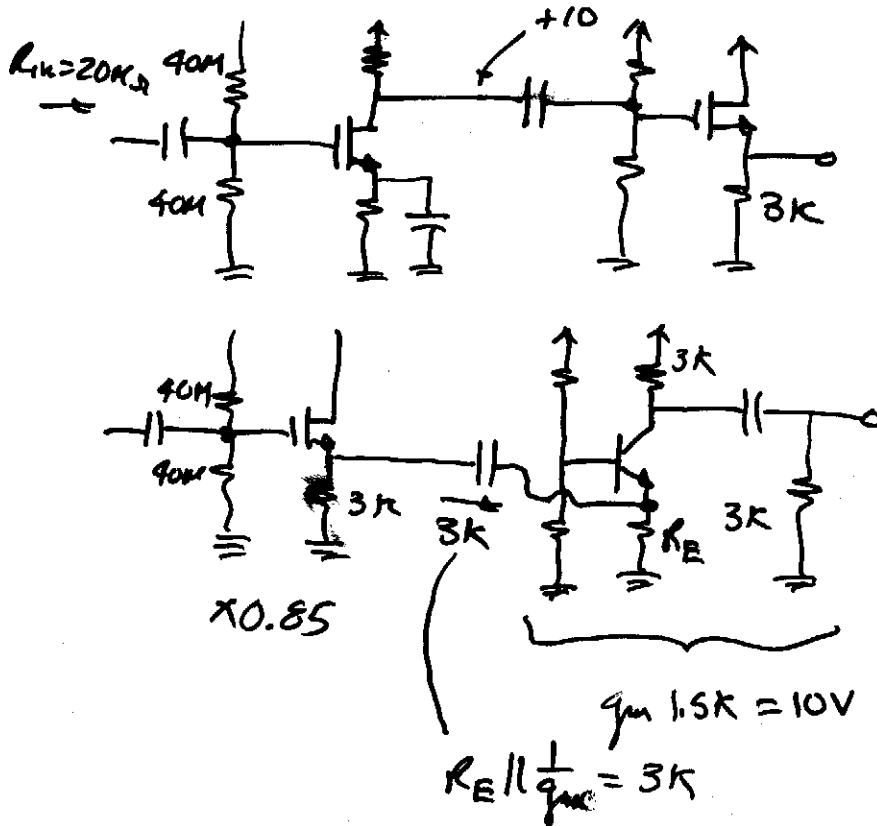

Chapter 15 - Multistage Amplifiers

Using more than 1 transistor gives additional flexibility in meeting a set of amplifier specs.

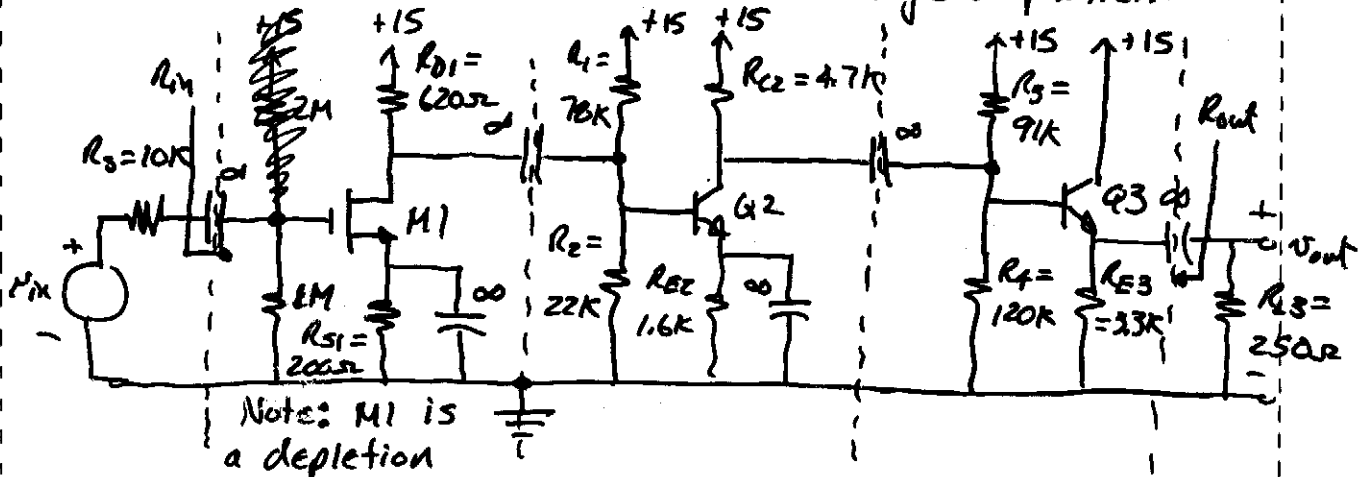Example CS-CE-CC → Good Voltage amplifier.



Voltage Amplifier - Cont'd

M1: $K_N = 10 \text{ mA/V}^2$, $V_{TN} = -2 \text{ V}$, $\lambda = 0.02 \text{ V}^{-1}$

Q2: $\beta_F = 150$, $V_{A2} = 80 \text{ V}$, $V_{BE} = 0.6 \text{ V}$

Q3: $\beta_F = 80$, $V_{A3} = 60$, $V_{BE} = 0.6 \text{ V}$

Q points & small-signal model parameters -


M1: $I_{D1} = 5 \text{ mA}$, $V_{D1} = 10.9 \text{ V} \rightarrow g_{m1} = 10 \text{ mS}$ & $r_{o1} = 12.2 \text{ k}\Omega$

Q2: $I_{C2} = 1.57 \text{ mA}$, $V_{CE2} = 5.09 \text{ V} \rightarrow g_{m2} = 62.8 \text{ mS}$
 $r_{\pi 2} = 2.39 \text{ k}\Omega$
 $r_{o2} = 54.2 \text{ k}\Omega$


Q3: $I_{C3} = 1.97 \text{ mA}$, $V_{CE3} = 8.96 \text{ V} \rightarrow g_{m3} = 79.6 \text{ mS}$
 $r_{\pi 3} = 1 \text{ k}\Omega$
 $r_{o3} = 34.4 \text{ k}\Omega$

AC analysis -

Simplified AC ckt:

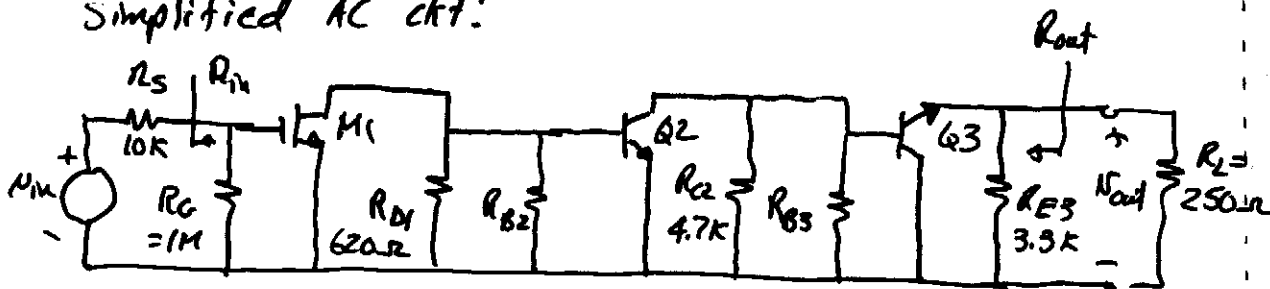

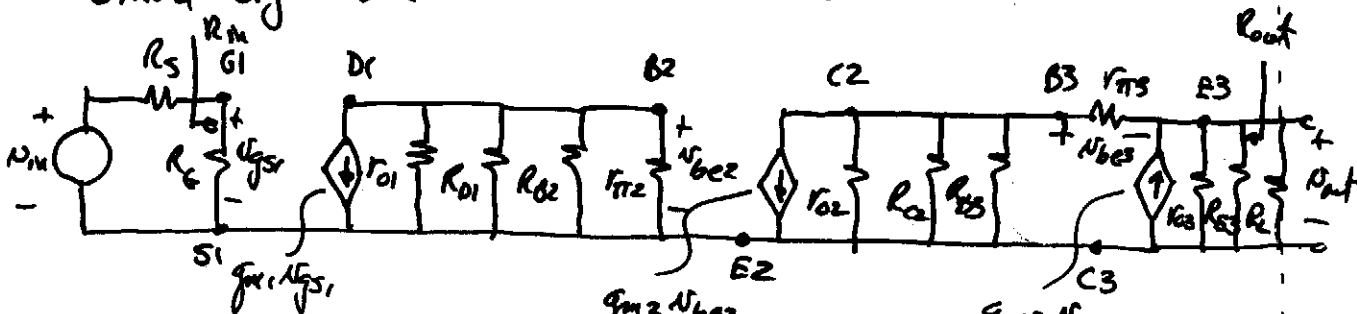Small-sig. model - $R_{B2} = 17.1 \text{ k}\Omega$ $R_{B3} = 51.75 \text{ k}\Omega$



$R_{in} = R_G = 1 \text{ M}\Omega$

$R_{out} = R_{E3} \parallel r_{o3} \parallel \left(\frac{r_{\pi 3} + r_{o2} \parallel R_{C2} \parallel R_{B3}}{1 + \beta_3} \right) = 60.4 \Omega$