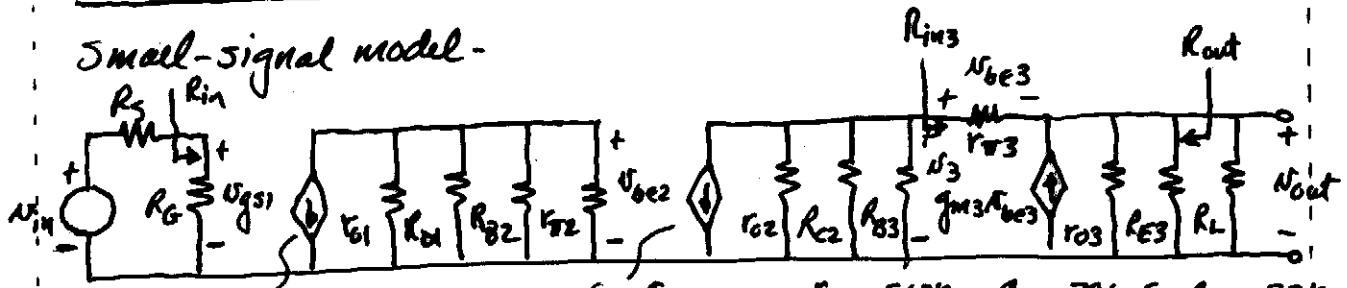


Voltage Amplifier Example - Continued

Small-signal model -




$R_S = 10k$ $g_{m1} = 10ms$ $r_{\pi 1} = 122k$ $g_{m2} = 62.8ms$ $r_{\pi 2} = 2.39k\Omega$ $r_{\pi 3} = 34.4k$
 $R_G = 1M$ $g_{m1} = 10ms$ $R_{D1} = 620\Omega$ $g_{m2} = 62.8ms$ $R_{C2} = 4.7k$ $r_{\pi 3} = 1k$ $R_{E3} = 3.3k$
 $R_{B2} = 17.16k$ $r_{\pi 2} = 2.39k\Omega$ $R_{B3} = 51.75k$ $r_{\pi 3} = 34.4k$

Find r_{in} , R_{out} and $\frac{N_{out}}{N_{in}}$.

$r_{in} = R_G = 1M\Omega$

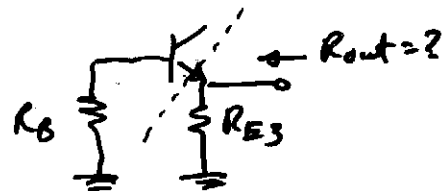$R_{out} = R_{E3} \parallel r_{\pi 3} \parallel \left[\frac{r_{\pi 3} + R_{B3} \parallel R_{C2} \parallel r_{\pi 2}}{1 + \beta_3} \right]$



$R_{out} = R_{E3} \parallel \frac{r_{\pi 3} + R_B}{1 + \beta}$

$= 3.3k \parallel 34.4k \parallel \left[\frac{1k + 51.75k \parallel 4.7k \parallel 54.2k}{81} \right] = 60.4\Omega$

$\frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{N_{be3}} \right) \left(\frac{N_{be3}}{N_3} \right) \left(\frac{N_3}{N_{be2}} \right) \left(\frac{N_{be2}}{N_{gs1}} \right) \left(\frac{N_{gs1}}{N_{in}} \right)$

$\frac{N_{out}}{N_{be3}} = \left(g_{m3} + \frac{1}{r_{\pi 3}} \right) \left[r_{\pi 3} \parallel R_{E3} \parallel R_L \right] = (1 + \beta_3) \frac{r_{\pi 3} \parallel R_{E3} \parallel R_L}{r_{\pi 3}}$
 $\approx \beta_3 \left(\frac{R_{E3} \parallel R_L}{r_{\pi 3}} \right) = 81 \left(\frac{232}{1000} \right) = 18.82$

$\frac{N_{be3}}{N_3} = \frac{r_{\pi 3}}{R_{in3}} = \frac{r_{\pi 3}}{r_{\pi 3} + (1 + \beta_3) [r_{\pi 3} \parallel R_{E3} \parallel R_L]} = \frac{1k}{19.82k} = \frac{1}{19.82}$

$\frac{N_3}{N_{be2}} = -g_{m2} \left[r_{\pi 2} \parallel R_{C2} \parallel R_{B3} \parallel R_{in3} \right] = -62.8 (3.322) = -208.6$

$\frac{N_{be2}}{N_{gs1}} = -g_{m1} \left[r_{\pi 1} \parallel R_{D1} \parallel R_{B2} \parallel r_{\pi 2} \right] = (-10) (0.475) = -4.756$

$\frac{N_{gs1}}{N_{in}} = \frac{R_G}{R_S + R_G} = \left(\frac{1}{1.01} \right)$

$\frac{N_{out}}{N_{in}} = (18.82) \left(\frac{1}{19.82} \right) (-208.6) (-4.756) \left(\frac{1}{1.01} \right) = 938.6 \text{ V/V}$

Voltage Amplifier Example - Cont'd

Current gain:

$$\frac{i_{out}}{i_{in}} = \frac{\frac{N_{out}}{R_{L3}}}{\frac{N_{in}}{R_{s+R_{in}}}} = \left(\frac{N_{out}}{N_{in}}\right) \left(\frac{R_{s+R_{in}}}{R_{L3}}\right) = \underline{3.79 \times 10^6 \text{ A/A}}$$

Power gain:

$$\frac{P_{out}}{P_{in}} = \left(\frac{N_{out}}{N_{in}}\right) \left(\frac{i_{out}}{i_{in}}\right) = 3.56 \times 10^9 \text{ W/W}$$

Input signal range:

How large can N_{in} be and still be small signal?

MOSFETS $N_{gs1} \leq 0.2 (V_{GS} - V_T)$

BJT $N_{be} \leq 5 \text{ mV}$

Stage 1 -

$$N_{gs1} \leq 0.2 (V_{GS1} - V_{TN}) = 0.2 (-1 \text{ V} + 2) = 0.2 \text{ V}$$

$$\text{max } N_{in} \approx 200 \text{ mV}$$

Stage 2 -

$$N_{be2} \leq 5 \text{ mV} \rightarrow N_{in(\text{max})} = \frac{5 \text{ mV}}{\text{Gain}}$$

* Gain from output of stage to amplifier input

$$N_{in(\text{max})} = \frac{5 \text{ mV}}{4.786} = 1.06 \text{ mV}$$

Stage 3 -

$$N_{be3} < 5 \text{ mV} \rightarrow N_{in(\text{max})}$$


$$N_{in(\text{max})} = \frac{5 \text{ mV}}{\left(\frac{N_{be3}}{N_3}\right) \left(\frac{N_3}{N_{be2}}\right) \left(\frac{N_{be2}}{N_{gs1}}\right) \left(\frac{N_{gs1}}{N_{in}}\right)} = 0.1 \text{ mV}$$

To keep the voltage in small-signal conditions

$$N_{in(\text{max})} = 100 \text{ } \mu\text{A} \rightarrow N_{out} = \underline{98.4 \text{ mV}}$$


Comments on Sec. 15.2

1.) Direct coupled amplifiers.

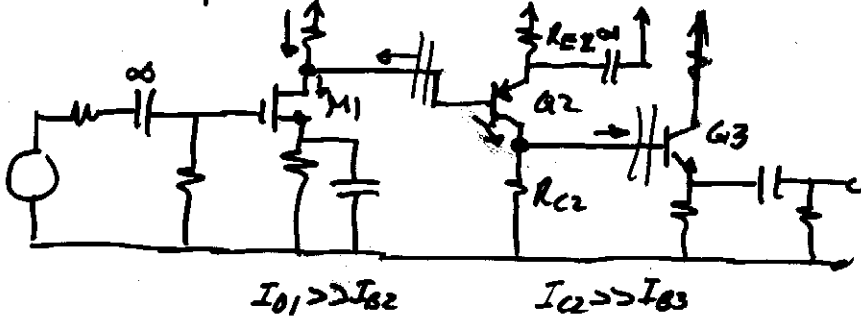

$I_{O1} \gg I_{B2}$ $I_{C2} \gg I_{B3}$


2.) Darlington Configuration

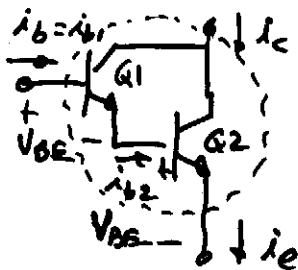

$$i_c = i_{c1} + i_{c2} = \beta_1 i_{b1} + \beta_2 i_{b2}$$

$$= \beta_1 i_b + \beta_2 (1 + \beta_1) i_b \approx \beta_2 (1 + \beta_1) i_b$$
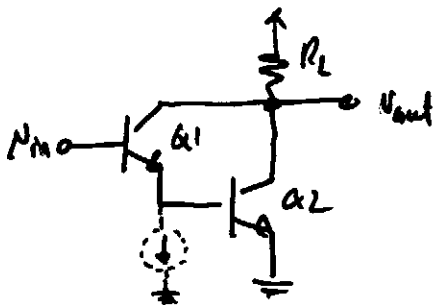
$$i_c = \beta_{eff} i_b \rightarrow \beta_{eff} = \beta_2 (1 + \beta_1)$$



$$R_m = r_{\pi 1} + (1 + \beta_1) r_{\pi 2} = \frac{N_{in}}{i_b}$$

$$N_{out} = -\beta_{eff} R_L i_b$$

$$\frac{N_{out}}{N_{in}} = \frac{-\beta_2 (1 + \beta_1) R_L}{r_{\pi 1} + (1 + \beta_1) r_{\pi 2}} \approx \frac{-\beta_2 (1 + \beta_1) R_L}{2 r_{\pi 1}}$$

$$r_{\pi 1} = \frac{\beta_1 V_T}{I_{C1}} \quad \text{and} \quad r_{\pi 2} = \frac{\beta_2 V_T}{I_{C2}} = \frac{\beta_2 V_T}{\beta_1 I_{C1}} \approx \frac{1}{g_m}$$

Sec. 15.3

Diff. amps.

Quiz 06