


$$\underline{A_{vd}} = \frac{v_{o1}}{v_{id}} = -\frac{g_m R_C}{2} \Rightarrow \underline{v_{o1}} = -\underline{g_m R_C} \frac{v_{id}}{2}$$

$$\underline{R_{in}} = r_{\pi} \quad \underline{R_{id}} = \frac{v_{id}}{i_b} = \frac{v_{id}}{\frac{v_{id}}{2r_{\pi}}} = \underline{2r_{\pi}}$$

$$\underline{R_{od}} = 2(R_C \parallel R_o)$$

$$v_{o1} = -g_m R_C \frac{v_{id}}{2}$$

MOSFET




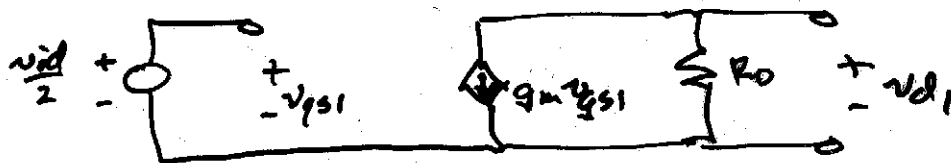


$$\underline{v_{o1}} = -g_m R_o \frac{v_{gs}}{2} = -\underline{g_m R_o} \frac{v_{id}}{2}$$

$$\underline{A_{vd}} = \frac{v_{o1}}{v_{id}} = -\frac{g_m R_o}{2} \Rightarrow \underline{v_{o1}} = -\underline{g_m R_o} \frac{v_{id}}{2}$$

$$\underline{R_{id}} = \infty$$
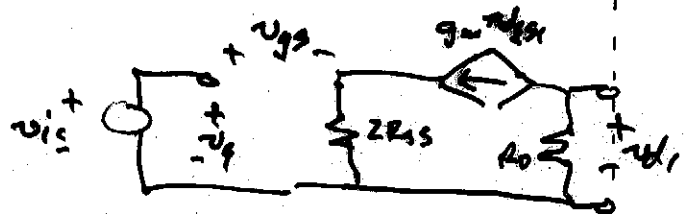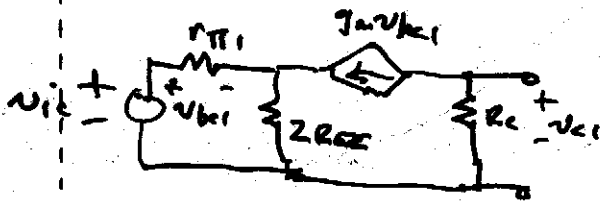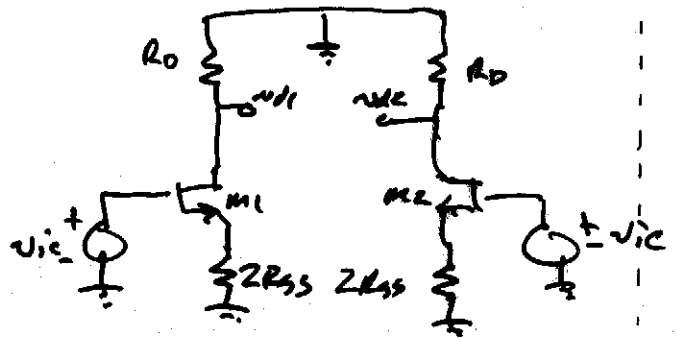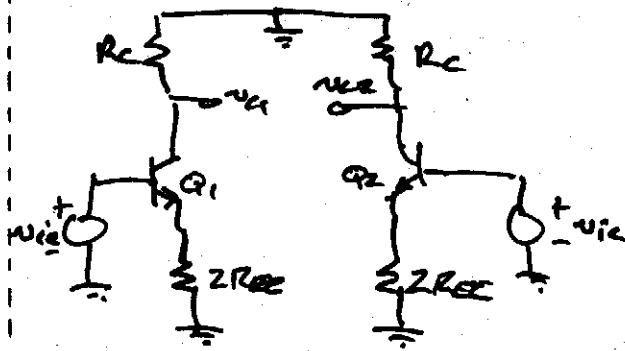
$$\underline{R_{od}} = 2(R_o \parallel R_o)$$



$$A_{od} = \frac{v_{od}}{v_{ic}} = \frac{v_{ce1}}{v_{be1}} \frac{v_{be1}}{v_{ic}}$$

$$A_{od} = \frac{v_{od}}{v_{ic}} = \frac{v_{ds1}}{v_{gs1}} \frac{v_{gs1}}{v_{ic}}$$

$$v_{be1} = v_{b1} - v_{e1} = v_{ic} - 2R_{EE} \left(\frac{1}{r_{\pi 1}} + g_m \right) v_{be1}$$

$$v_{gs} = v_{ic} - g_m 2R_{SS} v_{gs}$$

$$\frac{v_{be1}}{v_{ic}} = \frac{1}{1 + \frac{2R_{EE}}{r_{\pi 1}} (1 + \beta_1)}$$

$$\frac{v_{gs}}{v_{ic}} = \frac{1}{1 + 2g_m R_{SS}}$$

$$\therefore \frac{v_{ce1}}{v_{ic}} = \frac{-g_m R_c}{1 + \frac{2R_{EE}}{r_{\pi 1}} (1 + \beta_1)}$$

$$\therefore A_{od} = \frac{g_m R_D}{1 + 2g_m R_{SS}}$$

$$R_{ic} = \infty$$

$$A_{od} = \frac{-\beta_1 R_c}{r_{\pi 1} + (1 + \beta_1) 2R_{EE}}$$

$$CMRR = \frac{|A_{od}|}{|A_{oc}|} = \frac{g_m R_D / 2}{\frac{2R_D}{1 + 2g_m R_{SS}}}$$



$$R_{ic} = \frac{v_{ic}}{i_{ib}} = \frac{r_{\pi 1} + (1 + \beta) 2R_{EE}}{2}$$

$$\Rightarrow \underline{CMRR} \approx g_m R_{SS}$$





$$CMRR = \frac{|A_{od}|}{|A_{oc}|} = \frac{g_m R_c}{2\beta_1 R_c} \left[r_{\pi 1} + (1 + \beta) 2R_{EE} \right]$$

$$CMRR = \frac{1}{2} + \frac{(1 + \beta) R_{EE}}{r_{\pi 1}} \approx \underline{g_m R_{EE}}$$

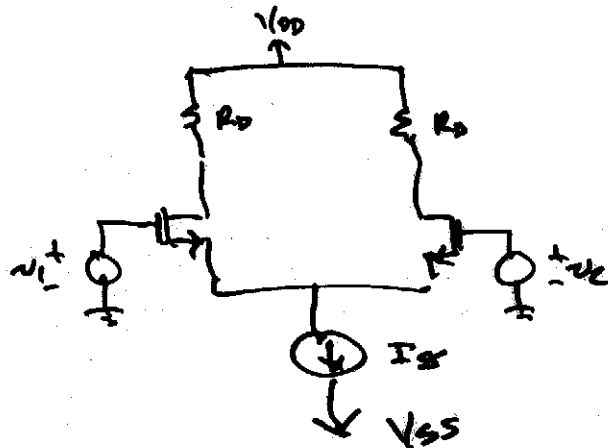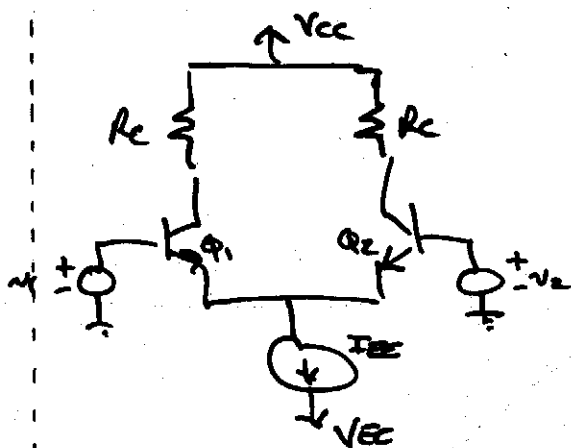CURRENT SINK BIASING OF DIFFERENTIAL AMPS



AC circuit

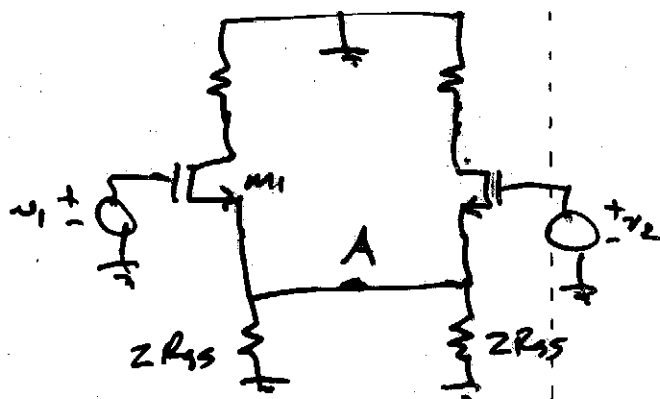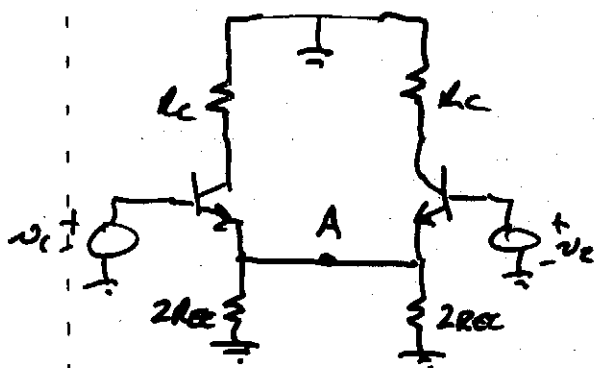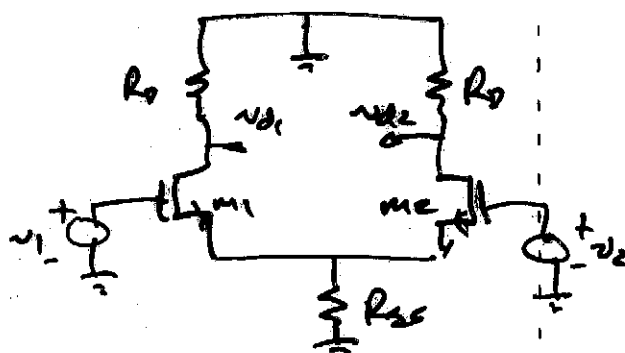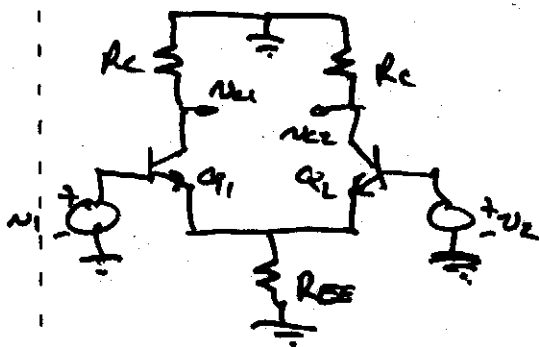

- FOR DIFF. MODE ANALYSIS (v_{id}), ground 'A' node and repeat previous analysis
- FOR COMMON MODE ANALYSIS (v_{ic}), cut the connection at 'A' and repeat previous analysis for half-circuits.


CH. 1717.1 Amplifier Frequency Response

$$A_v(s) = \frac{a_0 + a_1 s + a_2 s^2 + \dots + a_n s^n}{b_0 + b_1 s + b_2 s^2 + \dots + b_n s^n}$$

$$= A_{mid} F_L(s) F_H(s)$$

$$F_L(s) = \frac{(s + \omega_{z1}^L)(s + \omega_{z2}^L) \dots (s + \omega_{zk}^L)}{(s + \omega_{p1}^L)(s + \omega_{p2}^L) \dots (s + \omega_{pk}^L)}$$

$$F_H(s) = \frac{(1 + \frac{s}{\omega_{z1}^H})(1 + \frac{s}{\omega_{z2}^H}) \dots (1 + \frac{s}{\omega_{zk}^H})}{(1 + \frac{s}{\omega_{p1}^H})(1 + \frac{s}{\omega_{p2}^H}) \dots (1 + \frac{s}{\omega_{pk}^H})}$$

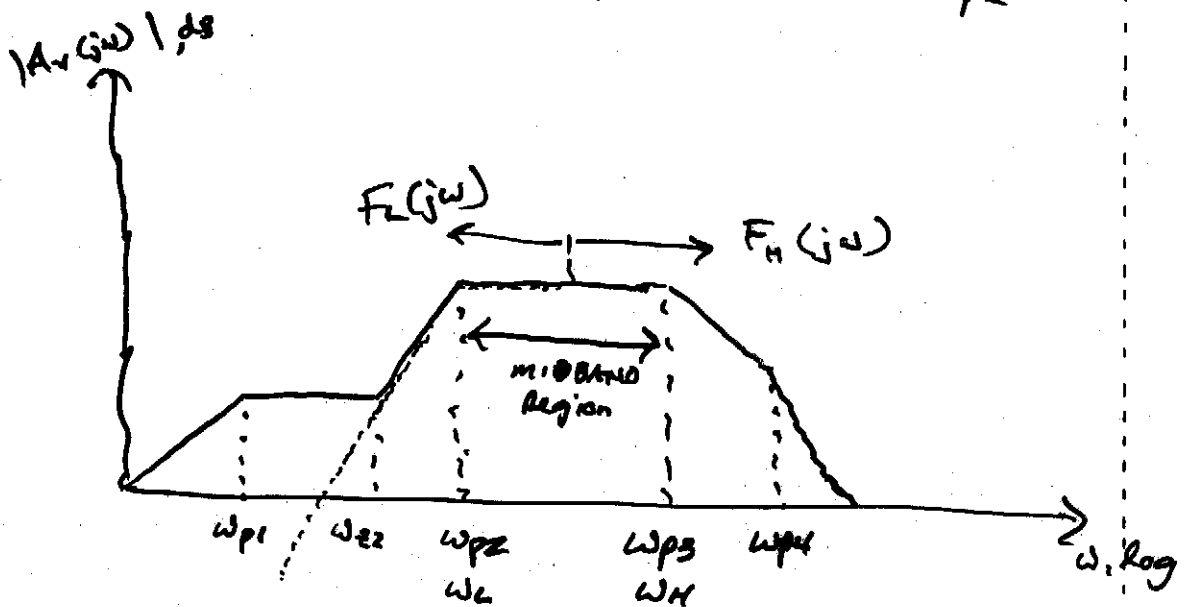Low FREQ. Response

1.) $\omega_L \approx \omega_p$ (dominant) if ω_p (dominant) ≥ 4 (next smallest pole)

2.) $\omega_L \approx \sqrt{\sum_n \omega_{pn}^2 - 2 \sum_n \omega_{zn}^2}$ \Rightarrow estimation in absence of a dominant pole.