

AMPLIFIER FREQ. RESPONSE (CONT.)

High FREQ. RESPONSE (1.) $\omega_H \approx \omega_p$ (dominant) if $\omega_p \leq \frac{1}{4}$ (next lowest pole)


$$2.) \omega_H = \frac{1}{\sqrt{\sum_n \frac{1}{\omega_{pn}^2} - 2 \sum_n \frac{1}{\omega_{zn}^2}}}$$

17.2 FINDING Poles/ZEROS

- 1.) Direct analysis
- 2.) Approximate methods

17.3 SHORT-CIRCUIT TIME CONSTANT METHOD



$$\underline{\omega_L} \approx \sum_{i=1}^n \frac{1}{R_{is} C_i}$$

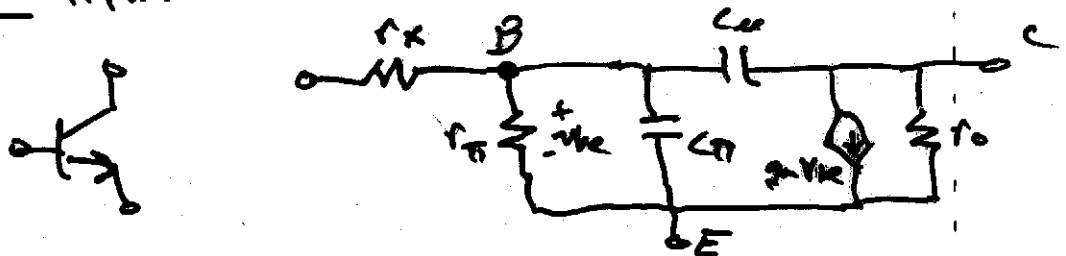17.4/17.5 TRANSISTOR MODELS AT HIGH FREQS1) BJT HYBRID- π 

$$C_{\mu} = \frac{C_{\mu 0}}{\sqrt{1 + \frac{V_{CE}}{\phi_{jc}}}} \quad C_{T} = g_m T_F$$

$$\underline{\text{U.G.B.W.}} \quad \omega_T = \frac{g_m}{C_{\mu} + C_T}$$

2) MOSFET

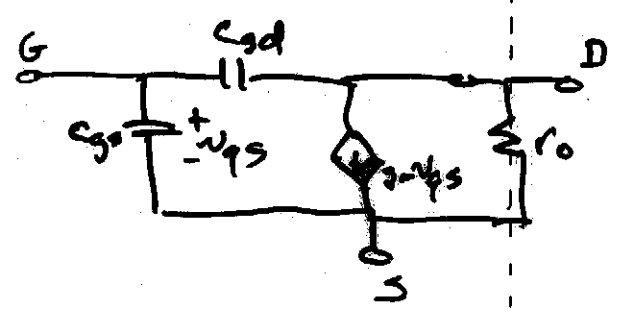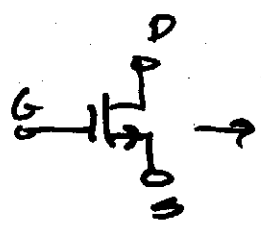

$$\underline{\underline{\omega_T}} = \frac{g_m}{C_{gs} + C_{gd}}$$


17.6 HIGH FREQ Analysis: Goal Find ω_H


- 1.) Direct analysis
- 2.) Approximate 2nd order poly. approximation (polynomial)

17.8 OPEN CIRCUIT TIME-CONSTANT METHOD

$$\omega_H \approx \frac{1}{\sum_{i=1}^m R_{io} C_i}$$

MOSFET Example

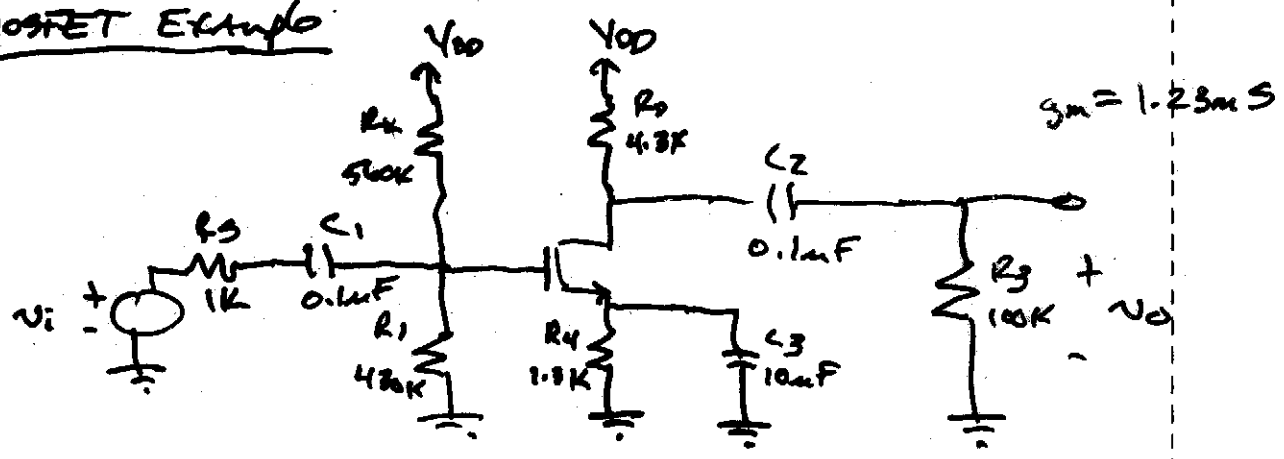

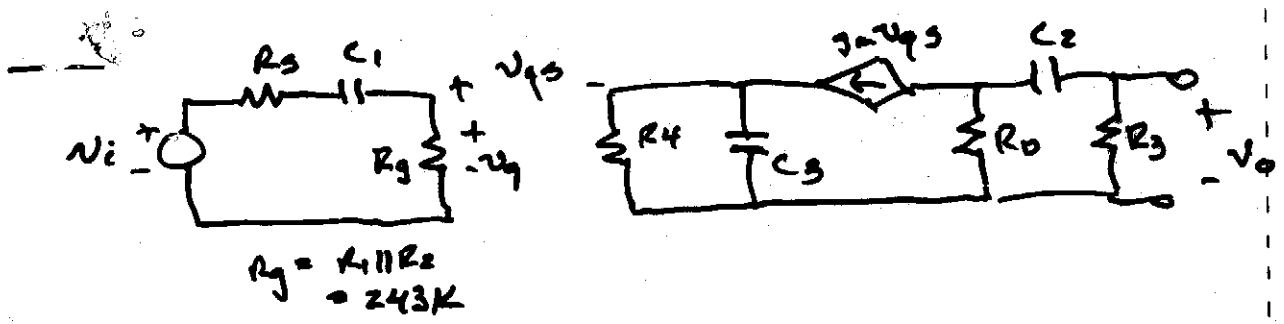

1.) Direct Analysis - only approximation \rightarrow τ_0 large

$$\frac{V_o}{V_i} = \left(\frac{V_o}{V_{gs}} \right) \left(\frac{V_{gs}}{V_g} \right) \left(\frac{V_g}{V_i} \right)$$

$$V_o = -g_m V_{gs} \left(\frac{R_o}{R_o + R_L + \frac{1}{sC_2}} \right) R_L = \frac{-g_m R_L R_o}{R_o + R_L} \left(\frac{s}{s + \frac{1}{C_2(R_o + R_L)}} \right) V_g$$

$$V_{gs} = V_g - V_s = V_g - g_m V_{gs} \left(\frac{R_4 \frac{1}{sC_3}}{R_4 + \frac{1}{sC_3}} \right) = V_g - \frac{g_m R_4}{sC_3 R_4 + 1} V_{gs}$$

$$V_{gs} \left[1 + \frac{g_m R_4}{sC_3 R_4 + 1} \right] = V_g \Rightarrow \frac{V_{gs}}{V_g} = \frac{sC_3 R_4 + 1}{sC_3 R_4 + 1 + g_m R_4}$$

$$\left\{ \frac{V_{gs}}{V_g} = \frac{s + \frac{1}{C_3 R_4}}{s + \frac{1 + g_m R_4}{C_3 R_4}} \right.$$

$$V_g = \frac{R_o}{R_s + R_g + \frac{1}{sC_1}} V_i = \left(\frac{R_o}{R_s + R_g} \right) \left(\frac{s}{s + \frac{1}{C_1(R_s + R_g)}} \right)$$

$$\frac{V_o(s)}{V_i(s)} = \underbrace{\left[\left(\frac{-g_m R_L R_o}{R_o + R_L} \right) \left(\frac{R_o}{R_s + R_g} \right) \right]}_{A_{mid}} \underbrace{\left[\frac{s^2 (s + \frac{1}{R_4 C_3})}{\left[s + \frac{1}{C_1(R_s + R_g)} \right] \left[s + \frac{1 + g_m R_4}{R_4 C_3} \right]} \right]}_{F_L(s)}$$


Example (cont)

$$\omega_{p1} = \frac{1}{0.1\mu\text{F}(244\text{K})} = -41 \text{ rad/sec}$$

$$\omega_{p3} = \frac{1}{(0.1\mu\text{F})(104.3\text{K})} = -95.9 \text{ rad/sec}$$

$$\omega_{p2} = - \left(\frac{1 + (1.23)(1.3)}{(1.3\text{K})(10\mu\text{F})} \right) = -200 \text{ rad/sec}$$

$$\therefore f_L = \frac{1}{2\pi} \sqrt{200^2 + 95.9^2 + 41^2 - 2(76.9)^2} = \underline{\underline{31.5 \text{ Hz}}}$$

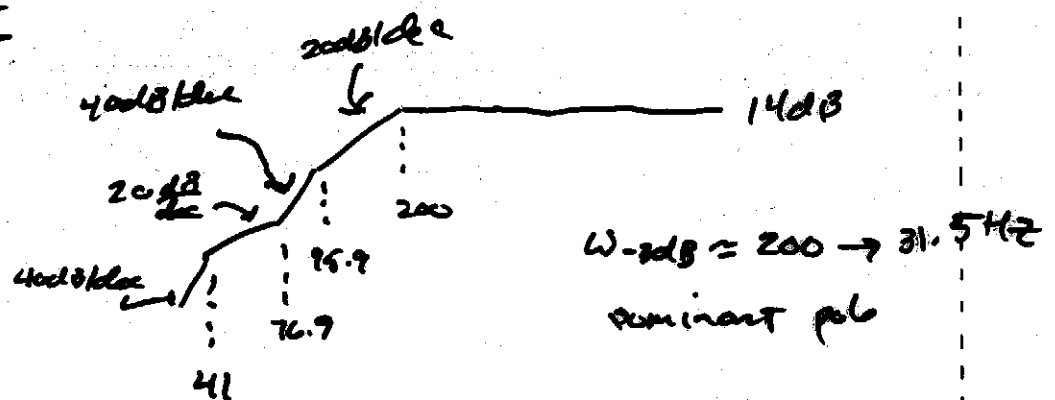Bode Plot2.) Find ω_L by shortcut CXT T.C. method

$$R_{1S} = R_1 + R_6 = 244\text{K}, \quad R_{2S} = R_2 + R_3 = 104.3\text{K}$$

$$R_{3S} = \frac{1}{g_m} \parallel R_4 = \frac{R_4}{1 + g_m R_4} = \frac{1.3\text{K}}{1 + (1.23)(1.3)} = 0.5\text{K}$$

$$\therefore \omega_L = \frac{1}{(244\text{K})(0.1\mu\text{F})} + \frac{1}{(104.3\text{K})(0.1\mu\text{F})} + \frac{1}{(0.5\text{K})(10\mu\text{F})}$$

$$\omega_L = 0.337 \times 10^3 = 337 \text{ rad/sec} \rightarrow 53.6 \text{ Hz}$$