

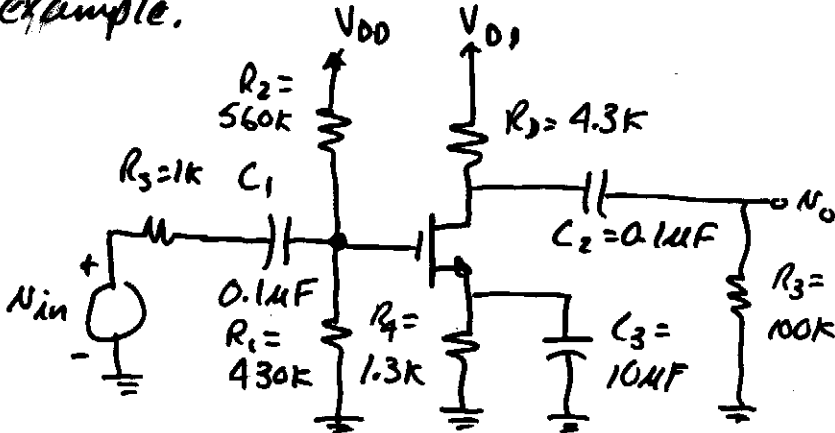


MOSFET Example

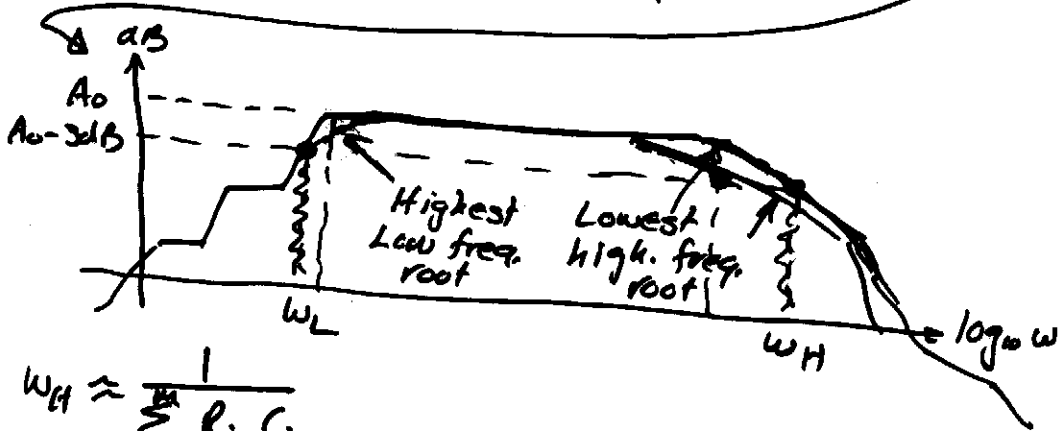Use the OCTC approach to find ω_H of the previous example.




Roots and frequency response -

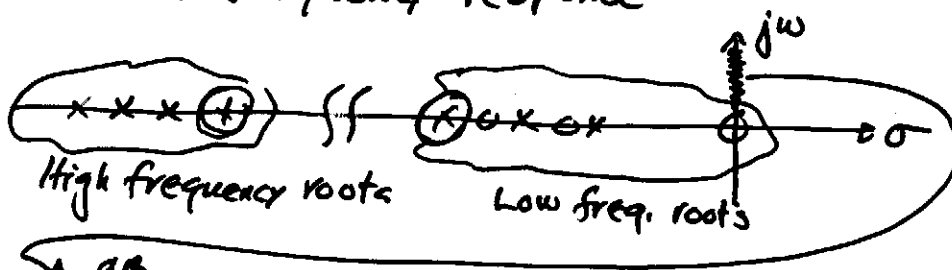


$$\omega_H \approx \frac{1}{\sum_{i=1}^n R_{i0} C_i}$$

where R_{i0} is the resistance seen by C_i with all other capacitors open.


High-frequency s.s. model -

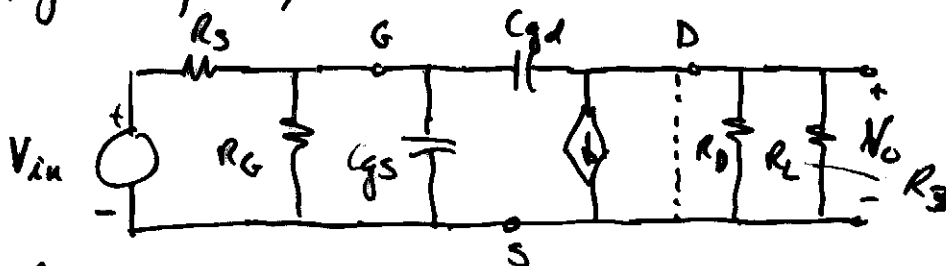

R_{eqs0} :

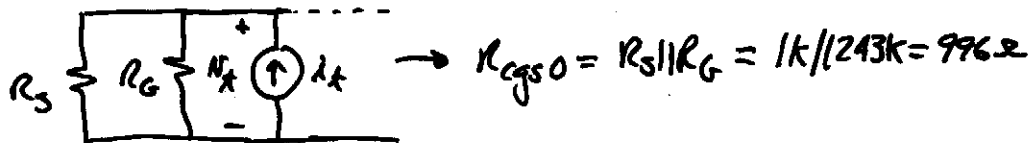

R_{eqd0} :

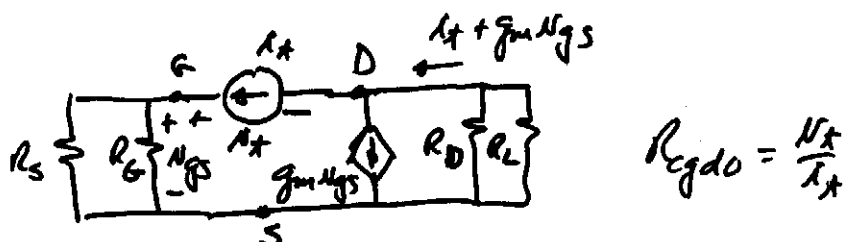

$$i_x = i_x (R_s || R_G) + (i_x + g_m v_{gs}) R_D || R_L$$

$$v_{gs} = i_x (R_s || R_G)$$

$$i_x = i_x \left[(R_s || R_G) + (R_D || R_L) + g_m (R_D || R_L) (R_s || R_G) \right]$$

$$\begin{aligned} \therefore R_{eqd0} &= (R_s || R_G) [1 + g_m (R_D || R_L)] + R_D || R_L \\ &= 0.996k [1 + 5.07] + 4.122k = 10.168k \end{aligned}$$

$$\omega_H \approx \frac{1}{R_{eqs0} C_{gs} + R_{eqd0} C_{gd}} = \frac{1}{(0.996k) 10pF + 10.168k (2pF)}$$

$$33.93 \times 10^6 \text{ rads/sec} \rightarrow \underline{f_H = 5.3 \text{ MHz}}$$

Miller effect (7.22 MHz)

Direct analysis (5.67 MHz)

General Concept-

1.) Find the roots (high freq.)

a.) Direct method $\rightarrow A(s) = \frac{K(s+z_1)}{s^2 + A_1s + A_0}$

b.) Use the approx. polynomial solution (that the roots are real)

$$(s+a)(s+b) = s^2 + A_1s + A_0$$

$$a \approx A_1, \quad b \approx \frac{A_0}{A_1} \quad \text{IF } a \ll b$$

2.) Find ω_H


a.) Dominant root (lowest pole $\approx \omega_H$)

b.) OLC

c.) Miller effect



BJT Example

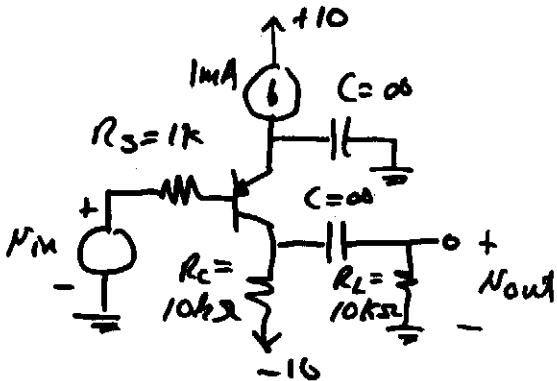

$\beta = 100, C_u = 2pF, V_A = 25mV,$
 $f_T = 500MHz, r_b = r_x = 0\Omega,$
 $r_o = \infty.$ Find ω_H

a.) Find r_{π}, g_m & C_{π}

$$g_m = \frac{I_C}{V_T} = \frac{1mA}{25mV} = \frac{1}{25} = 40mS$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{100 \times 25}{1} = 2.5k\Omega$$

$$C_{\pi} = \frac{g_m}{\omega_T} - C_u = \frac{40mS}{1000\pi \times 10^6} - 2pF$$

$$C_{\pi} = 10.732pF$$

b.) If $r_{\pi} = 1k, g_m = 10mS$
 and $C_{\pi} = 10pF,$ find ω_H .

