
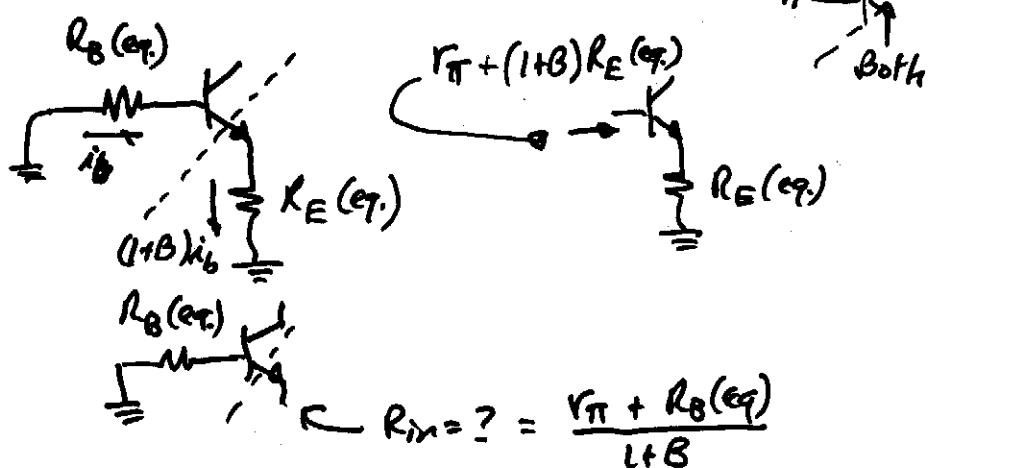


Impedance reflection of BJT

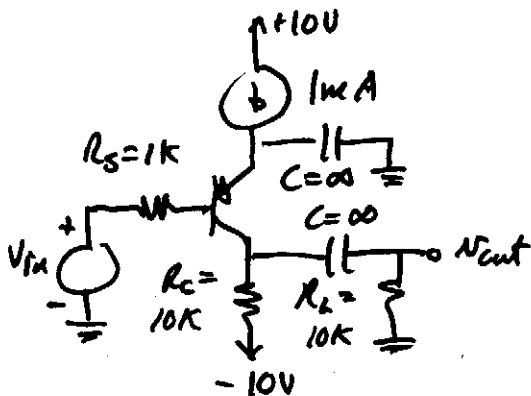

Note that if $R_B(eq) = 0$, that $R_{in}(emitter) = \frac{r_{\pi}}{1+B} = \frac{1}{g_m}$


Back to BJT Example



$\beta = 100, C_{\mu} = 2pF, V_A = 25mV,$
 $f_T = 500MHz, r_x = r_b = 0$ and $V_{be} = 0.7V$

- a.) Find C_{π}, r_{π} and g_m .
- b.) If $r_{\pi} = 1k, g_m = 10mS$ and $C_{\mu} = 10pF$, find f_H .

S.S. High Frequency Model -

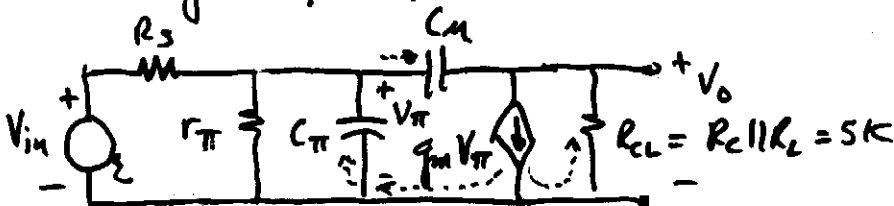


$$MBG = \frac{V_o}{V_{in}} = \left(\frac{V_o}{V_{\pi}} \right) \left(\frac{V_{\pi}}{V_{in}} \right) = (-g_m R_{CL}) \left(\frac{r_{\pi}}{r_{\pi} + R_S} \right) = (-10.5) \left(\frac{1}{2} \right) = \underline{\underline{-25 V_o}}$$

1.) Use the Miller effect to find f_H .

$K = \frac{V_o}{V_{\pi}}$ For the Miller effect to work $R_{CL} \ll \frac{1}{\omega C_{\mu}}$

If $\frac{1}{\omega_H C_M} \gg R_{CL}$, then $K = -g_m(R_{CL} \parallel R_L) = -50V/V$
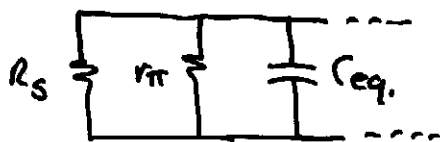
$$C_{eq} = C_{\pi} + C_M(1-K) = 10\mu F + 2\mu F(51) = 112\mu F$$



$$\text{Dominant pole} = \omega_H = \frac{1}{C_{eq}(r_{\pi} \parallel R_s)}$$


$$\omega_H = \frac{1}{(112\mu F)(0.5K)} = \frac{1000 \times 10^6}{56} = 17.86 \text{ Mrads/sec.}$$

$$\underline{\underline{f_H = 2.842 \text{ MHz}}}$$


Check assumption:

$$\frac{1}{\omega_H C_M} = \frac{10^6}{(1786)(2)} = 28K\Omega > 5K\Omega$$


Repeat b) using the OCTC method -

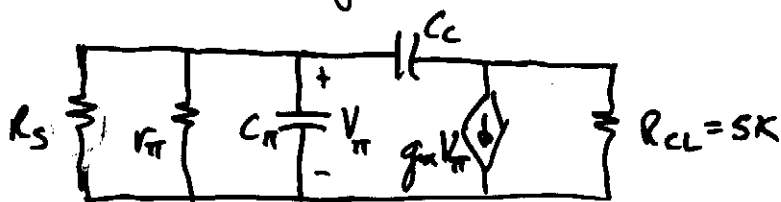

$R_{\pi O}$:

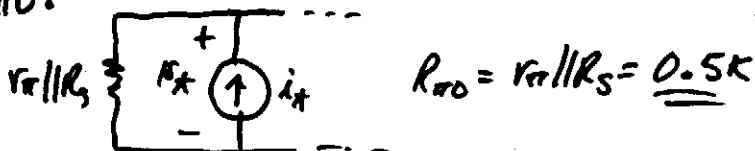

$R_{L O}$:

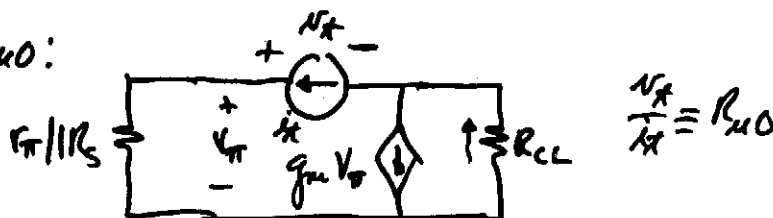

$$V_{\pi} = i_x(r_{\pi} \parallel R_s) + (i_x + g_m V_{\pi})R_{CL} = V_{\pi} + i_x R_{CL} + g_m R_{CL} V_{\pi}$$

$$V_{\pi} = i_x R_{CL} + (1 + g_m R_{CL})(r_{\pi} \parallel R_s) i_x$$

$$R_{L O} = \frac{V_{\pi}}{i_x} = R_{CL} + (1 + g_m R_{CL})(r_{\pi} \parallel R_s) = 5K + (51)(0.5K) = 30.5K$$




Cont'd

$$\omega_H \approx \frac{1}{R_{T0} C_T + R_{M0} C_M} = \frac{10^9}{(0.5)(10) + (30.5)(2)} = 15.06 \text{ Mrads/sec}$$


$$f_H = \frac{15.06}{2\pi} \text{ MHz} = 2.4 \text{ MHz}$$

Low frequency analysis:

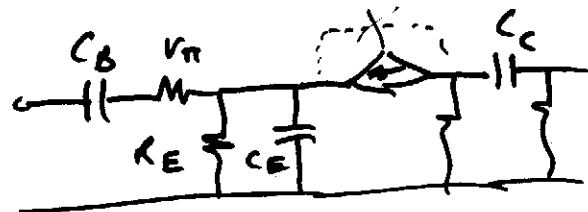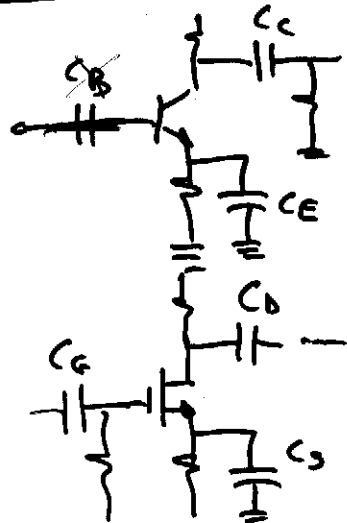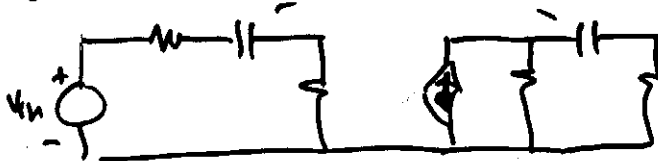If the capacitances (coupling & bypass) are isolated from each other, then direct analysis and the SCTC give the same results.



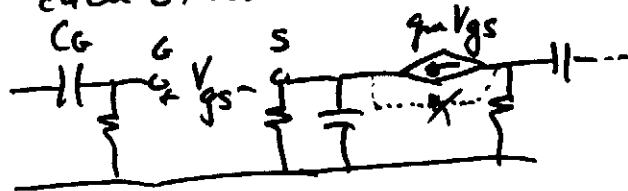C_B and C_E are NOT isolated from each other



Next:

- 1.) MBG & ω_H of an emitter follower
- 2.) MBG & ω_H of a diff. amp.