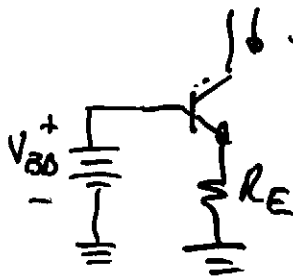


CHAPTER 18 - FEEDBACK

Feedback is a great conceptual tool, however it is a somewhat poor analytical tool.



Suppose I_C increases

$$1.) I_C \uparrow \Rightarrow I_E \uparrow$$


$$2.) I_E \uparrow \Rightarrow V_E \uparrow$$

$$3.) V_E \uparrow \Rightarrow V_{BE} \downarrow$$

$$4.) V_{BE} \downarrow \Rightarrow I_C \downarrow$$

Classic Single Loop Feedback

Block diagram -

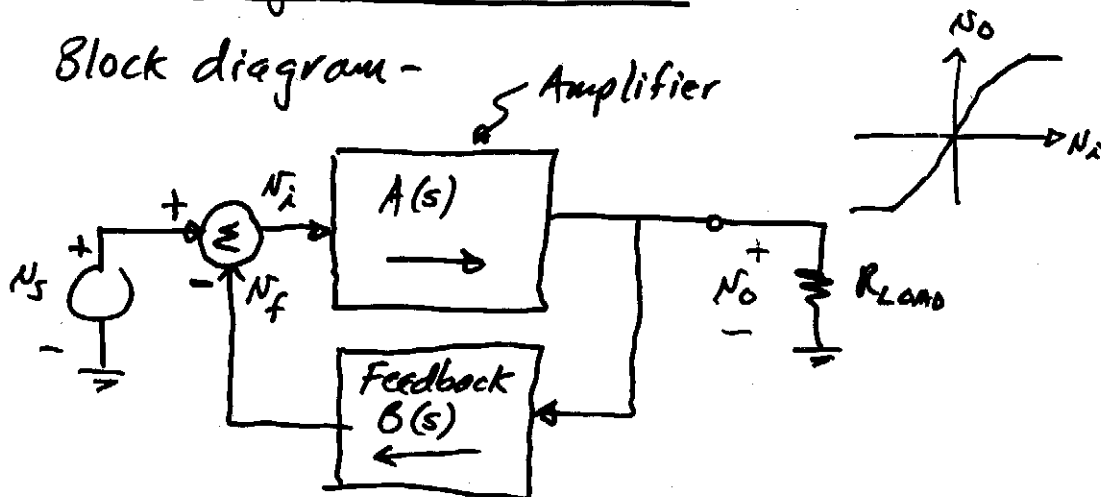

$$N_o = A(s) N_i = A(s) [N_s - N_f] = A(s) N_s - A(s) [B(s) N_o]$$

$$N_o [1 + A(s) B(s)] = A(s) N_s$$

$$\therefore \text{Closed loop voltage gain} = \boxed{\frac{N_o}{N_s} = \frac{A(s)}{1 + A(s) B(s)}}$$

$$\text{Loop gain} \equiv T(s) = A(s) B(s) \rightarrow \frac{N_o}{N_s} = \frac{A(s)}{1 + T(s)}$$

$$\text{If } A(s) B(s) \gg 1, \text{ then } \frac{N_o}{N_s} \rightarrow \frac{1}{B(s)}$$

Positive feedback: $T(s) < 0$


Negative feedback: $T(s) > 0$

Types of Amplifiers

Type	Input Variable	Output Variable
VCVS	Voltage (series)	Voltage (shunt)
CCVS	Current (shunt)	Voltage (shunt)
CCCS	Current (shunt)	Current (series)
VCCS	Voltage (series)	Current (series)

Voltage Amplifiers - Series-Shunt Feedback

Topology

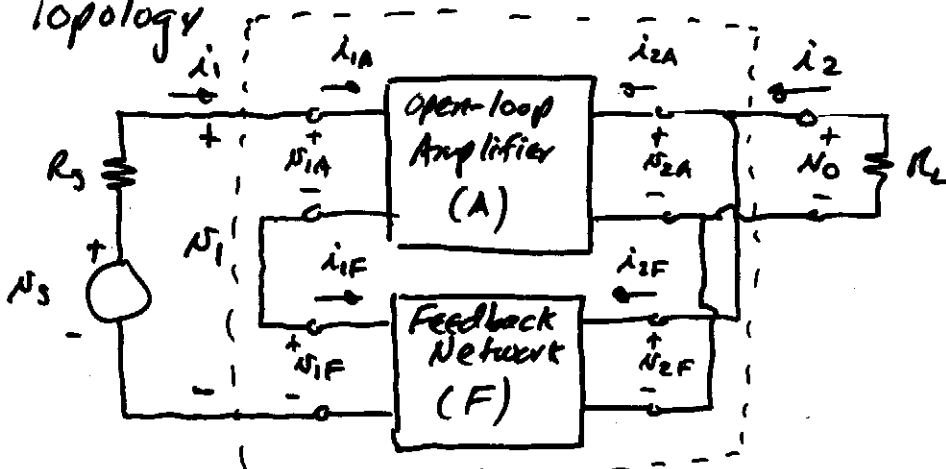

h-parameters -

$$N_1 = h_{11} i_1 + h_{12} N_2$$

$$i_2 = h_{21} i_1 + h_{22} N_2$$

Feedback network:

$$N_{1F} = h_{11F} i_{1F} + h_{12F} N_{2F}$$

$$i_{2F} = h_{21F} i_{1F} + h_{22F} N_{2F}$$

Amplifier:

$$N_{1A} = h_{11A} i_{1A} + h_{12A} N_{2A}$$

$$i_{2A} = h_{21A} i_{1A} + h_{22A} N_{2A}$$

Total (dotted box):

$$N_1 = h_{11T} i_1 + h_{12T} N_0$$

$$i_2 = h_{21T} i_1 + h_{22T} N_0$$

$$\therefore N_1 = (h_{11A} + h_{11F}) i_1 + (h_{12A} + h_{12F}) N_0$$

$$i_2 = (h_{21A} + h_{21F}) i_1 + (h_{22A} + h_{22F}) N_0$$

We observe that for a "good" amplifier $h_{12A} \rightarrow 0$
and for a "good" feedback network $h_{21F} \rightarrow 0$

As a consequence, we can write the total h-parameters as,

$$N_1 \approx h_{11T} i_1 + h_{12F} N_0$$

$$i_2 \approx h_{21A} i_1 + h_{22T} N_0$$

Recall that $N_1 = N_S + i_1 R_S$

$$\text{or } N_S = N_1 + i_1 R_S$$

$$\text{and } N_0 = -i_2 R_L$$

$$\therefore N_S = h_{11T} i_1 + h_{12F} N_0 + i_1 R_S \rightarrow N_S = (h_{11T} + R_S) i_1 + h_{12F} N_0$$

$$\rightarrow -\frac{N_0}{R_L} = h_{21A} i_1 + h_{22T} N_0 \rightarrow 0 = h_{21A} i_1 + \left(h_{22T} + \frac{1}{R_L} \right) N_0$$

$$\text{Solve for } \frac{N_0}{N_S} = \frac{A}{1 + AF}$$

$$i_1 = -\frac{(h_{22T} + G_L)}{h_{21A}} N_0$$

$$N_S = (h_{11T} + R_S) i_1 + h_{12F} N_0$$

$$\frac{N_0}{N_S} = \frac{+h_{21A}}{h_{12F} h_{21A} - (h_{11T} + R_S)(h_{22T} + G_L)}$$

$$\frac{N_0}{N_S} = \frac{-h_{21A}}{(R_S + h_{11T})(G_L + h_{22T})} = \frac{A}{1 + AF}$$

$$A = \frac{-h_{21A}}{(R_S + h_{11T})(G_L + h_{22T})}$$

$$F = h_{12F}$$