

Voltage Amplifier - Series Shunt Feedback - Cont'd

$$\beta = h_{12F}, \quad A = \frac{-h_{21A}}{(R_S + h_{11T})(h_{22T} + G_L)}, \quad R_{in} = R_S + h_{11T}$$

$$R_{out} = \frac{1}{h_{22T} + G_L}$$


$$A_F = \frac{A}{1 + A\beta}, \quad R_{inF} = R_{in}(1 + A\beta), \quad \text{and} \quad R_{outF} = \frac{R_{out}}{1 + A\beta}$$

Summary of Series-Shunt Fb. Analysis -

- 1.) Find h_{11T} (h_{11E} and h_{11A}) - input resistance w. output S.C.
- 2.) Find h_{22T} (h_{22E} and h_{22A}) - output conductance w. input O.C.
- 3.) Find $h_{12F} = \beta$
- 4.) Find A ($\beta = 0$) includes h_{11F} & h_{22E}
- 5.) $A_F = \frac{A}{1 + A\beta}$
- 6.) $R_{inF} = R_{in}(\beta = 0) [1 + A\beta]$
- 7.) $R_{outF} = \frac{R_{out}(\beta = 0)}{1 + A\beta}$

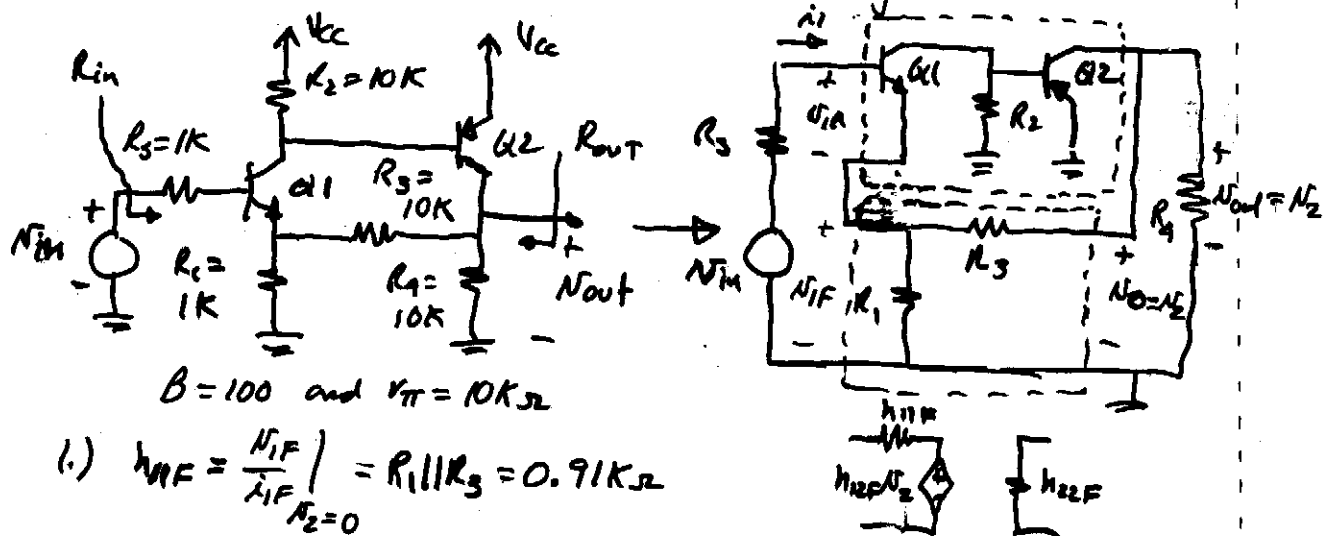Example of Series-Shunt Feedback


Find R_{inF} , R_{outF} and A_F for the following circuit -




$$2.) h_{22F} = \left. \frac{V_{2F}}{I_{2F}} \right|_{i_1=0} = \frac{1}{R_1 + R_3} = \frac{1}{11k}$$

$$3.) h_{12F} = \beta = \left. \frac{V_{1F}}{I_{2F}} \right|_{i_1=0} = \frac{R_1}{R_1 + R_3} = \frac{1}{11}$$

4) ($\beta = 0$)

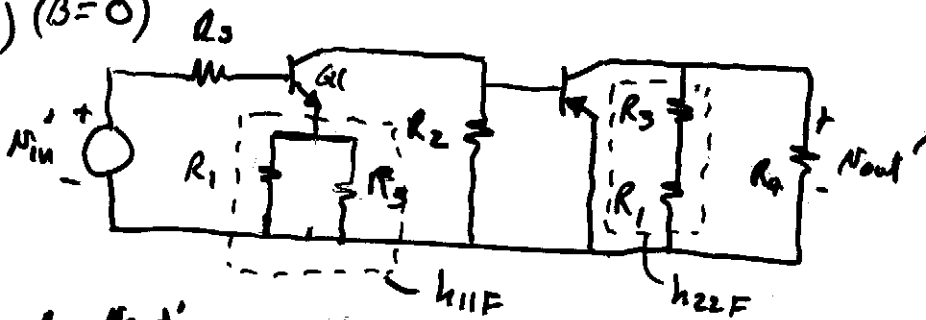

$$A = \frac{N_{out'}}{N_{in}'}$$

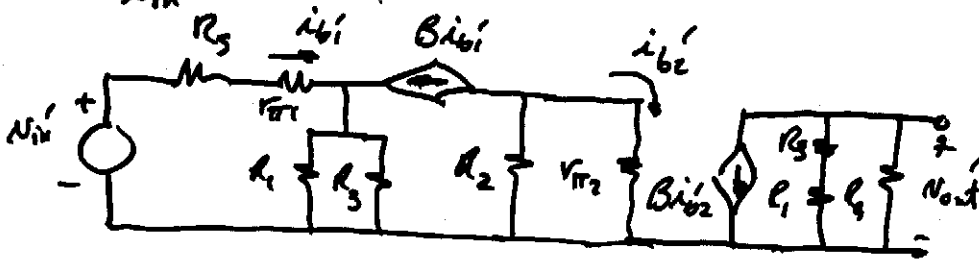

$$\frac{N_{out'}}{N_{in}'} = \left(\frac{N_{out}'}{V_{b2}'} \right) \left(\frac{V_{b2}'}{i_{b2}'} \right) \left(\frac{i_{b2}'}{i_{b1}'} \right) \left(\frac{i_{b1}'}{N_{in}'} \right)$$

\uparrow
 $\frac{1}{R_{in}}$